



Chapter 9


Input/Output (I/O) Ports and Interfacing

Updated: 3/13/12

Basic Concepts in I/O Interfacing and PIC18 I/O Ports (1 of 2)

- I/O devices (or peripherals) such as LEDs and keyboards are essential components of the microprocessor-based or microcontroller-based systems.
 - Classified into two groups
 - input devices
 - output devices

Block Diagram of I/O Interfacing

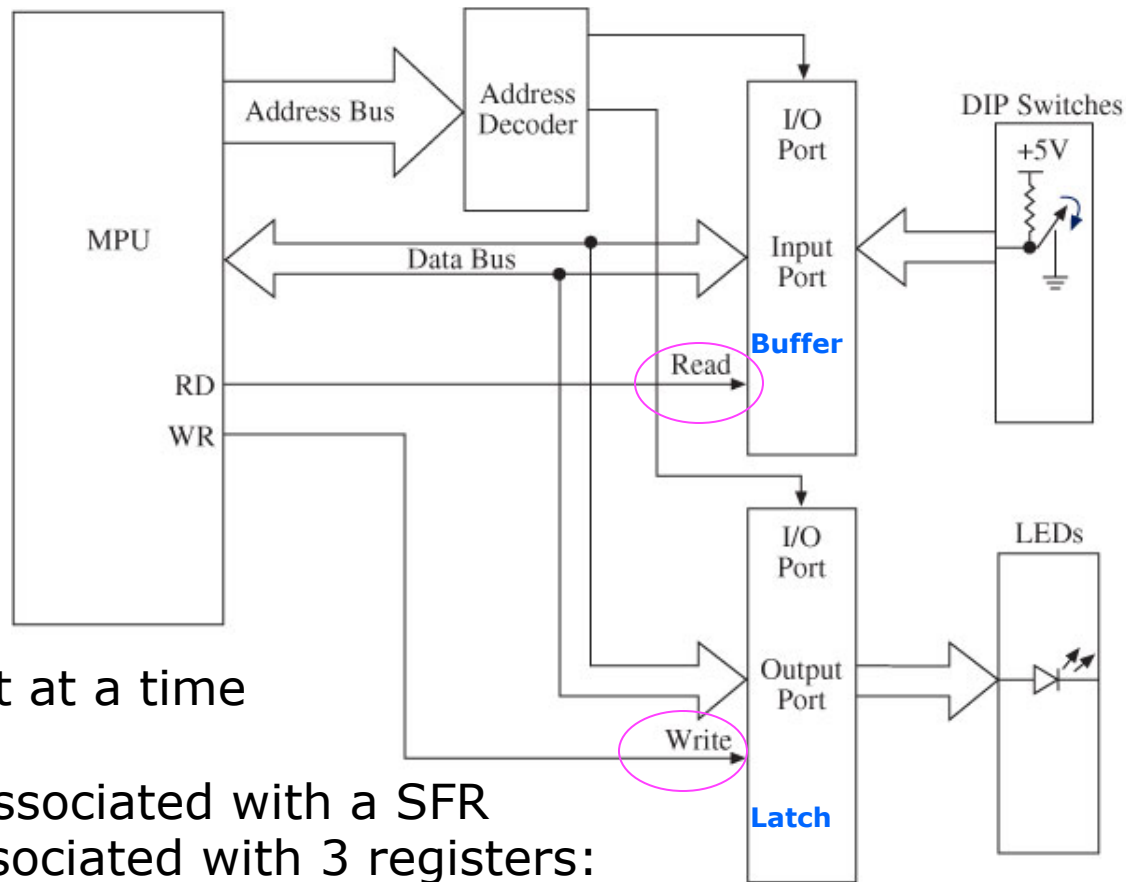

Access one port at a time
8-bit registers
I/O ports are associated with a SFR
Each port is associated with 3 registers:
PORT / LAT / TRIS


I/O Ports:

Interfacing and Addressing

- ❑ To read (receive) binary data from an input peripheral
 - MPU **places the address** of an input port on the address bus, **enables the** input port by asserting the RD signal, and **reads data** using the data bus.
- ❑ To write (send) binary data to an output peripheral
 - MPU **places the address** of an output port on the address bus, **places data** on data bus, and **asserts the WR** signal to enable the output port.
- ❑ Remember:
 - Writing to the port
 - ❑ When the MPU sends out or transfers data to an output port
 - Reading from the port
 - ❑ When the MPU receives data from an input port

PIC18F452/4520 I/O Ports (1 of 5)

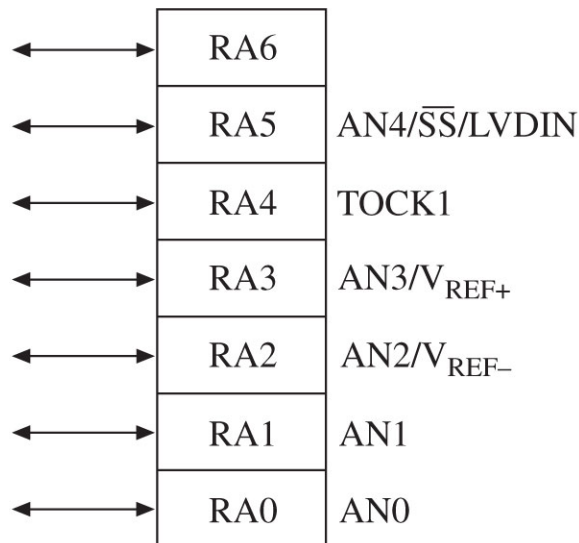- MCU includes five I/O ports
 - PORTA, PORTB, PORTC, PORTD, and PORTE
- Ports are multiplexed meaning they can be set up by writing instructions to perform various functions



PORTA: Example of Multiple Functions

- Digital I/O: RA6-RA0
- Analog Input: AN0-AN4
- V_{REF+} : A/D Reference Plus Voltage
- V_{REF-} : A/D Reference Minus Voltage
- TOCK1: Timer0 Ext. Clock
- SS: SPI Slave Select Input
- LVDIN: Low voltage Detect Input

PIC18F452/4520 I/O Ports (2 of 5)

- Each I/O port is associated with the special functions registers (SFRs) to setup various functions.
 - Can be set up as entire ports or each pin can be set up.
 - **PORT**: This register functions as a latch or a buffer determined by the logic levels written into the associated TRIS register.
 - **TRIS**: This is a data direction register. Writing logic 0 to a pin sets up the pin as an output pin, and logic 1 sets up the pin as an input pin.
 - **LAT**: This determines if port is bidirectional .

PIC18F452/4520 I/O Ports (3 of 5)


- Internal block diagram of PORTB includes:
 - Three internal D flip-flops (latches)
 - Data latch to output data
 - TRIS latch to setup data direction
 - Input latch for input data

PIC18F452/4520 I/O Ports (4 of 5)

□ PORTB Internal Block Diagram

Three internal D flip-flops (latches):

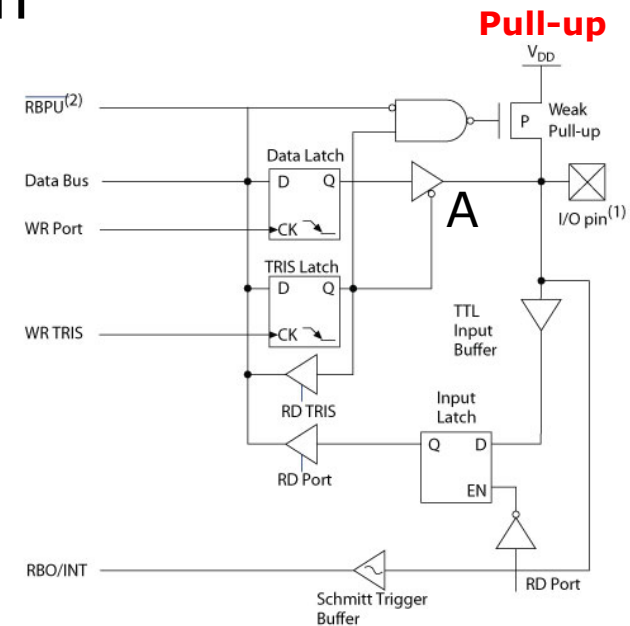- Data latch to output data
- TRIS latch to setup data direction
- Input latch for input data




Not **Q- TRIS: 0 → A is enabled**

Q- TRIS: 1 → A is disabled

Interfacing Output Peripherals (1 of 2)

- Commonly used output peripherals in embedded systems are
 - LEDs, seven-segment LEDs, and LCDs; the simplest is LED
- Two ways of connecting LEDs to I/O ports:
 - LED cathodes are grounded and logic 1 from the I/O port turns on the LEDs - The current is supplied by the I/O port called **current sourcing**.
 - LED anodes are connected to the power supply and logic 0 from the I/O port turns on the LEDs - The current is received by the chip called **current sinking**.

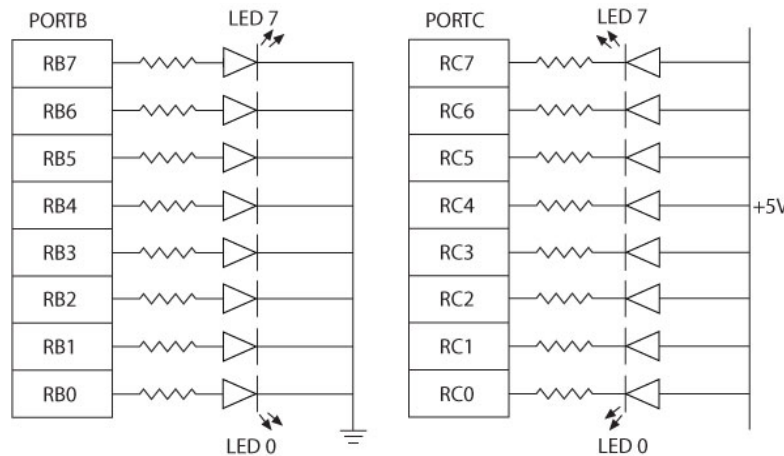

Common Cathode
Active high


Common Anode
Active low

Interfacing Seven-Segment LEDs as an Output (1 of 4)

□ Seven-segment LEDs

- Often used to display BCD numbers (1 through 9) and a few alphabets
- A group of eight LEDs physically mounted in the shape of the number eight plus a decimal point as shown in Figure 9-5 (a)
- Each LED is called a **segment** and labeled as 'a' through 'g'.

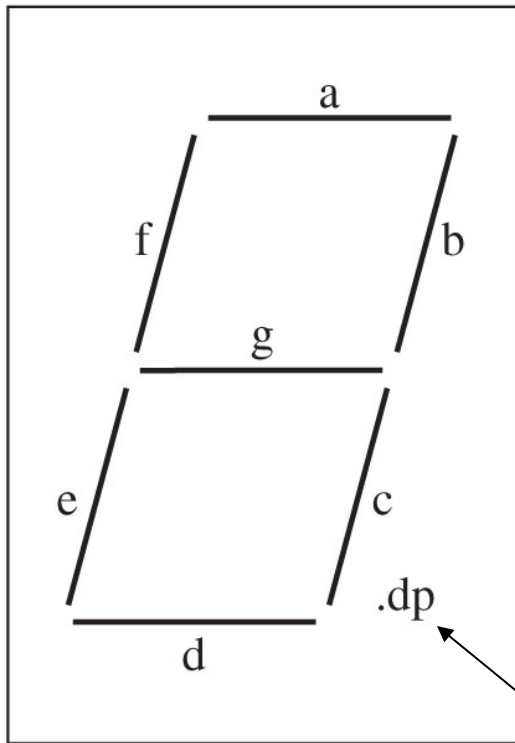
Interfacing Seven-Segment LEDs as an Output (2 of 4)



- Two types of seven-segment LEDs
 - Common anode
 - Common cathode


decimal point

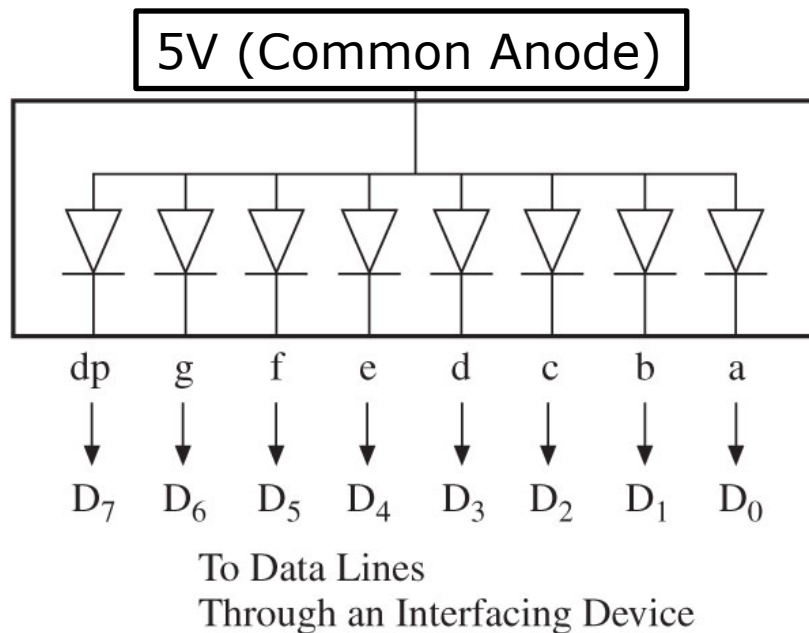Interfacing Seven-Segment LEDs as an Output (3 of 4)





- ❑ In a common anode seven-segment LED
 - All anodes are connected together to a power supply and cathodes are connected to data lines
- ❑ Logic 0 turns on a segment.
- ❑ Example: To display digit 1, all segments except b and c should be off.
- ❑ Byte 11111001 = F9H will display digit 1.

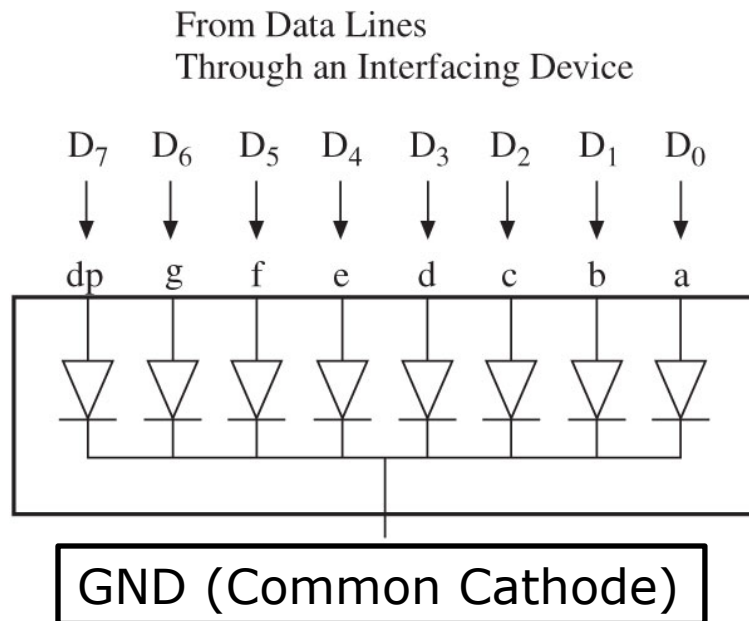Interfacing Seven-Segment LEDs as an Output (4 of 4)





- ❑ In a common cathode seven-segment LED
 - All cathodes are connected together to ground and the anodes are connected to data lines
- ❑ Logic 1 turns on a segment.
- ❑ Example: To display digit 1, all segments except b and c should be off.
- ❑ Byte 00000110 = 06H will display digit 1.


Segment LEDs to PORTB and PORTC

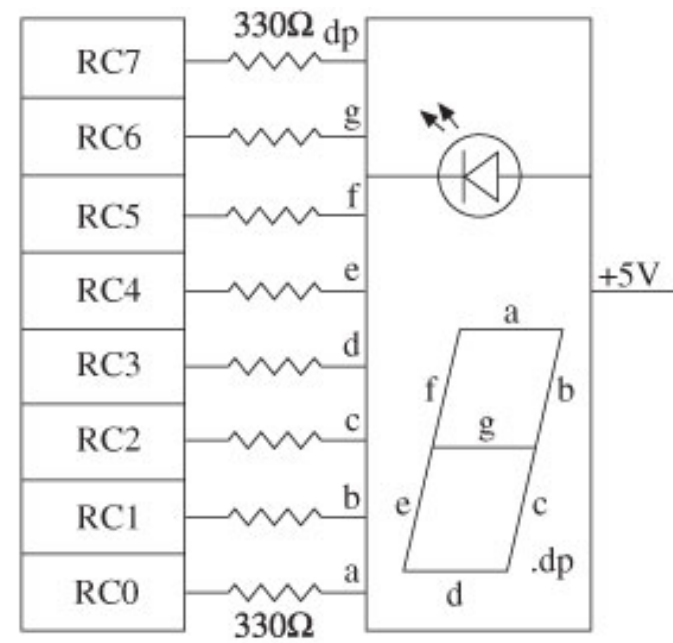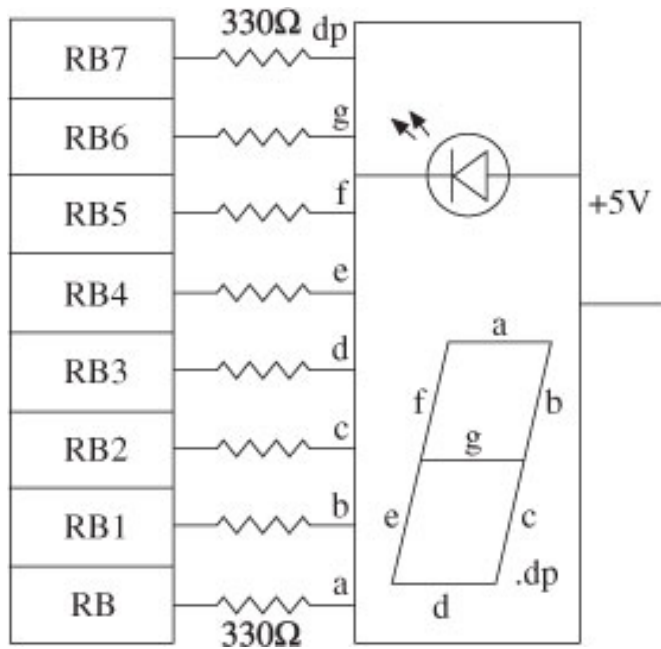

Seven-Segment Chips

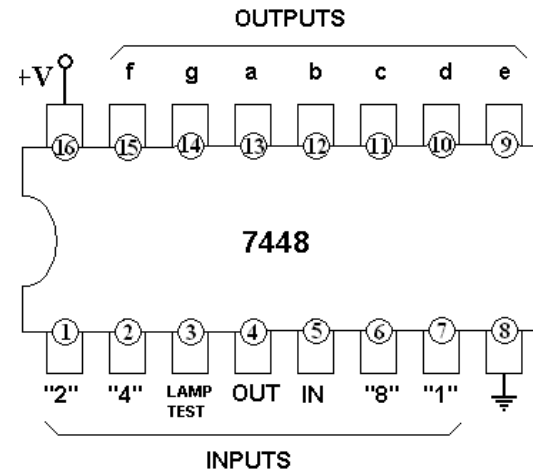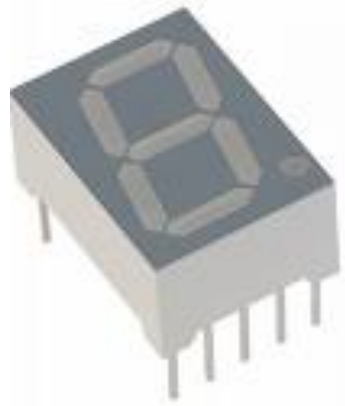

**ALPHA/
NUMERIC C/A
DISPLAY**

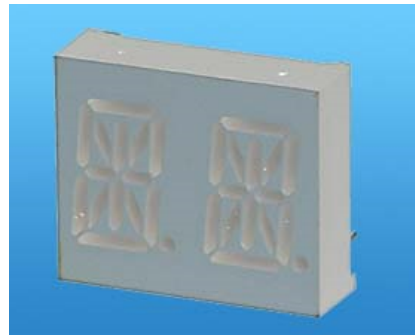


Sample Program


```

0001      Title "Ex9-4 BCD Digit Display"
0002      List p=18F452, f =inhx32
0003      #include <p18F452.inc>          ;This is a header file
0004
0005 REGO   EQU    0x00
0006 NUMBER EQU    0x9
0007
0008      ORG      00
0009
0010      GOTO     0x20
0011
0012 START:  CLRF   PORTB          ;Initial reading of PORTB
0013
0014      CLRF    TRISB           ;Set up PORTB as output
0015
0016      MOVLW   NUMBER          ;BCD code for digit 9
0017
0018      MOVLW   UPPER CODEADDR  ;Copy upper 16-bit of code address
0019
0020      MOVWF   TBLPTRU         ;21-bit pointer to upper 16-bit
0021
0022      MOVLW   HIGH CODEADDR   ;Copy high 8-bit of code address
0023
0024      MOVWF   TBLPTRH         ;21-bit pointer to high 8-bit
0025
0026      MOVLW   LOW CODEADDR    ;Copy low 13-bit of code address
0027
0028      MOVWF   TBLPTRL        ;21-bit pointer to low 13-bit
0029
0030      MOVF    REGO, 0, 0
0031
0032      ADDWF   TBLPTRL, 1, 0
0033
0034      TBLRD*
0035
0036      MOVFF   TABLAT, PORTB   ;Turn on LED
0037
0038
0039      ORG     0x40             ;Store LED code starting at location 0040H
0040
0041 CODEADDR: DB    0xc0, 0xF9, 0xA4, 0xB0, 0x99 ;LED code for digits 0 to 4
0042          DB    0x92, 0x82, 0xF8, 0x80, 0x98 ;LED code for digits 5 to 9

```

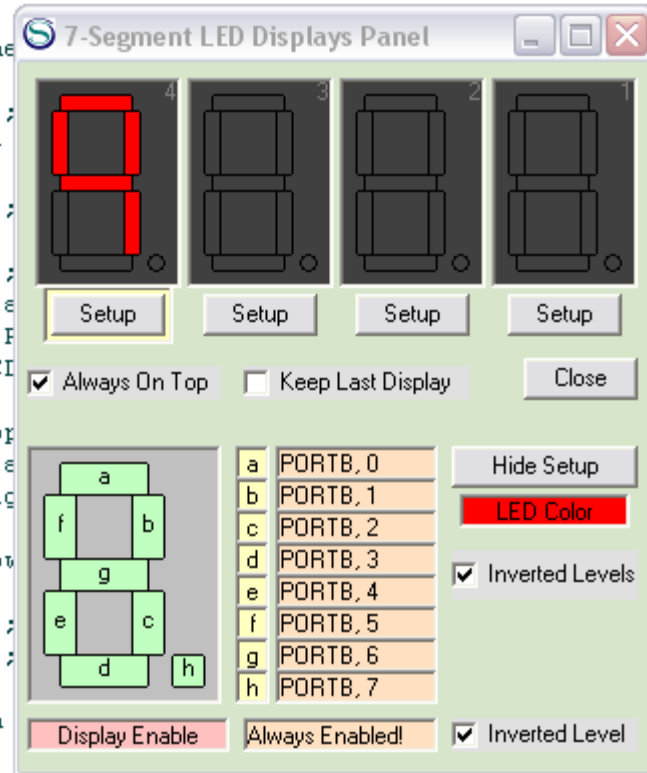

Interfacing to Multiple 7-Segments

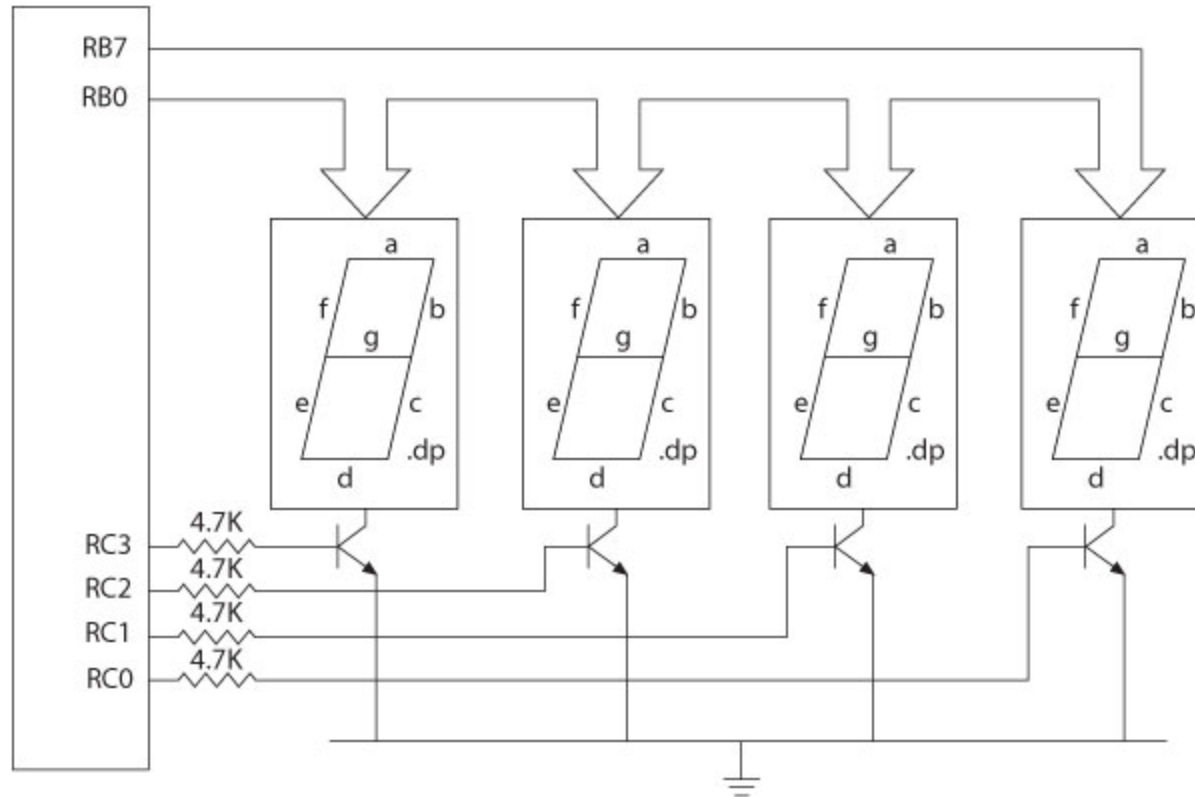

Using the Simulator

File Simulation Rate Tools Options Help STEP

Program Location: C:\Microchip_projects\Illust9-8 Multiplex Seven Segment.hex
Microcontroller: PIC18F4520 Clock Frequency: 8.0 MHz

Last Instruction: **MOVLW 0x02** Next Instruction: **MOVWF 0x011A**

Instructions Counter: 307 Clock Cycles Counter: 1500

Program Counter and Working Register
PC: 00003E
W Register (WREG): 02

Real Time Duration: 187.50 µs

Special Function Registers (SFRs)

Address and Name	Hex Value	Binary Value
FFFh TOSU	00	
FFEh TOSH	00	
FFDh TOSL	00	
FFCh STKPTR	00	
FFBh PCLATU	00	
FFAh PCLATH	00	
FF9h PCL	3E	
FF8h TBLPTRU	00	
FF7h TBLPTRH	00	
FF6h TBLPTRL	00	
FF5h TABLAT	00	
FF4h PRODH	00	
FF3h PRODL	00	
FF2h INTCON1	00	
FF1h INTCON2	F5	
FF0h INTCON3	C0	

General Purpose Registers (GPRs)

Addr.	Hex Value	Addr.	Hex Value
00Ch	00	01Ch	00
00Dh	00	01Dh	00
00Eh	00	01Eh	00
00Fh	00	01Fh	00
010h	00	020h	7D
011h	00	021h	3F
012h	00	022h	3F
013h	00	023h	5B
014h	00	024h	00
015h	00	025h	00
016h	00	026h	00
017h	00	027h	00
018h	00	028h	00
019h	00	029h	00
01Ah	00	02Ah	00
01Bh	00	02Bh	00

7-Segment LED Displays Panel

Setup Setup Setup Setup

Always On Top Keep Last Display

LED Color Inverted Levels


Display Enable: PORTC, 3 Inverted Level

Segment	Port
a	PORTB, 0
b	PORTB, 1
c	PORTB, 2
d	PORTB, 3
e	PORTB, 4
f	PORTB, 5
g	PORTB, 6
h	PORTB, 7

Interfacing Input Peripherals



- ❑ Commonly used input peripherals in embedded systems are:
 - DIP switches, push-button keys, keyboards, and A/D converters.
- ❑ DIP switch: One side of the switch is tied high (to a power supply through a resistor called a pull-up resistor), and the other side is grounded. The logic level changes when the position is switched.
- ❑ Push-button key: The connection is the same as in the DIP switch except that contact is momentary.

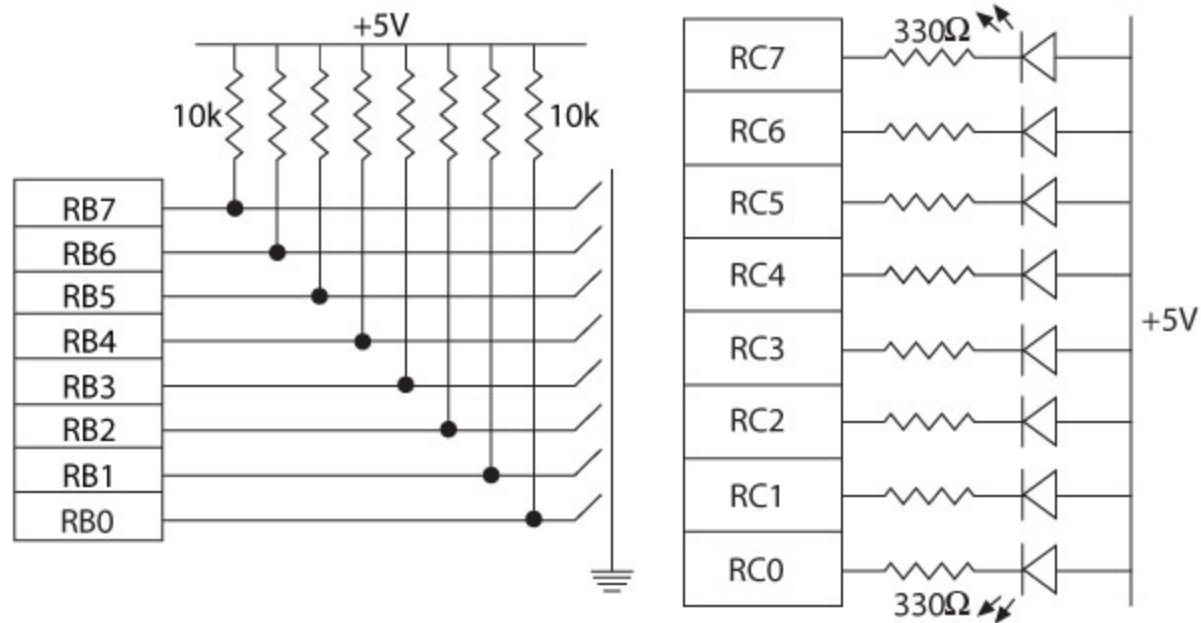Interfacing Dip Switches and Interfacing LEDs



Driving a RELAY & SOLENOID

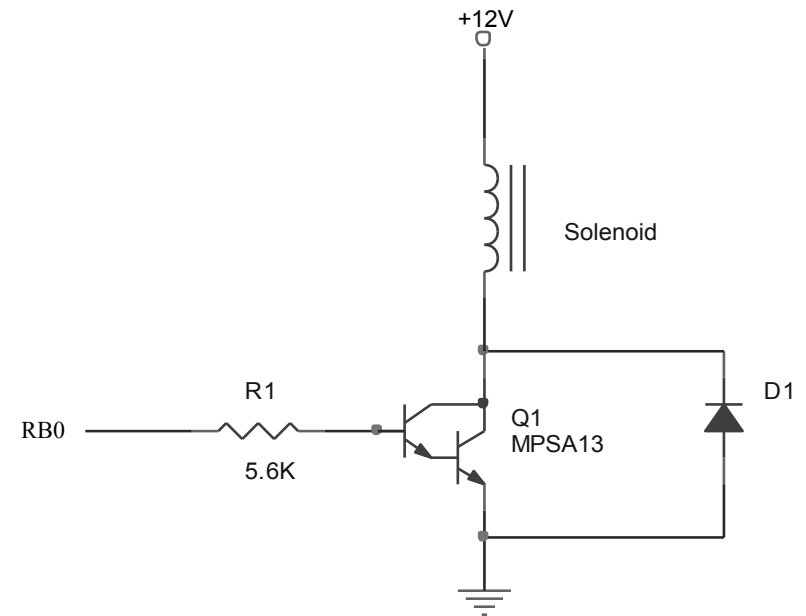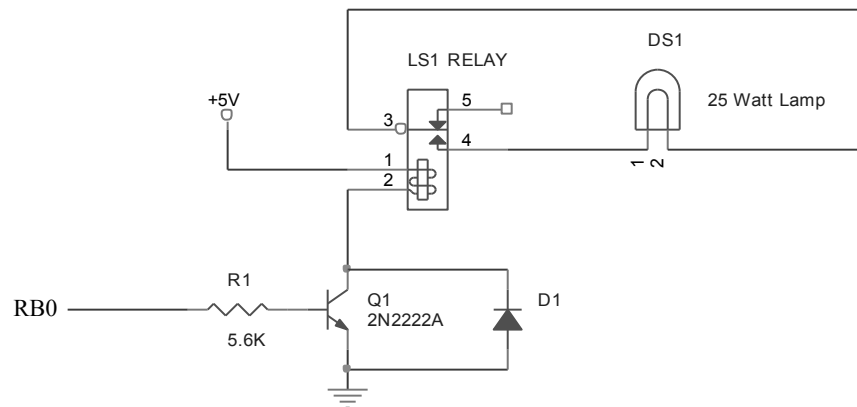- Controlling appliances
- Driving solenoid




Example: Reading from an I/O Port

- ❑ The instruction: **MOVF PORTB, W** reads from PORTB.
- ❑ To execute the instruction, the MPU does the following:
 - Reads the instruction from memory
 - Places the address of PORTB (F81H) on the address bus of data memory
 - Selects PORTB
 - Asserts the RD signal and enables PORTB
 - Reads logic levels (1/0) of the switches and places on the data bus
 - Saves the reading in the WREG

Internal Pull-Up Resistor (2 of 2)

- Bit7 (RBPU) in the INTCON2 register enables or disables the pull-up resistor
 - Instruction to Enable Pull Up Resistors:
BCF INTCON2 7, 0

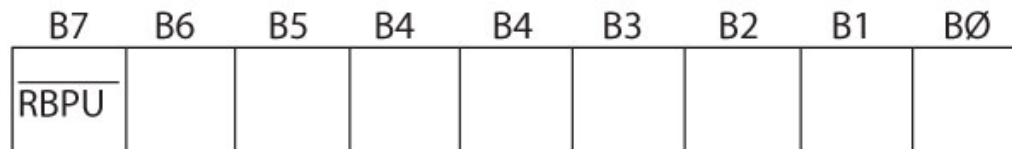C Code: `INTCON2bit.RBPU = 0 // pull-ups on`





$\overline{\text{RBPU}}$ = PORTB pull-up resistor enable bit
0 = Pull-up resistors are enabled
1 = Pull-up resistors are disabled


Interfacing Push-Button Keys (1 of 2)

- Electrical connection of a push-button key is same as that of a DIP switch except that the connection is temporary when the key is pressed.
 - When a key is pressed (or released), mechanical metal contact bounces and can be read as multiple inputs.
 - The reading of one contact as multiple inputs can be eliminated by a key-debounce technique, using either hardware or software.

Interfacing Push-Button Keys (2 of 2)

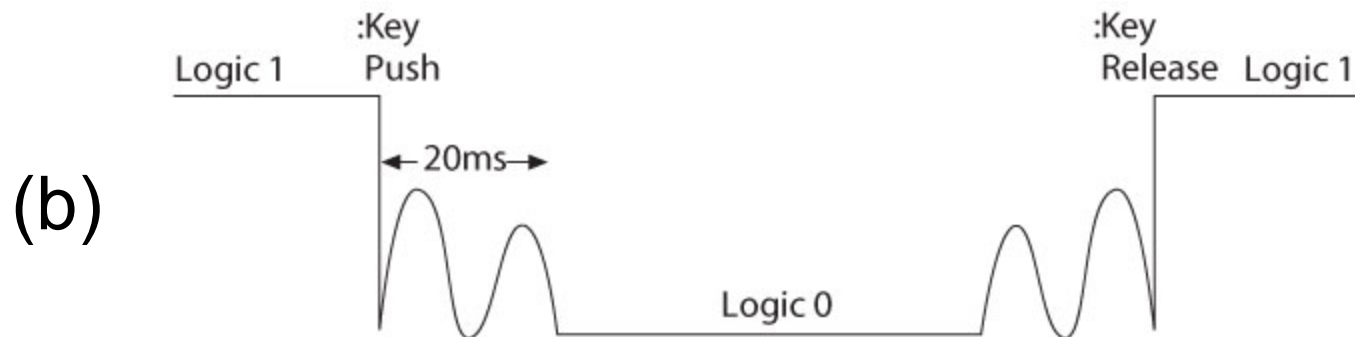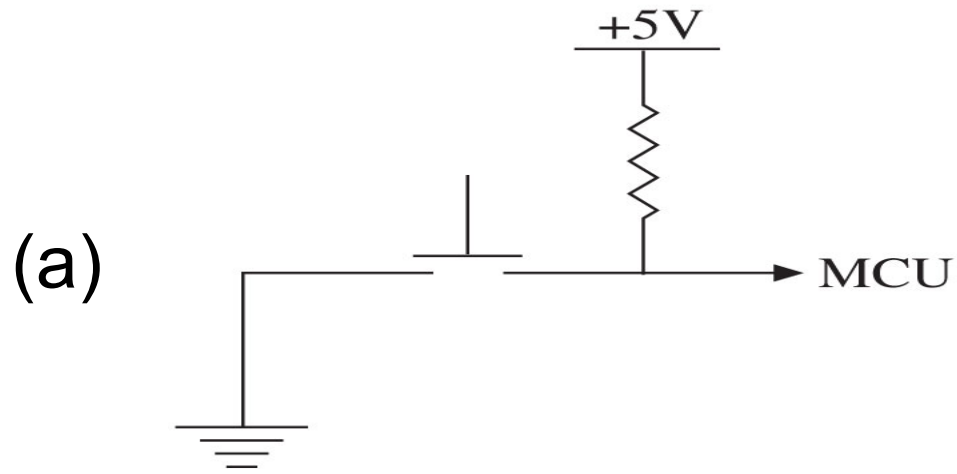

Various Switches

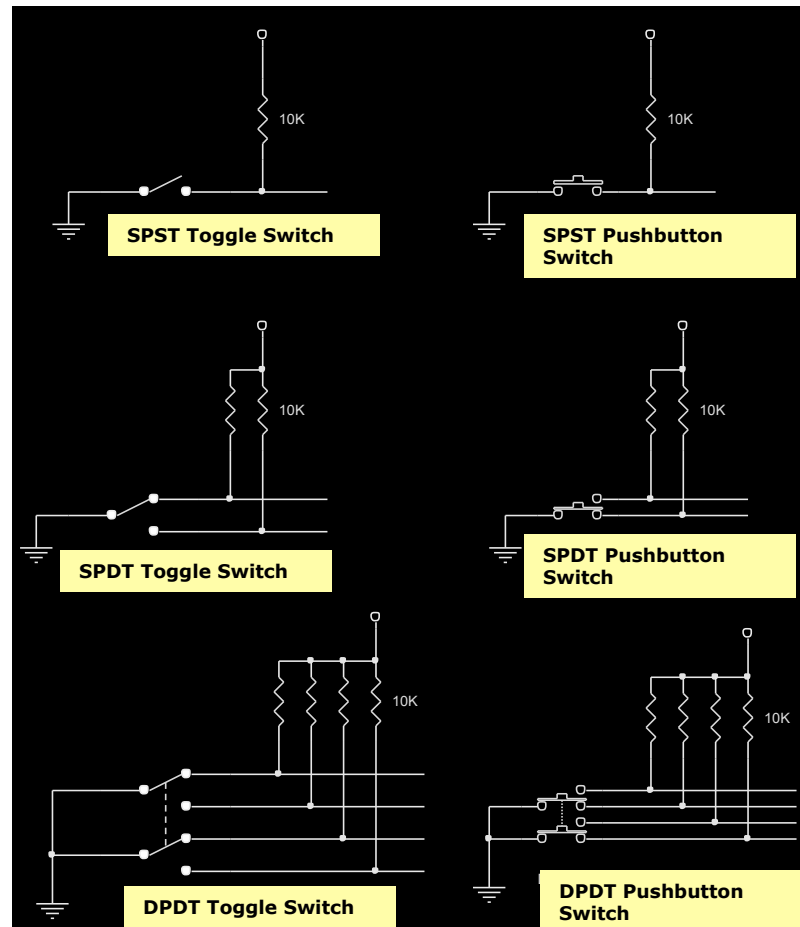

Key Debounce Techniques

□ Hardware technique

- Two circuits, based on the principles of generating a delay and switching the logic level at a certain threshold level.
- Two NAND gates connected back to back, equivalent of a S-R latch. The output of the S-R latch is a pulse without a bounce.
- An integrated circuit (MAX 6816) that bounces the key internally and provides a steady output.


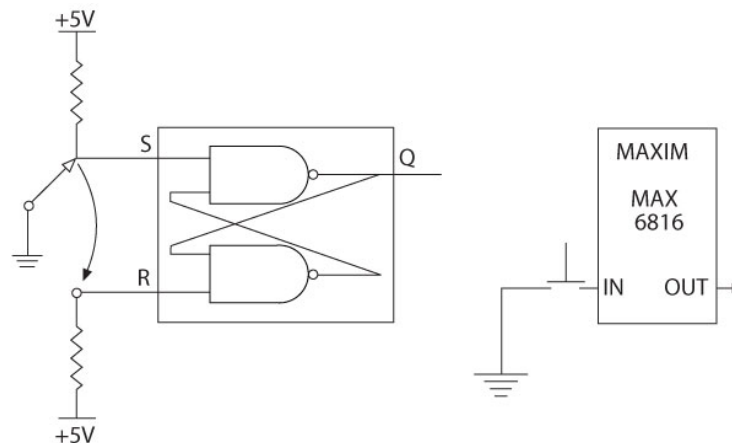


Illustration:

Interfacing Push-Button Keys (1 of 6)

□ Problem statement

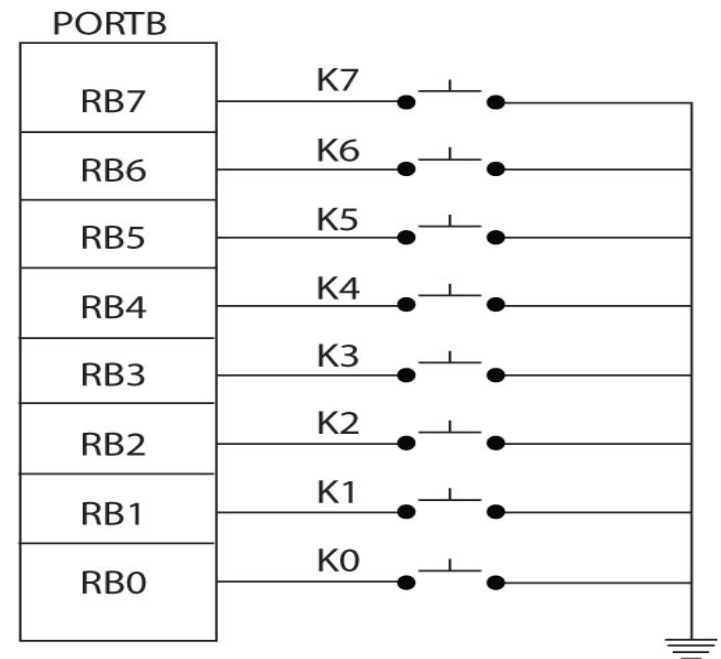- A bank of push-button keys are connected as inputs to PORTB.
- The pull-up resistors are internal to PORTB.
- Write a program to recognize a key pressed, debounce the key, and identify its location in the key bank with numbers from 0 to 7.




Interfacing Push-Button Keys (3 of 6)

□ Hardware

- PORTB should be set up as input port
- Internal pull-up resistors should be enabled


□ Software

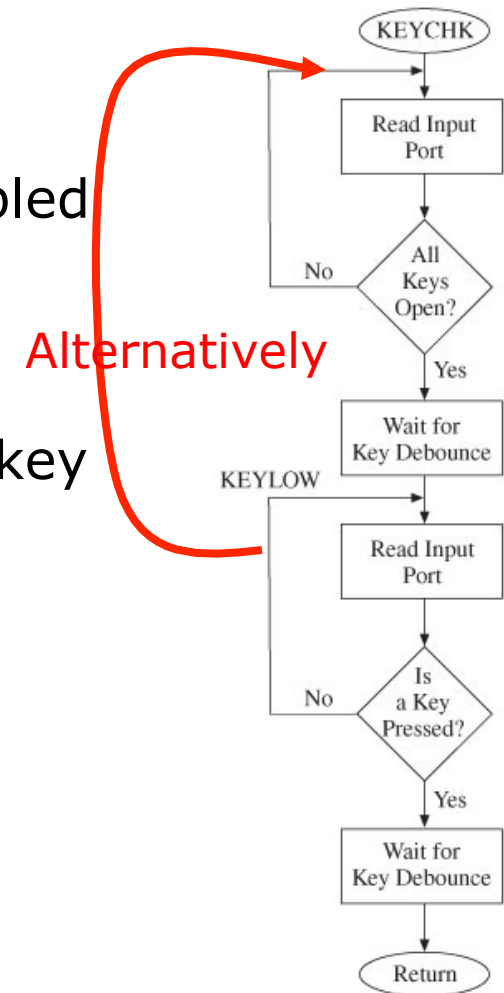- Checking a key closure Debouncing the key
- Encoding the key



Interfacing Push-Button Keys

- Software Debouncing

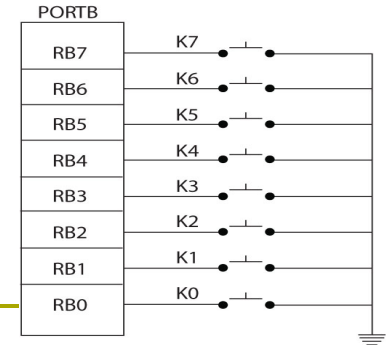

- ❑ Checking a key closure
 - When a key is **open**, the logic level is **one** (assuming pull-ups are enabled) and when it is **closed**, the logic level is **zero**.
 - When all keys are open, the reading will be 0xFF, and when a key is closed, the reading will be less than 0xFF.
 - ❑ Therefore, any reading less than FFH indicates a key closure.
 - ❑ This will be the first read!
- ❑ Debouncing the key
 - Software technique
 - ❑ Wait for 20 ms.
 - ❑ Read the port again.
 - ❑ If the reading is still less than FFH, it indicates that a key is pressed.
- ❑ Encoding the key
 - Key closure can be identified by rotating the reading right and looking for 'No Carry' and counting the rotations

Software Debouncing – Used for Active LOW!

```
□ // >>> Don't forget the #include <delays.h> statement <<<
□ // ***** Switch *****
□ // to use this function, make sure that it is invoked as follows
□ //
□ // Switch( 0x04 ) ← switch on bit 2
□ //
□ // or
□ //
□ // Switch( 0x40 ) ← switch on bit 6
□ //
□ // or
□ //
□ // Switch( 0x03 ) ← switches bits 0 and 1
□ //
□ // ***** CONSTANTS *****
□ #define KEYPORT PORTA // change to match the actual port
□ #define DELAY 15 // change as needed for time delay – 15 msec.
□ void Switch( char bit )
□ {
□     do // wait for release
□     {
□         while ( ( KEYPORT & bit ) != bit );
□         Delay1KTCYx(DELAY);
□     }
□     while( ( KEYPORT & bit ) != bit );
□     do // wait for press
□     {
□         while ( ( KEYPORT & bit ) == bit );
□         Delay1KTCYx(DELAY);
□     }
□     while( ( KEYPORT & bit ) == bit );
□ }
```

Switch(0x22)
0010 0010
Bits 1 or 5 is activated

Software Debouncing – Used for Active LOW! Another Example

```
void main (void)
{
    unsigned char Switch_Count = 0;

    LED_Display = 1;           // initialize

    TRISD = 0b00000000;      // PORTD bits 7:0 are all outputs (0)

    INTCON2bits.RBPU = 0;    // enable PORTB internal pullups
    WPUBbits.WPUB0 = 1;      // enable pull up on RB0
    ANSELH = 0x00;          // AN8-12 are digital inputs (AN12 on RB0)
    TRISBbits.TRISB0 = 1;    // PORTB bit 0 (connected to switch) is input (1)


    while (1)
    {
        LATD = LED_Display;   // output LED_Display value to PORTD LEDs

        LED_Display <<= 1;    // rotate display by 1

        if (LED_Display == 0)
            LED_Display = 1;  // rotated bit out, so set bit 0

        while (Switch_Pin != 1); // wait for switch to be released


        Switch_Count = 5;
        do
        { // monitor switch input for 5 lows in a row to debounce
            if (Switch_Pin == 0)
            { // pressed state detected
                Switch_Count++;
            }
            else
            {
                Switch_Count = 0;
            }
            Delay10TCYx(25); // delay 250 cycles or 1ms.
        } while (Switch_Count < DetectsInARow);
    }
}
```

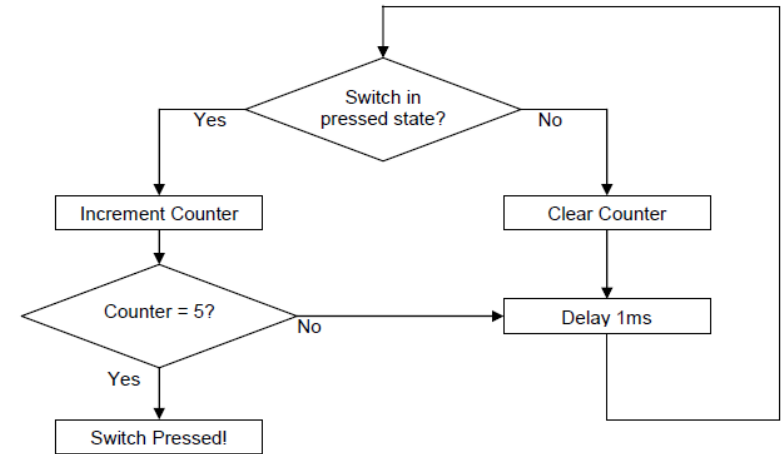


#define Switch_Pin PORTBbits.RB0
The demo board switch is connected to I/O pin RB0, which is normally pulled up to VDD internally. **When the switch is pressed, it pulls RB0 to ground (low state).**

PIC18F46K20 Pin Diagram

44-pin TQFP

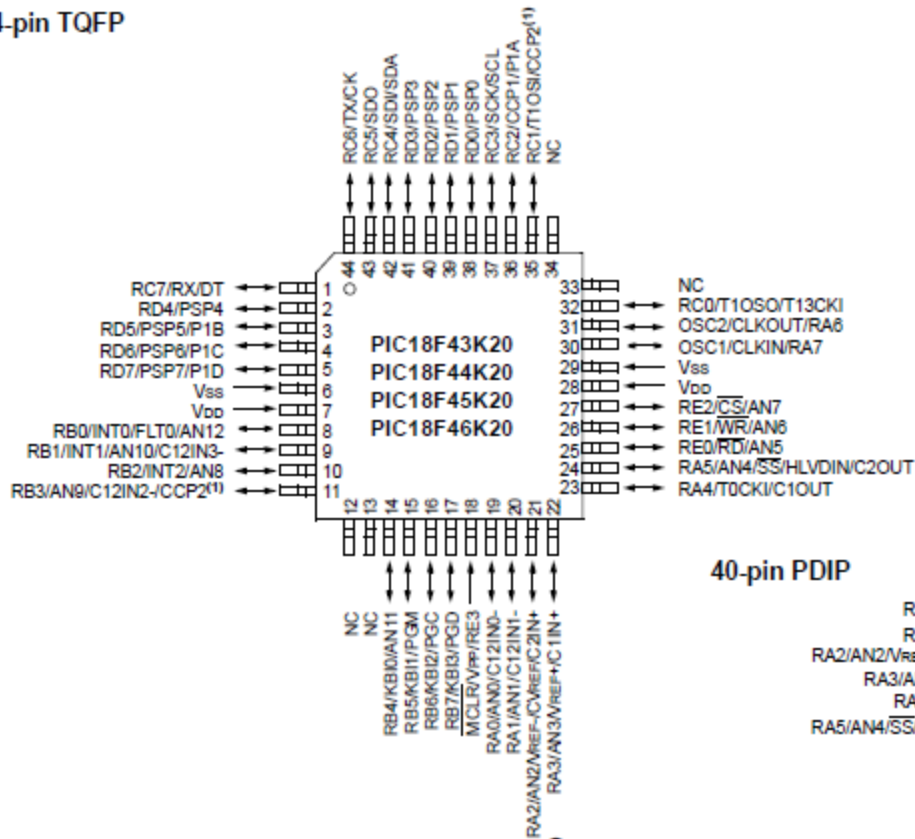

40-pin PDIP

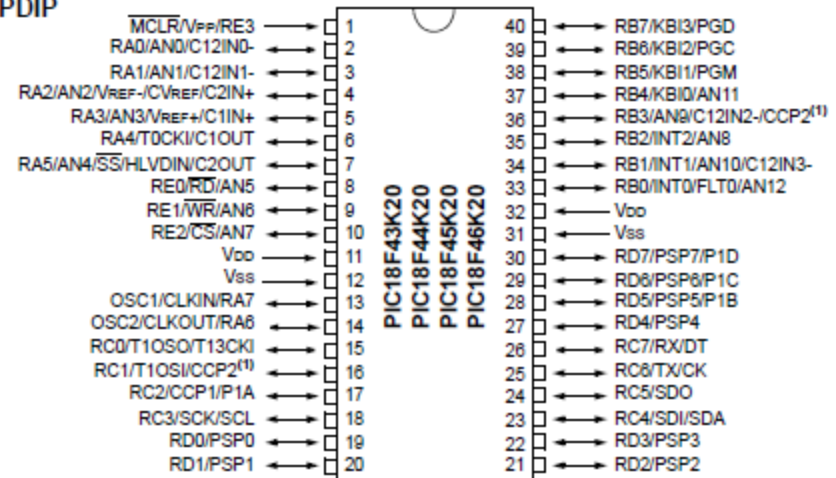

Digital Input Port

```

INTCON2bits.RBPU = 0;           // enable PORTB internal pullups Interrupt Control
WPUBbits.WPUB0 = 1;           // enable pull up on RB0 Weak Pull Up
ANSELH = 0x00;                // AN8-12 are digital inputs (AN12 on RB0) Analog Sel
TRISBbits.TRISB0 = 1;         // PORTB bit 0 (connected to switch) is input (1)
    
```

REGISTER 10-3: ANSELH: ANALOG SELECT REGISTER 2

U-0	U-0	U-0	R/W-1 ⁽¹⁾	R/W-1 ⁽¹⁾	R/W-1 ⁽¹⁾	R/W-1 ⁽¹⁾	R/W-1 ⁽¹⁾	
—	—	—	ANS12	ANS11	ANS10	ANS9	ANS8	
bit 7								bit 0


Legend:			
R = Readable bit	W = Writable bit	U = Unimplemented bit, read as '0'	
-n = Value at POR	'1' = Bit is set	'0' = Bit is cleared	x = Bit is unknown

- bit 7-5 **Unimplemented:** Read as '0'
- bit 4 **ANS12:** RB0 Analog Select Control bit
 - 1 = Digital input buffer of RB0 is disabled
 - 0 = Digital input buffer of RB0 is enabled

Pins are configured as **analog or digital** in the SFRs **ANSEL** and **ANSELH**

PIC18F46K20

40-pin PDIP

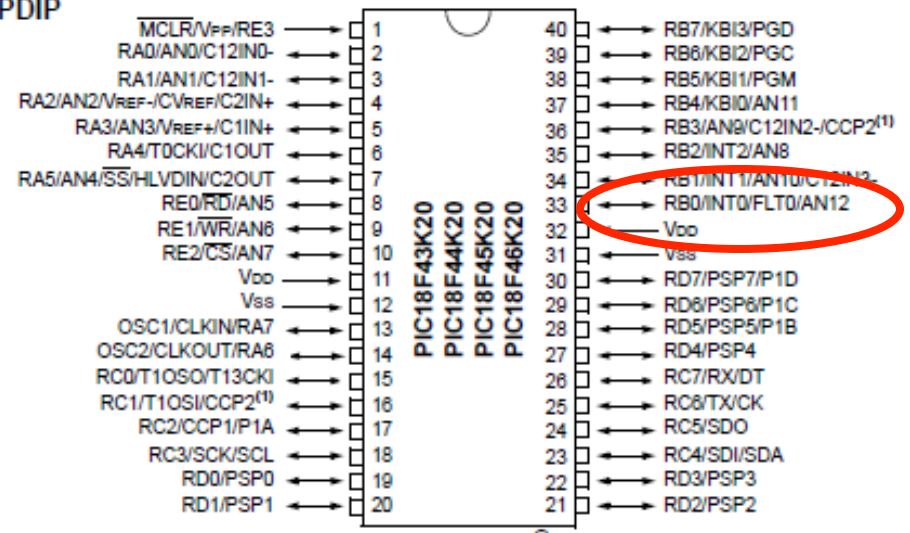


Class Exercise

- Find the following bits in the Data Sheet:
 - <http://ww1.microchip.com/downloads/en/DeviceDoc/41303G.pdf>

```
INTCON2bits.RBPU = 0;           // enable PORTB internal pullups
WPUBbits.WPUB0 = 1;            // enable pull up on RB0
ANSELH = 0x00;                 // AN8-12 are digital inputs (AN12 on RB0)
TRISBbits.TRISB0 = 1;          // PORTB bit 0 (connected to switch) is input (1)
```

Interfacing a Matrix Keyboard

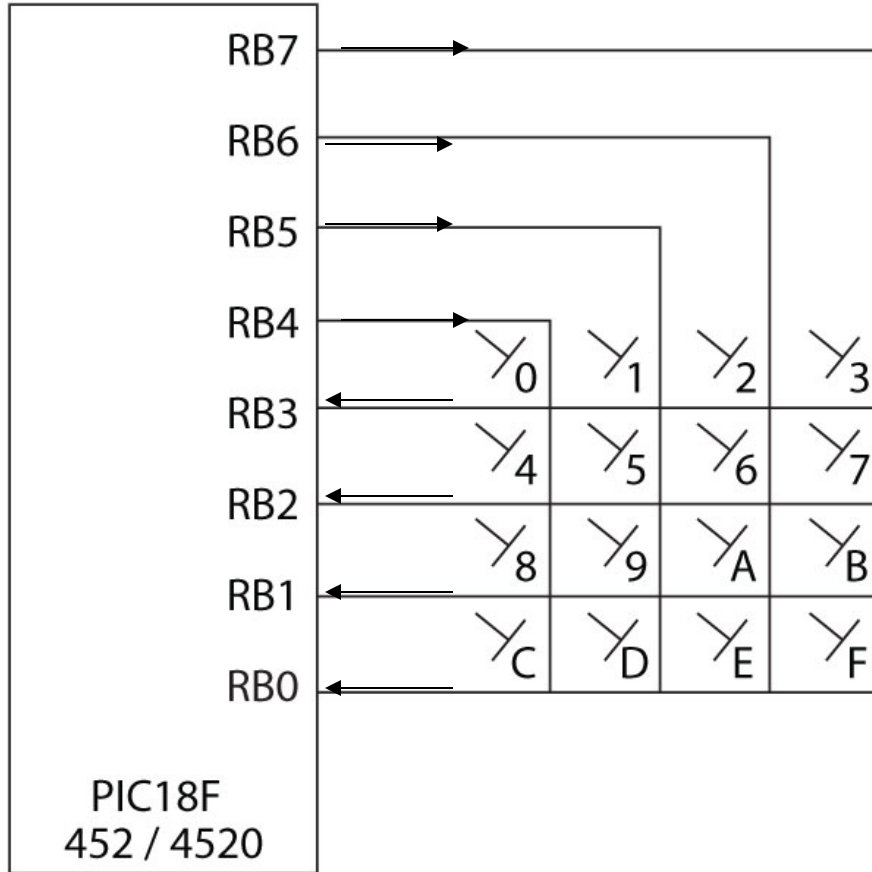


1	2	3
4	5	6
7	8	9
10	0	11

Actual Keyboard

0	4	8
1	5	9
2	6	10
3	7	11

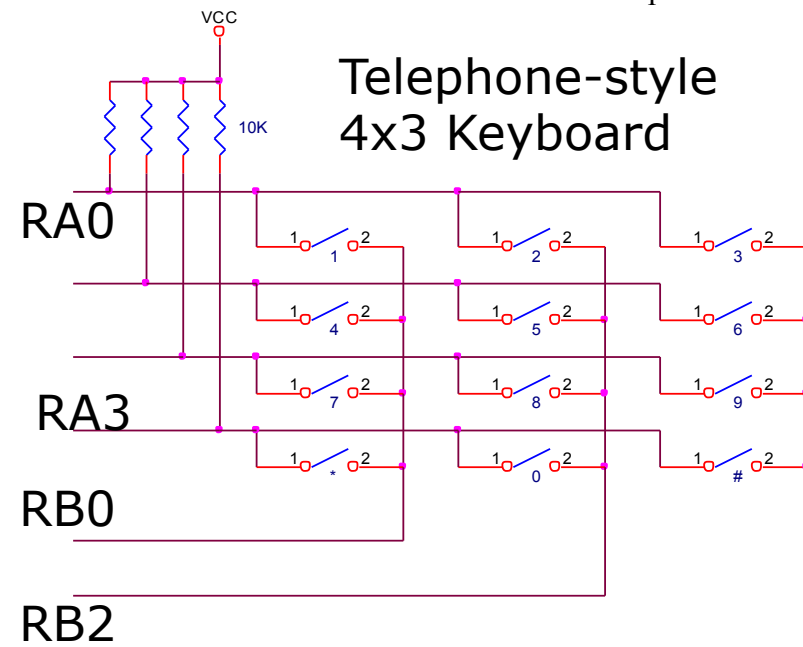Keyboard as seen by software
before the lookup table



Interfacing a Matrix Keyboard

□ Software


- To recognize and encode the key pressed, the program should:
 - Ground all the columns by sending zeros.
 - Check each key in a row for logic zero.
 - Ground one column at a time and check all the rows in that column.
 - Once a key is identified, it is encoded based on its position in the column.

Matrix Keyboard Software

```
□ //
□ // key codes for a telephone style keypad
□ // stored as static constants in the program memory
□ //
□ rom near char lookupKey[] =
□ {
□     1, 4, 7, 10,           // left column
□     2, 5, 8, 0,           // middle column
□     3, 6, 9, 11           // right column
□ };
□ //
□ // uses function Switch
□ //
□ unsigned char Key(void)
□ {
□     #define MASK 0x0f           // set mask
□     #define ROWS 4              // set number of rows
□     char a;
□     char keyCode;
□     PORTB = keyCode = 0;        //clear Port B & keyCode
□     Switch( MASK );            // de-bounce and wait for any key
□     PORTB = 0xFE;              // select a leftmost column
□
□     while ( ( PORTA & MASK ) == MASK ) // while no key is found
□     {
□         PORTB = (PORTB << 1) | 1; // get next column
□         keyCode += ROWS;          // add rows to keycode
□     }
□     for ( a = 1; a != 0; a <= 1)
□     {
□         if ( ( PORTA & a ) == 0 ) // find row
□             break;
□         keyCode++;
□     }
□     return lookupKey[keyCode]; // lookup correct key code
□ }
□ }
```

1	2	3
4	5	6
7	8	9
10	0	11

7-Segment Interface

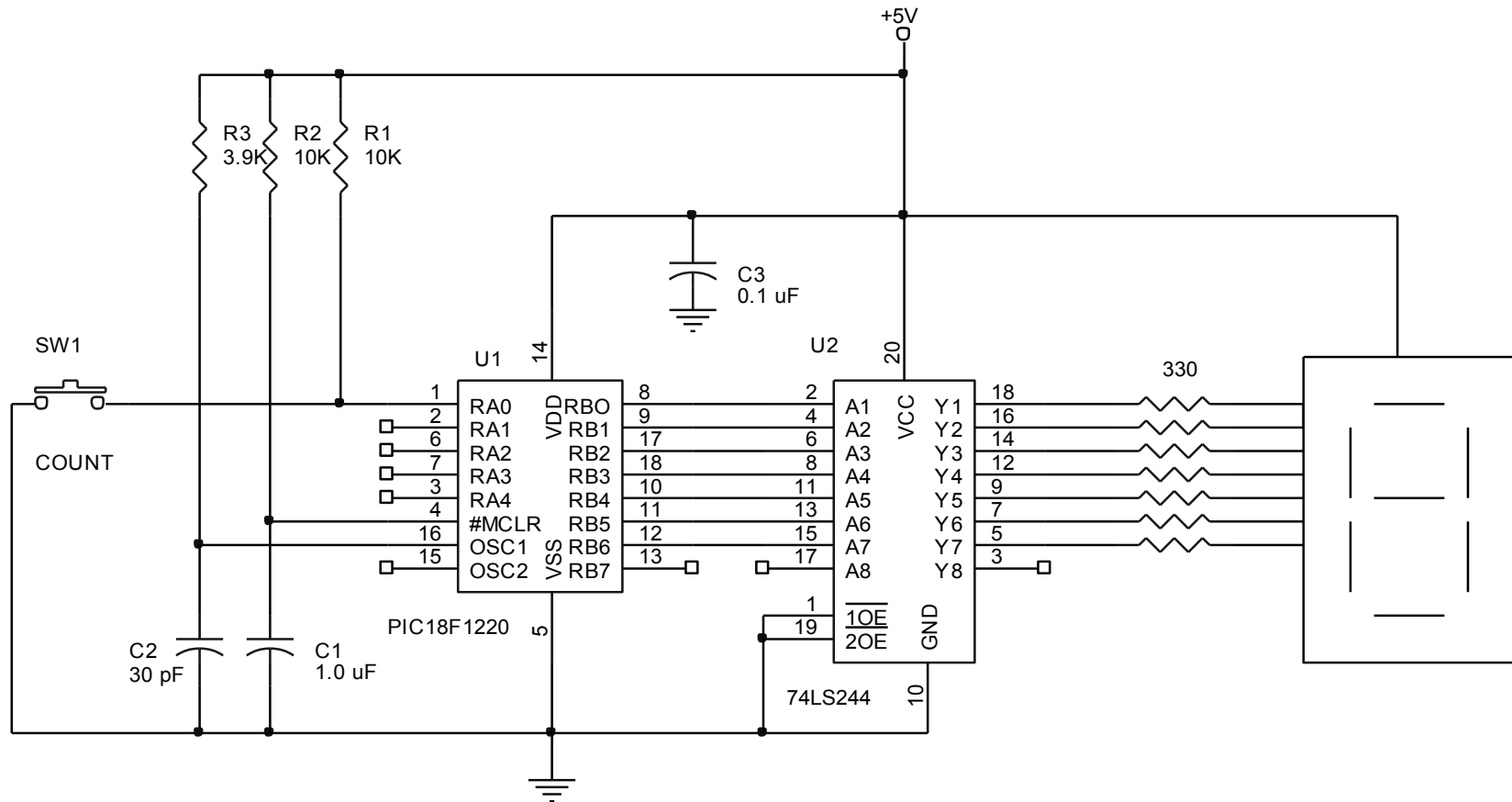

```

□ // ***** program memory data *****
□ rom near char look7[] = // 7-segment lookup table
□ {
□     0x40,           // 0         active low signals
□     0x79,           // 1         x g f e d c b a
□     0x24,           // 2
□     0x30,           // 3
□     0x19,           // 4
□     0x12,           // 5
□     0x02,           // 6
□     0x78,           // 7
□     0x00,           // 8
□     0x10           // 9
□ };
□ // ***** data memory data *****
□ int count;
□ #pragma code
□ // ***** de-bounce functions *****
□ void Switch( char bit )
□ {
□     do               // wait for release
□     {
□         while ( ( PORTA & bit ) != bit );
□         Delay1KTCYx(30);           // 15 ms delay
□     }while( ( PORTA & bit ) != bit );
□     do               // wait for press
□     {
□         while ( ( PORTA & bit ) == bit );
□         Delay1KTCYx(30);
□     }while( ( PORTA & bit ) == bit );
□ }
□ // ***** main program *****
□ void main (void)
□ {
□     ADCON1 = 0x7F;           // Ports A and B are digital
□     TRISA = 1;               // Port A, bit 0 is input
□     TRISB = 0;               // Port B is output
□     count = 0;               // start count at zero
□     while ( 1 )              // main loop
□     {
□         PORTB = look7[count]; // display number
□         Switch( 1 );          // wait for pushbutton
□         count++;
□         if ( count >= 10 )
□             count = 0;
□     }
□ }

```


7-Segment
Control Software with
De-bounce →
Each time the input is
Pressed the number
Shown by the 7-segment
Increments!

Interfacing LCD

(Liquid Crystal Display)

- Problem statement
 - Interface a 2-line x 20 character LCD module with the built-in [HD44780](#) controller to I/O ports of the PIC18 microcontroller
- Multi-LCDs refer to LCDs with different interfaces

LCD

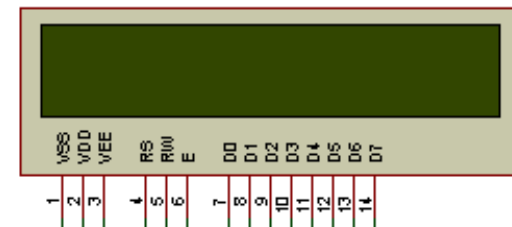

Converting to ASCII


- ❑ The LCD can represent characters in ASCII
- ❑ For example number 0x08 → must be converted to 0x38
- ❑ To perform this:
 - If W=0x08 then ASCII=XORLW 0x30→W=38

Dec	Hx	Oct	Char	Dec	Hx	Oct	Html	Chr	Dec	Hx	Oct	Html	Chr	Dec	Hx	Oct	Html	Chr
0	0	000	NUL (null)	32	20	040	 	Space	64	40	100	@	@	96	60	140	`	`
1	1	001	SOH (start of heading)	33	21	041	!	!	65	41	101	A	A	97	61	141	a	a
2	2	002	STX (start of text)	34	22	042	"	"	66	42	102	B	B	98	62	142	b	b
3	3	003	ETX (end of text)	35	23	043	#	#	67	43	103	C	C	99	63	143	c	c
4	4	004	EOT (end of transmission)	36	24	044	$	\$	68	44	104	D	D	100	64	144	d	d
5	5	005	ENQ (enquiry)	37	25	045	%	%	69	45	105	E	E	101	65	145	e	e
6	6	006	ACK (acknowledge)	38	26	046	&	&	70	46	106	F	F	102	66	146	f	f
7	7	007	BEL (bell)	39	27	047	'	'	71	47	107	G	G	103	67	147	g	g
8	8	010	BS (backspace)	40	28	050	((72	48	110	H	H	104	68	150	h	h
9	9	011	TAB (horizontal tab)	41	29	051))	73	49	111	I	I	105	69	151	i	i
10	A	012	LF (NL line feed, new line)	42	2A	052	*	*	74	4A	112	J	J	106	6A	152	j	j
11	B	013	VT (vertical tab)	43	2B	053	+	+	75	4B	113	K	K	107	6B	153	k	k
12	C	014	FF (NP form feed, new page)	44	2C	054	,	,	76	4C	114	L	L	108	6C	154	l	l
13	D	015	CR (carriage return)	45	2D	055	-	-	77	4D	115	M	M	109	6D	155	m	m
14	E	016	SO (shift out)	46	2E	056	.	.	78	4E	116	N	N	110	6E	156	n	n
15	F	017	SI (shift in)	47	2F	057	/	/	79	4F	117	O	O	111	6F	157	o	o
16	10	020	DLE (data link escape)	48	30	060	0	0	80	50	120	P	P	112	70	160	p	p
17	11	021	DC1 (device control 1)	49	31	061	1	1	81	51	121	Q	Q	113	71	161	q	q
18	12	022	DC2 (device control 2)	50	32	062	2	2	82	52	122	R	R	114	72	162	r	r
19	13	023	DC3 (device control 3)	51	33	063	3	3	83	53	123	S	S	115	73	163	s	s
20	14	024	DC4 (device control 4)	52	34	064	4	4	84	54	124	T	T	116	74	164	t	t
21	15	025	NAK (negative acknowledge)	53	35	065	5	5	85	55	125	U	U	117	75	165	u	u
22	16	026	SYN (synchronous idle)	54	36	066	6	6	86	56	126	V	V	118	76	166	v	v
23	17	027	ETB (end of trans. block)	55	37	067	7	7	87	57	127	W	W	119	77	167	w	w
24	18	030	CAN (cancel)	56	38	070	8	8	88	58	130	X	X	120	78	170	x	x
25	19	031	EM (end of medium)	57	39	071	9	9	89	59	131	Y	Y	121	79	171	y	y
26	1A	032	SUB (substitute)	58	3A	072	:	:	90	5A	132	Z	Z	122	7A	172	z	z
27	1B	033	ESC (escape)	59	3B	073	;	;	91	5B	133	[[123	7B	173	{	{
28	1C	034	FS (file separator)	60	3C	074	<	<	92	5C	134	\	\	124	7C	174	|	
29	1D	035	GS (group separator)	61	3D	075	=	=	93	5D	135]]	125	7D	175	}	}
30	1E	036	RS (record separator)	62	3E	076	>	>	94	5E	136	^	^	126	7E	176	~	~
31	1F	037	US (unit separator)	63	3F	077	?	?	95	5F	137	_	_	127	7F	177		DEL


Interfacing LCD

Hardware

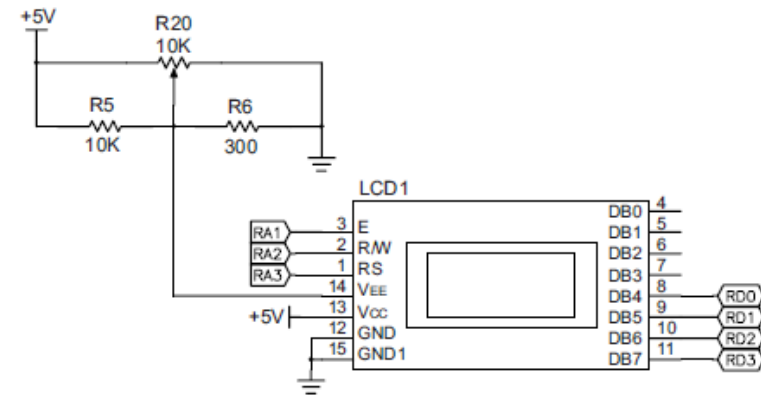- 20 x 2-line LCD displays (two lines with 20 characters per line)
- LCD has a display Data RAM (registers) that stores data in 8-bit character code.
- Each register in **Data RAM** has its own address that corresponds to its position on the line.
 - The **address range** for Line 1 is 00 to 13H and Line 2 is 40H to 53H.



PICDEMO

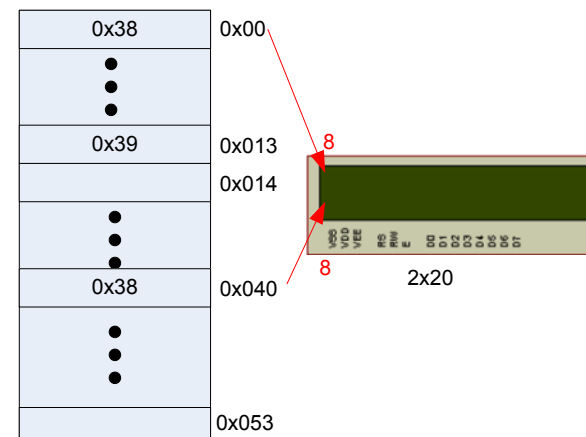

Interfacing LCD



□ Driver HD77480

■ Three control signals:

- RS - Register Select (RA3)
- R/W - Read/Write (RA2)
- E - Enable (RA1)

■ Three power connections

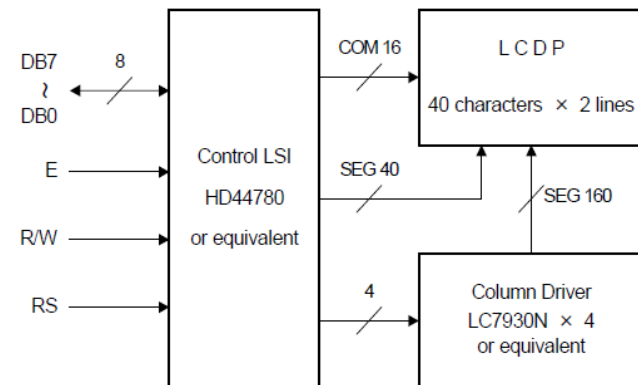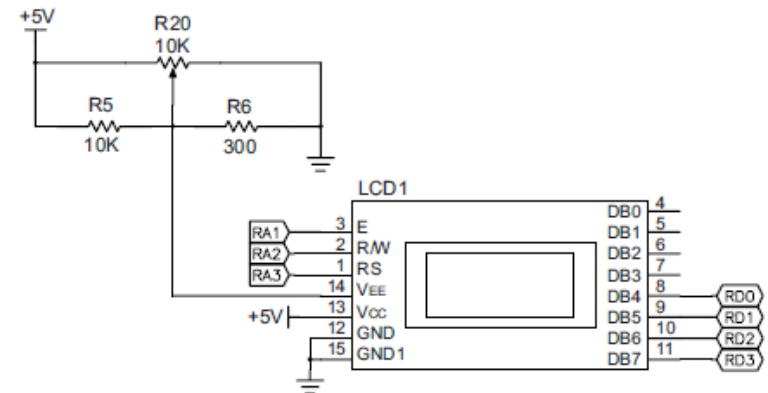- Power, ground, and the variable register to control the brightness



Interfacing LCD

- ❑ Can be interfaced either in the 8-bit mode or the 4-bit mode
 - In the 8-bit mode, all eight data lines are connected for data transfer
 - In the 4-bit mode, only four data lines (DB7-DB4 or DB3-DB0) are connected and two transfers per character (or instruction) are needed
- ❑ Driver (HD77480) has two 8-bit internal registers
 - Instruction Register (IR) to write instructions to set up LCD
 - Data Register (DR) to write data (ASCII characters)

IR REGISTER

DR REGISTER

Command and Instruction set for LCD type HD44780

Command	Code										Description	Execution Time
	RS	R/W	DB7	DB6	DB5	DB4	DB3	DB2	DB1	DB0		
Clear Display	0	0	0	0	0	0	0	0	0	1	Clears the display and returns the cursor to the home position (address 0).	82µs-1.64ms
Return Home	0	0	0	0	0	0	0	0	1	*	Returns the cursor to the home position (address 0). Also returns a shifted display to the home position. DD RAM contents remain unchanged.	40µs-1.64ms
Entry Mode Set	0	0	0	0	0	0	0	1	I/D	S	Sets the cursor move direction and enables/disables the display.	40µs
Display ON/OFF Control	0	0	0	0	0	0	1	D	C	B	Turns the display ON/OFF (D), or the cursor ON/OFF (C), and blink of the character at the cursor position (B).	40µs
Cursor & Display Shift	0	0	0	0	0	1	S/C	R/L	*	*	Moves the cursor and shifts the display without changing the DD RAM contents.	40µs
Function Set	0	0	0	0	1	DL	N\$	F	*	#	Sets the data width (DL), the number of lines in the display (L), and the character font (F).	40µs

Set CG RAM Address	0	0	0	1	A _{CG}		Sets the CG RAM address. CG RAM data can be read or altered after making this setting.	40µs
Set DD RAM Address	0	0	1	A _{DD}		Sets the DD RAM address. Data may be written or read after making this setting.	40µs	
Read Busy Flag & Address	0	1	BF	AC		Reads the BUSY flag (BF) indicating that an internal operation is being performed and reads the address counter contents.	1µs	
Write Data to CG or DD RAM	1	0	Write Data		Writes data into DD RAM or CG RAM.		46µs	
Read Data from CG or DD RAM	1	1	Read Data		Reads data from DD RAM or CG RAM.		46µs	
I/D = 1: Increment I/D = 0: Decrement S = 1: Accompanies display shift. S/C = 1: Display shift S/C = 0: cursor move R/L = 1: Shift to the right. R/L = 0: Shift to the left. DL = 1: 8 bits DL = 0: 4 bits N = 1: 2 lines N = 0: 1 line F = 1: 5x10 dots F = 0: 5 x 7 dots BF = 1: Busy BF = 0: Can accept data # Set to 1 on 24x4 modules \$ With KS0072 is Address Mode.							DD RAM: Display data RAM CG RAM: Character generator RAM A _{CG} : CG RAM Address A _{DD} : DD RAM Address Corresponds to cursor address. AC: Address counter Used for both DD and CG RAM address.	Execution times are typical. If transfers are timed by software and the busy flag is not used, add 10% to the above times.

Interfacing LCD

□ LCD Operation


- When the MPU writes an instruction to IR or data to DR, the controller:
 - Sets the data line DB7 high as a flag indicating that the controller is busy completing the operation
 - Sets the data line DB7 low after the completion of the operation
- The MPU should always check whether DB7 is low before sending an instruction or a data byte
- After the power up, DB7 cannot be checked for the first two initialization instructions.

Interfacing LCD

- ❑ Writing to or reading from LCD
- ❑ The MPU:
 - ❑ Asserts **RS** low to select IR
 - ❑ Reads from LCD by asserting the R/W signal high
 - ❑ Asserts the E signal high and then low (toggles) to latch a data byte or an instruction

 - ❑ Asserts **RS** high to select DR
 - ❑ Writes into LCD by asserting the R/W signal low
 - ❑ Asserts the E signal high and then low (toggles) to latch a data byte or an instruction


HD44780 Bus Timing

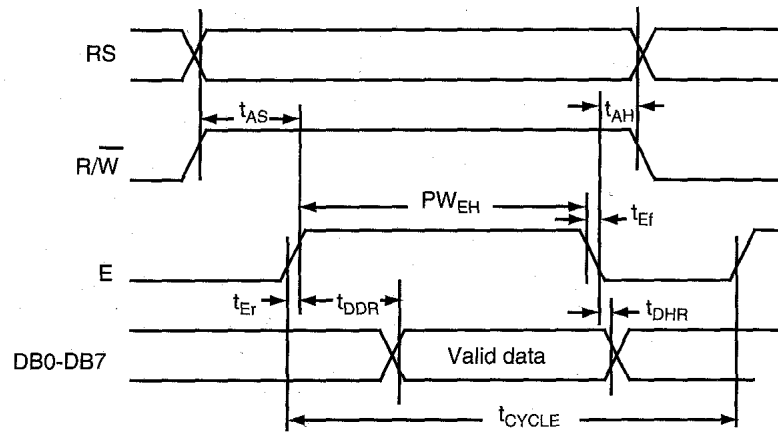

Read timing diagram

- Asserts **RS** high to select DR
- Writes into LCD by asserting the R/W signal low
- Asserts the E signal high and then low (toggles) to latch a data byte or an instruction

Symbol	Meaning	Min	Typ	Max.	Unit
t_{CYCLE}	Enable cycle time	1000	-	-	ns
PW_{EH}	Enable pulse width (high level)	450	-	-	ns
t_{Er}, t_{Ef}	Enable rise and decay time	-	-	25	ns
t_{AS}	Address setup time, RS, R/W, E	60	-	-	ns
t_{DDR}	Data delay time	-	-	360	ns
t_{DSW}	Data setup time	195	-	-	ns
t_H	Data hold time (write)	10	-	-	ns
t_{DHR}	Data hold time (read)	5	-	-	ns
t_{AH}	Address hold time	20	-	-	ns

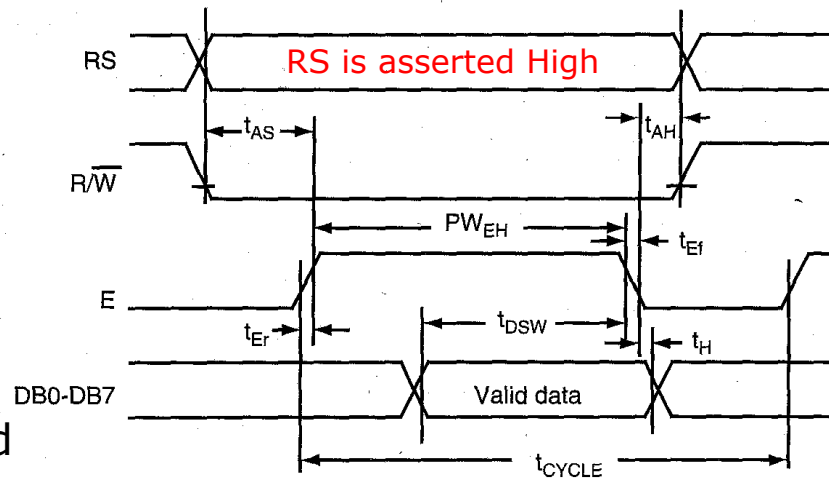

Write timing diagram

Interfacing LCD (Write)

□ Software

- To write into the LCD, the program should:
 - Send the initial instructions (commands) before it can check DB7 to set up the LCD in the 4-bit or the 8-bit mode.
 - Check DB7 and continue to check until it goes low.
 - Write instructions to IR to set up the LCD parameters such as the number of display lines and cursor status.
 - Write data to display a message.

Resetting LCD

- ❑ In 4-bit mode the data is sent in nibbles
 - First we send the higher nibble and then the lower nibble.
- ❑ To enable the 4-bit mode of LCD, we need to follow special sequence of initialization that tells the LCD controller that user has selected 4-bit mode of operation:
 - Wait for about 20mS
 - Send the first init value (0x30)
 - Wait for about 10mS
 - Send second init value (0x30)
 - Wait for about 1mS
 - Send third init value (0x30)
 - Wait for 1mS
 - Select bus width (0x30 - for 8-bit and 0x20 for 4-bit)
 - Wait for 1mS



<http://www.youtube.com/watch?v=tTym5apZwCE>

<http://video.google.com/videoplay?docid=7437543675646211278#>

Organic LED

- ❑ Organic light-emitting diodes - OLEDs - emit light when a current flows through them
- ❑ Unlike conventional LEDs, OLEDs are made from layers of plastic and other organic (**carbon-based**) materials
 - Very flexible!
- ❑ Applications: displays in MP3 players and phones
- ❑ Advantages:
 - cheaper than the techniques required to make conventional LEDs.
 - inherently thin
 - can be made on flexible plastic substrates
 - all colors, and multi-colors, are possible
- ❑ Disadvantages
 - incredibly sensitive to moisture which leads to short life - glass blocks all moisture, so displays made on a glass substrate and covered by a second glass sheet can have a long life, particularly if the edges are hermetically sealed

Organic LED

- OLEDs are generally made of several layers
- A typical stack (variations are possible):
 - Anode
 - Electron donor
 - Electron transport
 - Emitter
 - Hole transport
 - Hole donor.
 - Cathode

References

- <http://home.iae.nl/users/pouweha/lcd/lcd0.shtml>
- Huang