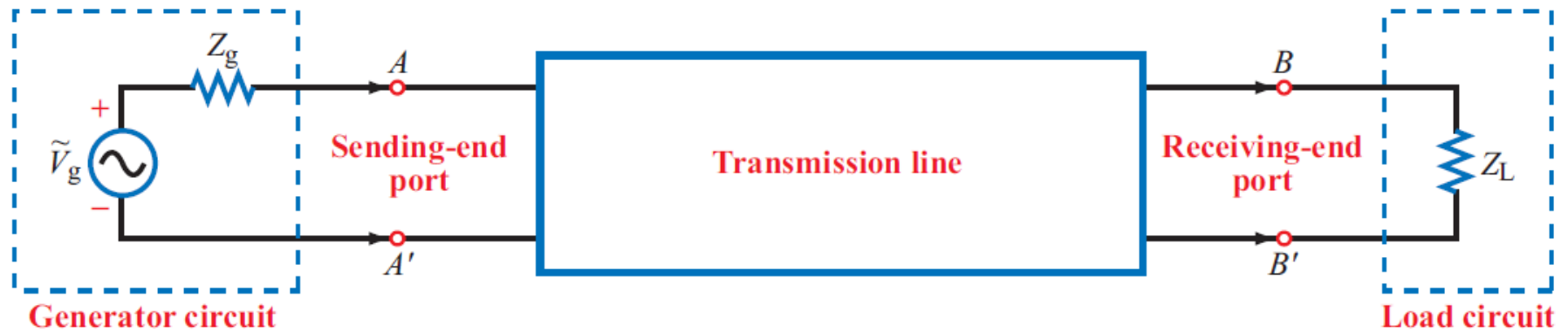


## 2. TRANSMISSION LINES

# Transmission Lines

A transmission line connects a generator to a load



## Transmission lines include:

- Two parallel wires
- Coaxial cable
- Microstrip line
- Optical fiber
- Waveguide
- etc.

# Transmission Line Effects


$$V_{AA'} = V_g(t) = V_0 \cos \omega t \quad (\text{V})$$

$$\begin{aligned} V_{BB'}(t) &= V_{AA'}(t - l/c) \quad \text{Delayed by } l/c \\ &= V_0 \cos [\omega(t - l/c)] \\ &= V_0 \cos(\omega t - \phi_0), \end{aligned}$$

At  $t = 0$ , and for  $f = 1 \text{ kHz}$ , if:

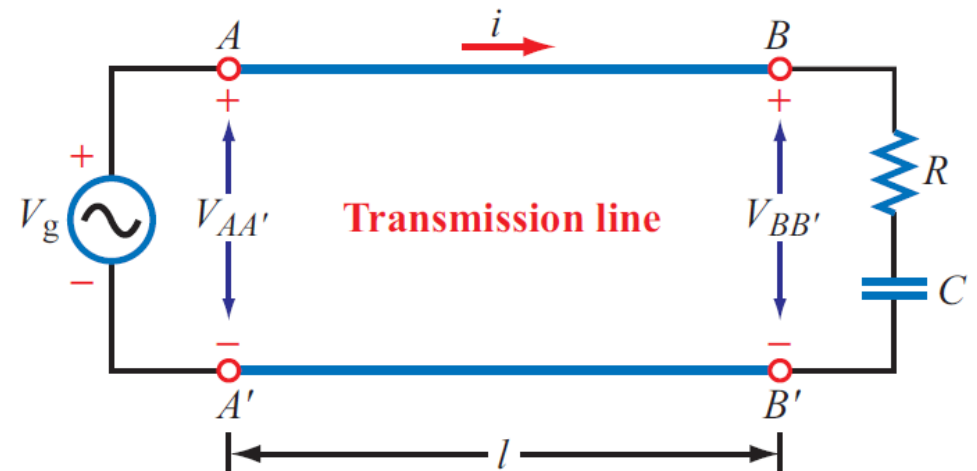(1)  $l = 5 \text{ cm}$ :

$$V_{BB'} = V_0 \cos(2\pi f l/c) = 0.9999999999998 V_0$$



(2) But if  $l = 20 \text{ km}$ :


$$V_{BB'} = 0.91 V_0$$

# Dispersion and Attenuation



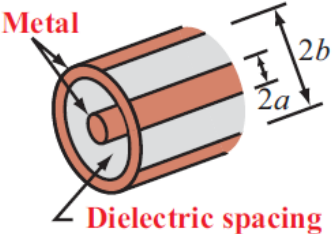
# Types of Transmission Modes


**TEM (Transverse Electromagnetic):** Electric and magnetic fields are orthogonal to one another, and both are orthogonal to direction of propagation




(a) Coaxial line

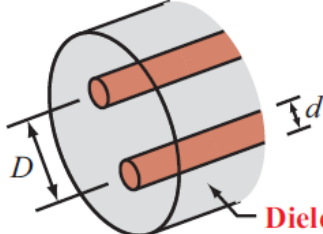


(b) Two-wire line

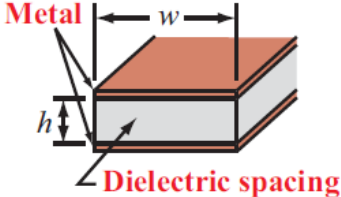


(c) Parallel-plate line

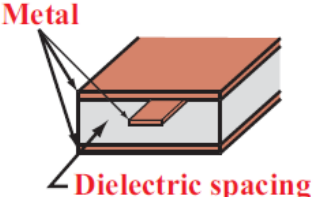

(d) Strip line

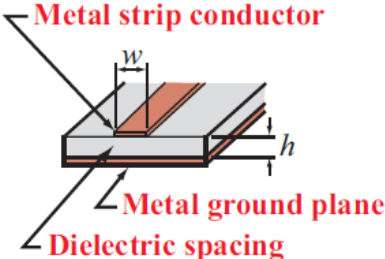


(e) Microstrip line

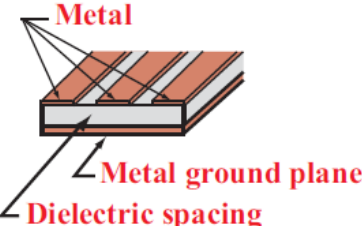


(f) Coplanar waveguide

**TEM Transmission Lines**

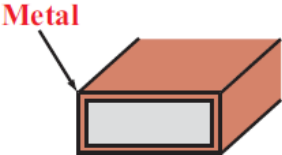


(g) Rectangular waveguide

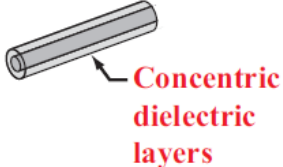


(h) Optical fiber

**Higher-Order Transmission Lines**

# Example of TEM Mode

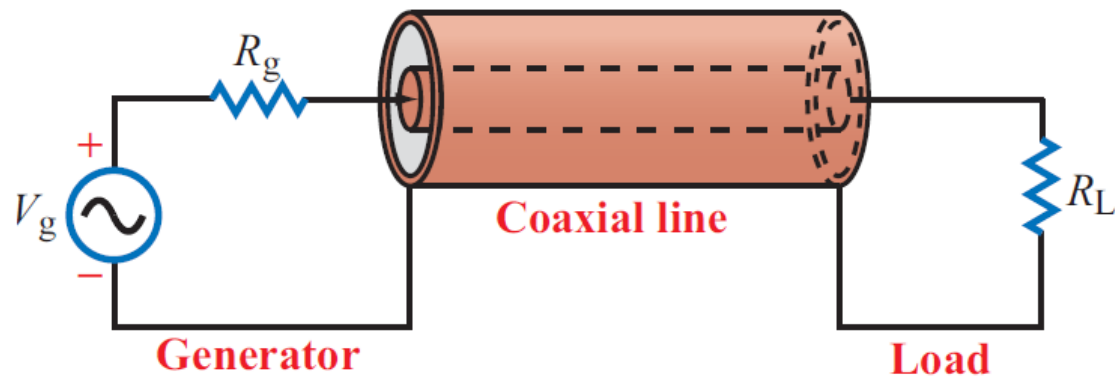

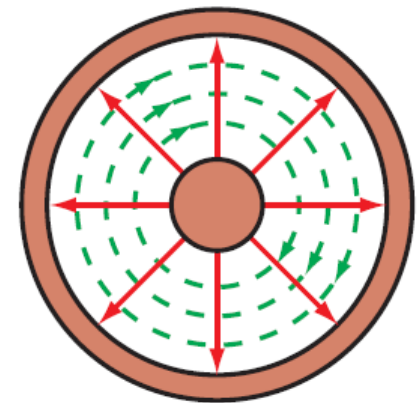--- Magnetic field lines  
— Electric field lines



Cross section

**Electric Field  $E$**  is radial  
**Magnetic Field  $H$**  is azimuthal  
Propagation is into the page


# Transmission Line Model



(a) Parallel-wire representation



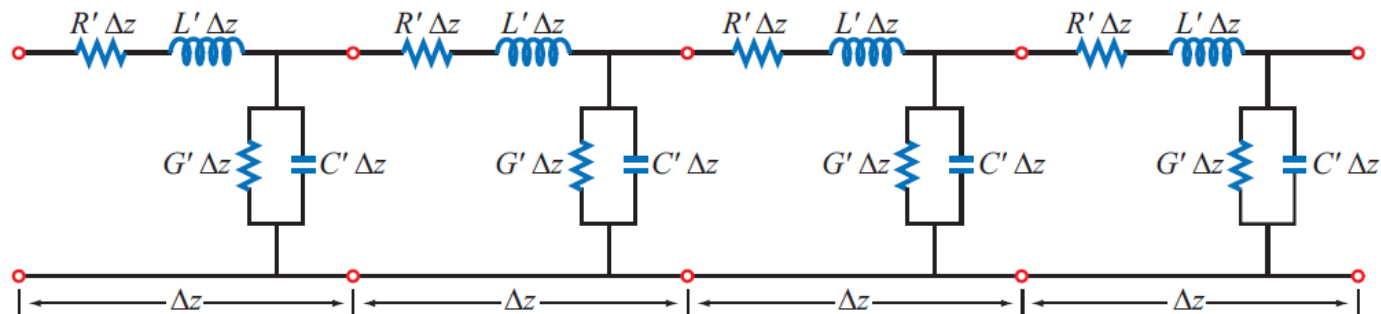(b) Differential sections each  $\Delta z$  long






(c) Each section is represented by an equivalent circuit

- $R'$ : The combined *resistance* of both conductors per unit length, in  $\Omega/\text{m}$ ,
- $L'$ : The combined *inductance* of both conductors per unit length, in  $\text{H}/\text{m}$ ,
- $G'$ : The *conductance* of the insulation medium between the two conductors per unit length, in  $\text{S}/\text{m}$ , and
- $C'$ : The *capacitance* of the two conductors per unit length, in  $\text{F}/\text{m}$ .

**Table 2-1:** Transmission-line parameters  $R'$ ,  $L'$ ,  $G'$ , and  $C'$  for three types of lines.

Parameter	Coaxial	Two-Wire	Parallel-Plate	Unit
$R'$	$\frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$	$\frac{2R_s}{\pi d}$	$\frac{2R_s}{w}$	$\Omega/\text{m}$
$L'$	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right]$	$\frac{\mu h}{w}$	$\text{H}/\text{m}$
$G'$	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\pi\sigma}{\ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\sigma w}{h}$	$\text{S}/\text{m}$
$C'$	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\epsilon w}{h}$	$\text{F}/\text{m}$

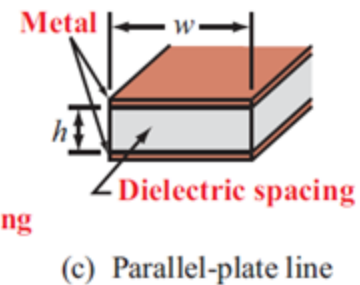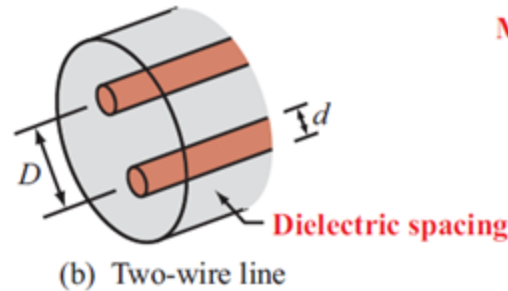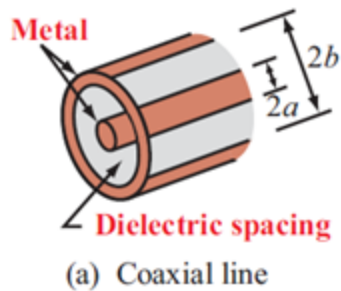Notes: (1) Refer to Fig. 2-4 for definitions of dimensions. (2)  $\mu$ ,  $\epsilon$ , and  $\sigma$  pertain to the insulating material between the conductors. (3)  $R_s = \sqrt{\pi f \mu_c / \sigma_c}$ . (4)  $\mu_c$  and  $\sigma_c$  pertain to the conductors. (5) If  $(D/d)^2 \gg 1$ , then  $\ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right] \simeq \ln(2D/d)$ .





# Applied Electromagnetics 6e

Textbook CD\*



## GETTING STARTED

- » [Welcome](#)
- » [Using this CD](#)
- » [Terms](#)
- » [Feedback](#)

## STUDENT RESOURCES

- » [Exercise Solutions](#)
- » [CD Modules](#)
- » [Solved Problems](#)
- » [Technology Briefs](#)
- » [Frequency Allocation Chart](#)

## WELCOME

Welcome to the CD-ROM companion of the sixth edition of *Applied Electromagnetics*, developed to serve the student as an interactive self-study supplement to the text.

The navigation is highly flexible; the user may go through the material in the order outlined in the table of contents or may proceed directly to any exercise, module, technology brief or solved problem of interest.

We hope you find this CD-ROM helpful and we welcome your [feedback](#) and suggestions.

Fawwaz Ulaby  
Eric Michielssen  
Umberto Ravaioli



## Module 2.2

## Coaxial Cable

Select: Impedance vs. Radius b

$$\sigma = 0.0 \text{ S/m}$$

$$\epsilon_r = 2.3$$

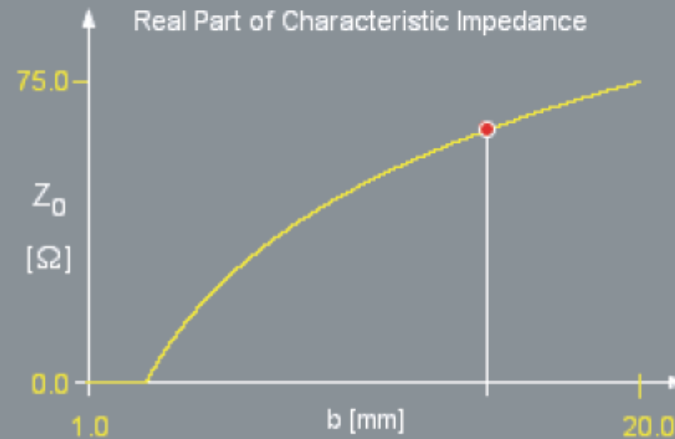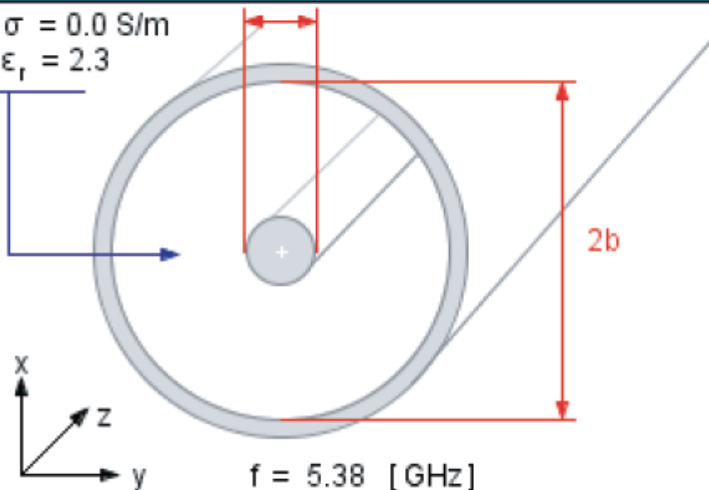

### Input

Inner radius a = 3.034 [mm]

Range

Shield radius b = 14.7579 [mm]

Range

Frequency f = 5.38E9 [Hz]

Range

$\epsilon_r$

2.3

$\sigma$  [S/m]

0.0

$\sigma_c$  [S/m]

5.797E7

Update

### Output

#### Structure Data

a = 3.034 [mm]

b / a = 4.86417

b = 14.7579 [mm]

$Z_0 = 62.584306 - j 0.0035419$  [ $\Omega$ ]

$C' = 80.775048$  [pF/m]

$L' = 316.37933$  [nH/m]

$R' = 1.210519$  [ $\Omega$ /m]

$G' = 0.0$  [S/m]


$\lambda_0 = 5.5762$  [cm] in vacuum

$\lambda = 3.6768$  [cm] in guide

$\alpha = 0.009671$  [Np/m]

$\beta = 170.88534$  [rad/m]

# Transmission-Line Equations

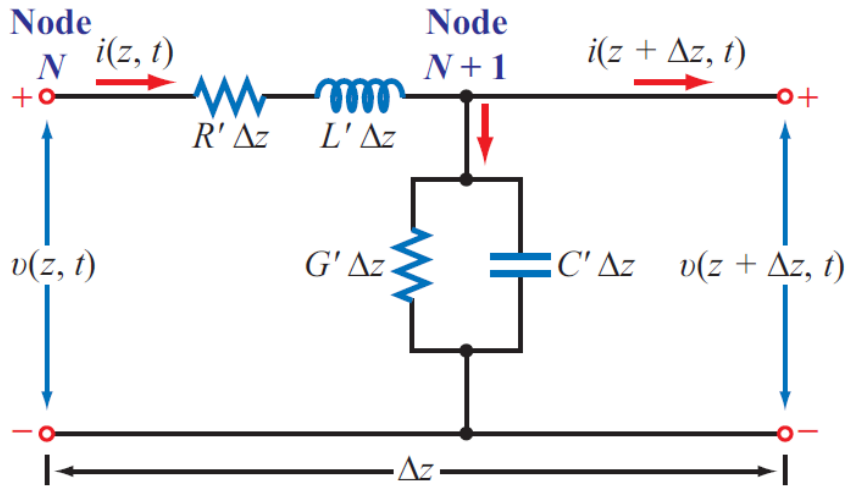

Remember:

**Kirchhoff Voltage Law:**

$$V_{in} - V_{out} - V_{R'} - V_{L'} = 0$$

**Kirchhoff Current Law:**

$$I_{in} - I_{out} - I_{C'} - I_{G'} = 0$$

**Note:**

$$V_L = L \cdot di/dt$$

$$I_C = C \cdot dv/dt$$

$$Ae^{j\theta} = A\cos(\theta) + Aj\sin(\theta)$$

$$\cos(\theta) = A \operatorname{Re}[Ae^{j\theta}]$$


$$\sin(\theta) = A \operatorname{Im}[Ae^{j\theta}]$$

$$E(z) = |E(z)| e^{j\theta_z}$$

$$|e^{j\theta}| = 1$$

$$C = A + jB \rightarrow \theta = \tan^{-1} \frac{B}{A}; |C| = \sqrt{A^2 + B^2}$$

# Transmission-Line Equations

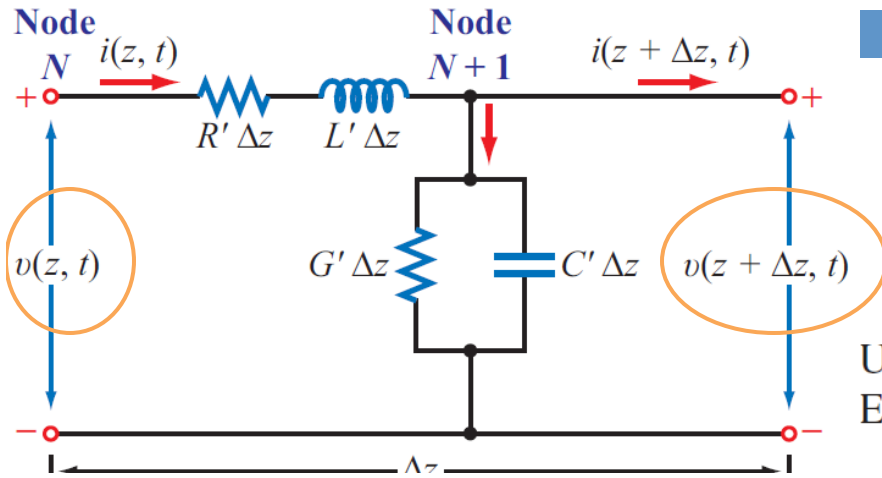

$$i(z, t) - G' \Delta z v(z + \Delta z, t) - C' \Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0. \quad (2.15)$$

Upon dividing all terms by  $\Delta z$  and taking the limit  $\Delta z \rightarrow 0$ , Eq. (2.15) becomes a second-order differential equation:

$$v(z, t) - R' \Delta z i(z, t) - L' \Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0.$$

$$-\frac{\partial i(z, t)}{\partial z} = G' v(z, t) + C' \frac{\partial v(z, t)}{\partial t}. \quad (2.16)$$

Upon dividing all terms by  $\Delta z$  and rearranging them, we obtain

$$-\left[ \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} \right] = R' i(z, t) + L' \frac{\partial i(z, t)}{\partial t}. \quad (2.13)$$

In the limit as  $\Delta z \rightarrow 0$ , Eq. (2.13) becomes a differential equation:

$$-\frac{\partial v(z, t)}{\partial z} = R' i(z, t) + L' \frac{\partial i(z, t)}{\partial t}. \quad (2.14)$$

**ac signals: use phasors**

$$v(z, t) = \Re[\tilde{V}(z) e^{j\omega t}],$$

$$i(z, t) = \Re[\tilde{I}(z) e^{j\omega t}],$$

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$

$$-\frac{d\tilde{I}(z)}{dz} = (G' + j\omega C') \tilde{V}(z).$$


Transmission Line Equation in Phasor Form

# Derivation of Wave Equations

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$

$$-\frac{d\tilde{I}(z)}{dz} = (G' + j\omega C') \tilde{V}(z).$$

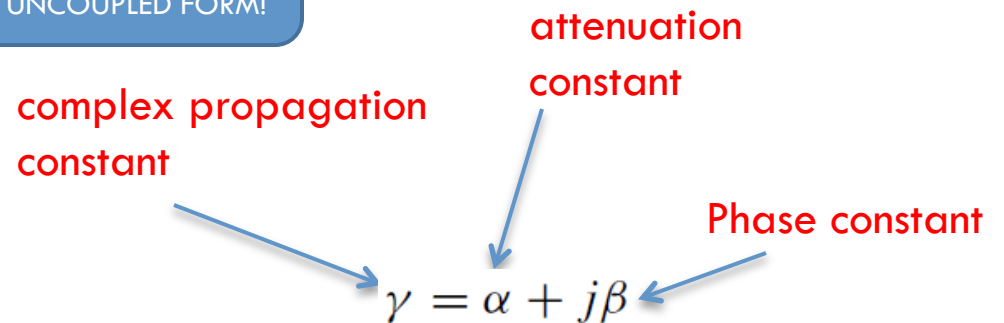Transmission Line Equation  
First Order Coupled Equations!  
WE WANT UNCOUPLED FORM!



Combining the two equations leads to:

$$\frac{d^2\tilde{V}(z)}{dz^2} - (R' + j\omega L')(G' + j\omega C') \tilde{V}(z) = 0,$$

$$\frac{d^2\tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0, \quad (2.21)$$

Second-order differential equation

Wave Equations for Transmission Line

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}. \quad (2.22)$$

Impedance and Shunt Admittance of the line

$$\alpha = \Re(\gamma)$$

$$= \Re\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right) \quad (\text{Np/m}), \quad (2.25a)$$

$$\beta = \Im(\gamma)$$

$$= \Im\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right) \quad (\text{rad/m}). \quad (2.25b)$$

Pay Attention to UNITS!

# Solution of Wave Equations (cont.)

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0, \quad (2.21)$$

$$\frac{d^2 \tilde{I}(z)}{dz^2} - \gamma^2 \tilde{I}(z) = 0. \quad (2.23)$$

Proposed form of solution:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$


Characteristic Impedance of the Line (ohm)

$$\frac{V_0^+}{I_0^+} = Z_0 = \frac{-V_0^-}{I_0^-},$$


Using:  $-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$

It follows that:  $\tilde{I}(z) = \frac{\gamma}{R' + j\omega L'} [V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z}]$

So What does V+ and V- Represent?

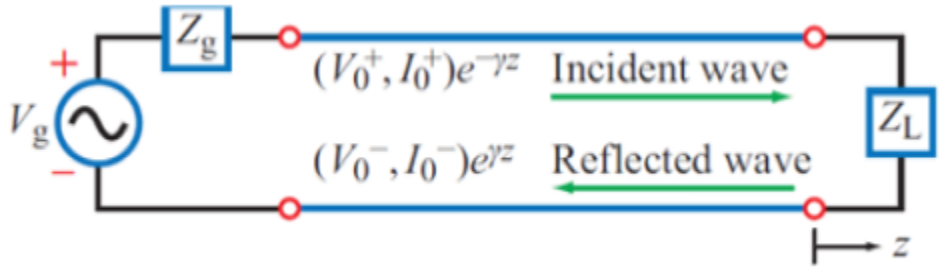
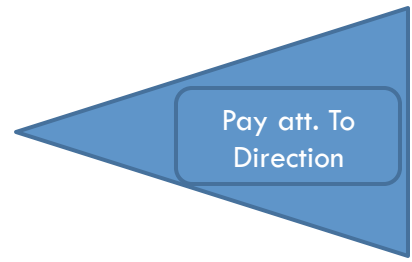
$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad (\Omega), \quad (2.29)$$



Make sure you know how we got this!

# Solution of Wave Equations (cont.)

So,  $V(z)$  and  $I(z)$  have two parts:  
But what are  $V_0^+$  and  $V_0^-$  ?

In general (each component has  
Magnitude and Phase):

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

$$V_0^+ = |V_0^+| e^{j\phi^+},$$

$$V_0^- = |V_0^-| e^{j\phi^-}.$$

Refer to  
Notes


$$\begin{aligned} v(z, t) &= \Re(\tilde{V}(z)e^{j\omega t}) \\ &= \Re\left[(V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}) e^{j\omega t}\right] \\ &= \Re\left[|V_0^+| e^{j\phi^+} e^{j\omega t} e^{-(\alpha+j\beta)z} \right. \\ &\quad \left. + |V_0^-| e^{j\phi^-} e^{j\omega t} e^{(\alpha+j\beta)z}\right] \\ &= |V_0^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) \\ &\quad + |V_0^-| e^{\alpha z} \cos(\omega t + \beta z + \phi^-) \end{aligned}$$

← We are interested in Sinusoidal  
Steady-state Condition

← wave along  $+z$  because coefficients of  $t$  and  $z$   
have opposite signs

← wave along  $-z$  because coefficients of  $t$  and  $z$  have  
the same sign

# Solution of Wave Equations (cont.)

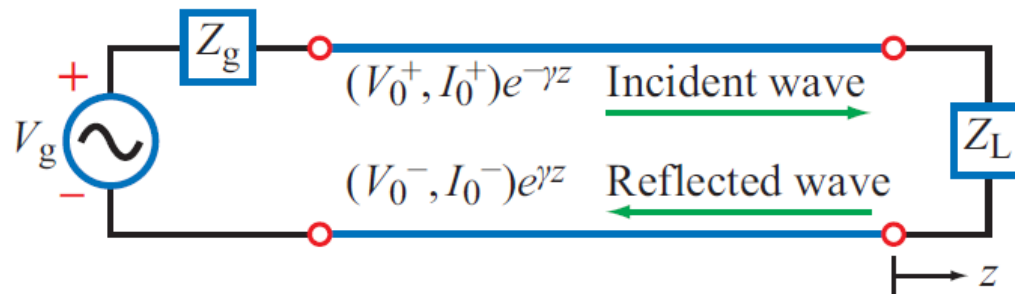

*The presence of two waves on the line propagating in opposite directions produces a standing wave.*

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

Applet for standing wave:

<http://www.physics.smu.edu/~olness/www/05fall1320/applet/pipe-waves.html>



# Example

- Verify the solution to the wave equation for voltage in phasor form:

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0, \quad (2.21)$$

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

Note:

$$V_0^+ = |V_0^+| e^{j\phi^+},$$

$$V_0^- = |V_0^-| e^{j\phi^-}.$$

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}. \quad (2.22)$$

$$\gamma = \alpha + j\beta$$

# Example 2-1: Air Line

Assume the following waves:

$$V(z,t) = 10 \cos(2\pi \cdot 700 \cdot 10^6 - 20z + 5)$$

$$I(z,t) = 0.2 \cos(2\pi \cdot 700 \cdot 10^6 - 20z + 5)$$

Assume having perfect dielectric insulator and the wire have perfect conductivity with no loss

Draw the transmission line model and Find  $C'$  and  $L'$

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad (\Omega),$$

$$\begin{aligned} \beta &= \Im(\gamma) \\ &= \Im\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right) \quad (\text{rad/m}). \end{aligned}$$

With  $R' = G' = 0$ , Eqs. (2.25b) and (2.29) reduce to

$$\begin{aligned} \beta &= \Im\left[\sqrt{(j\omega L')(j\omega C')}\right] \\ &= \Im\left(j\omega\sqrt{L'C'}\right) = \omega\sqrt{L'C'}, \\ Z_0 &= \sqrt{\frac{j\omega L'}{j\omega C'}} = \sqrt{\frac{L'}{C'}}. \end{aligned}$$

The ratio of  $\beta$  to  $Z_0$  is

$$\frac{\beta}{Z_0} = \omega C',$$

or

$$\begin{aligned} C' &= \frac{\beta}{\omega Z_0} \\ &= \frac{20}{2\pi \times 7 \times 10^8 \times 50} \\ &= 9.09 \times 10^{-11} \text{ (F/m)} = 90.9 \text{ (pF/m)}. \end{aligned}$$

From  $Z_0 = \sqrt{L'/C'}$ , it follows that

$$\begin{aligned} L' &= Z_0^2 C' \\ &= (50)^2 \times 90.9 \times 10^{-12} \\ &= 2.27 \times 10^{-7} \text{ (H/m)} = 227 \text{ (nH/m)}. \end{aligned}$$

# Section 2



# Transmission Line Characteristics



- Line characterization
  - ▣ Propagation Constant (function of frequency)
  - ▣ Impedance (function of frequency)
    - Lossy or Lossless
- If lossless (low ohmic losses)
  - ▣ Very high conductivity for the insulator
  - ▣ Negligible conductivity for the dielectric

# Lossless Transmission Line

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}.$$

If  $R' \ll \omega L'$  and  $G' \ll \omega C'$

Then:

$$\gamma = \alpha + j\beta = j\omega\sqrt{L'C'}, \quad (2.44)$$

$$\begin{aligned} \alpha &= 0 && \text{(lossless line),} \\ \beta &= \omega\sqrt{L'C'} && \text{(lossless line).} \end{aligned} \quad (2.45)$$

What is  $Z_0$ ? 
$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{L'C'}},$$

$$u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}}.$$

$$\beta = \omega\sqrt{\mu\varepsilon} \quad (\text{rad/m}), \quad (2.49)$$

$$u_p = \frac{1}{\sqrt{\mu\varepsilon}} \quad (\text{m/s}), \quad (2.50)$$

Non-dispersive line:

All frequency components have the same speed!

# Example

- Assume Lossless TL;
- Relative permittivity is 4
- $C' = 10 \text{ pF/m}$ 
  - ▣ Find phase velocity
  - ▣ Find  $L'$
  - ▣ Find  $Z_0$

```
>> u=4*pi*1e-7;
>> e=8.854e-12

e =

    8.8540e-012

>> up=sqrt(1/(u*e*4))

up =

    1.4990e+008

>> L=1/10e-12 * 1/(up*up)

L =

    4.4505e-006

>> Zo=sqrt(L/10e-12)

Zo =


    667.1211
```

**Table 2-2:** Characteristic parameters of transmission lines.

	<b>Propagation Constant</b> $\gamma = \alpha + j\beta$	<b>Phase Velocity</b> $u_p$	<b>Characteristic Impedance</b> $Z_0$
<b>General case</b>	$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$	$u_p = \omega/\beta$	$Z_0 = \sqrt{\frac{(R' + j\omega L')}{(G' + j\omega C')}}$
<b>Lossless</b> ( $R' = G' = 0$ )	$\alpha = 0, \beta = \omega\sqrt{\epsilon_r}/c$	$u_p = c/\sqrt{\epsilon_r}$	$Z_0 = \sqrt{L'/C'}$
<b>Lossless coaxial</b>	$\alpha = 0, \beta = \omega\sqrt{\epsilon_r}/c$	$u_p = c/\sqrt{\epsilon_r}$	$Z_0 = (60/\sqrt{\epsilon_r}) \ln(b/a)$
<b>Lossless two-wire</b>	$\alpha = 0, \beta = \omega\sqrt{\epsilon_r}/c$	$u_p = c/\sqrt{\epsilon_r}$	$Z_0 = (120/\sqrt{\epsilon_r})$ $\cdot \ln[(D/d) + \sqrt{(D/d)^2 - 1}]$ $Z_0 \simeq (120/\sqrt{\epsilon_r}) \ln(2D/d),$ if $D \gg d$
<b>Lossless parallel-plate</b>	$\alpha = 0, \beta = \omega\sqrt{\epsilon_r}/c$	$u_p = c/\sqrt{\epsilon_r}$	$Z_0 = (120\pi/\sqrt{\epsilon_r}) (h/w)$

Notes: (1)  $\mu = \mu_0$ ,  $\epsilon = \epsilon_r \epsilon_0$ ,  $c = 1/\sqrt{\mu_0 \epsilon_0}$ , and  $\sqrt{\mu_0/\epsilon_0} \simeq (120\pi) \Omega$ , where  $\epsilon_r$  is the relative permittivity of insulating material. (2) For coaxial line,  $a$  and  $b$  are radii of inner and outer conductors. (3) For two-wire line,  $d$  = wire diameter and  $D$  = separation between wire centers. (4) For parallel-plate line,  $w$  = width of plate and  $h$  = separation between the plates.

# The Big Idea....

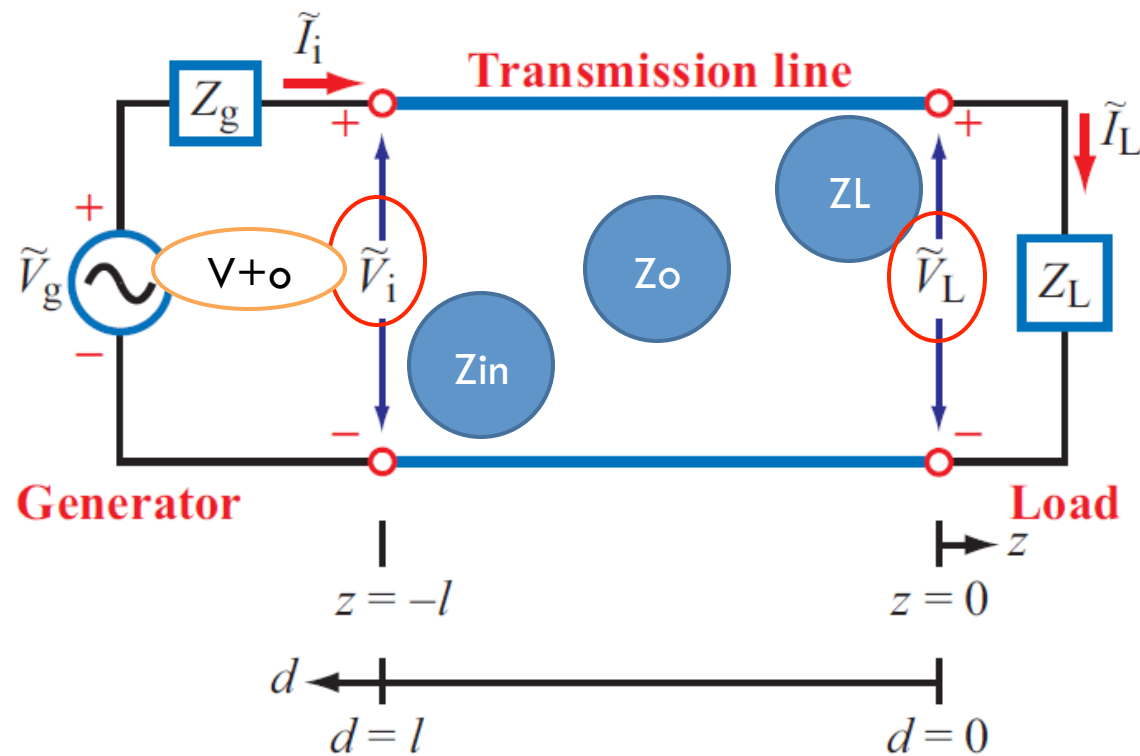

What is the voltage/current magnitude at different points of the line in the presence of load??



# Voltage Reflection Coefficient

Consider looking from the Load point of view

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

$$\tilde{V}_L = \tilde{V}(z=0) = V_0^+ + V_0^-,$$


$$\tilde{I}_L = \tilde{I}(z=0) = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}.$$

At the load ( $z = 0$ ):

$$Z_L = \frac{\tilde{V}_L}{\tilde{I}_L}$$

$$Z_L = \left( \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) Z_0.$$

The smaller  
the better!

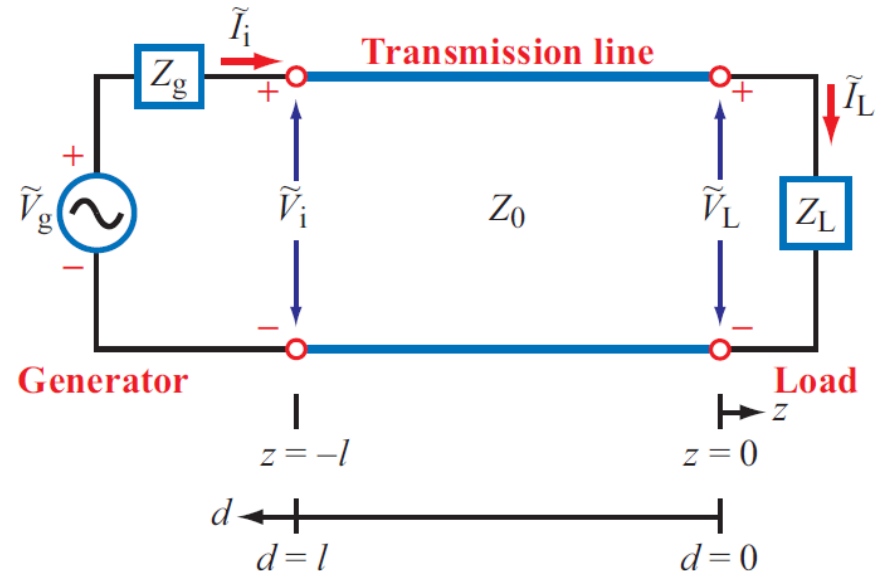

$$\begin{aligned} \Gamma &= \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} && \text{Reflection coefficient} \\ &= \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \\ &= \frac{z_L - 1}{z_L + 1} \quad (\text{dimensionless}), \quad (2.59) \end{aligned}$$

$$z_L = \frac{Z_L}{Z_0} \quad \text{Normalized load impedance}$$

# Expressing wave in phasor form:

□ Remember:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

□ If lossless

▣ no attenuation constant

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$

$$V_0^- = \Gamma V_0^+$$

All of these wave representations  
are **along** the  
Transmission Line

# Special Line Conditions (Lossless)

- Matching line
  - ▣  $Z_L = Z_0 \rightarrow \Gamma = 0; V_{\text{ref}} = 0$
- Open Circuit
  - ▣  $Z_L = \text{INF} \rightarrow \Gamma = 1; V_{\text{ref}} = V_{\text{inc}}$
- Short Circuit
  - ▣  $Z_L = 0 \rightarrow \Gamma = -1; V_{\text{ref}} = -V_{\text{inc}}$

$$\begin{aligned}\Gamma &= \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \\ &= \frac{z_L - 1}{z_L + 1} \quad (\text{dimensionless}), \quad (2.59)\end{aligned}$$

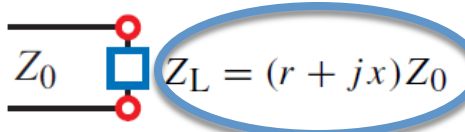
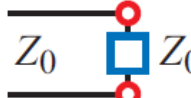

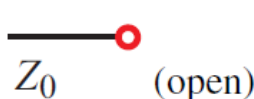
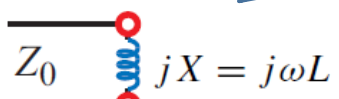
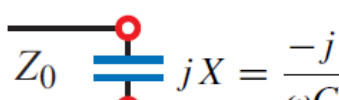
Remember:  
Everything is with respect  
to the load so far!

$$\frac{I_0^-}{I_0^+} = -\frac{V_0^-}{V_0^+} = -\Gamma. \quad (2.61)$$

# Voltage Reflection Coefficient

$$\Gamma = |\Gamma|e^{j\theta_r}$$

## Reflection Coefficient $\Gamma = |\Gamma|e^{j\theta_r}$

Load	$ \Gamma $	$\theta_r$
 $Z_L = (r + jx)Z_0$	$\left[ \frac{(r-1)^2 + x^2}{(r+1)^2 + x^2} \right]^{1/2}$	$\tan^{-1} \left( \frac{x}{r-1} \right) - \tan^{-1} \left( \frac{x}{r+1} \right)$
 $Z_0$	0 (no reflection)	irrelevant
 $Z_0$ (short)	1	$\pm 180^\circ$ (phase opposition)
 $Z_0$ (open)	1	0 (in-phase)
 $Z_0$ $jX = j\omega L$	1	$\pm 180^\circ - 2 \tan^{-1} x$
 $Z_0$ $jX = \frac{-j}{\omega C}$	1	$\pm 180^\circ + 2 \tan^{-1} x$


Pay attention!

Normalized load impedance

$$z_L = Z_L/Z_0 = (R + jX)/Z_0 = r + jx$$
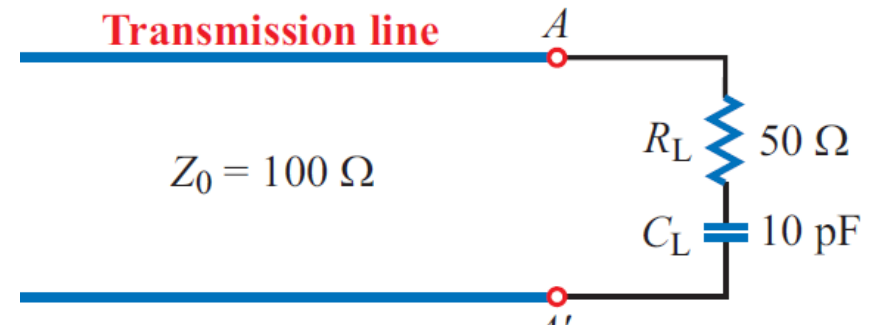
## Example

A  $100\text{-}\Omega$  transmission line is connected to a load consisting of a  $50\text{-}\Omega$  resistor in series with a  $10\text{-pF}$  capacitor. Find the reflection coefficient at the load for a  $100\text{-MHz}$  signal.



# Standing Waves


## Finding Voltage Magnitude

We are interested to know what happens to the magnitude of the  $|V|$  as such **interference** is created!

$$V_0^- = \Gamma V_0^+ \quad \text{When lossless!}$$

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$
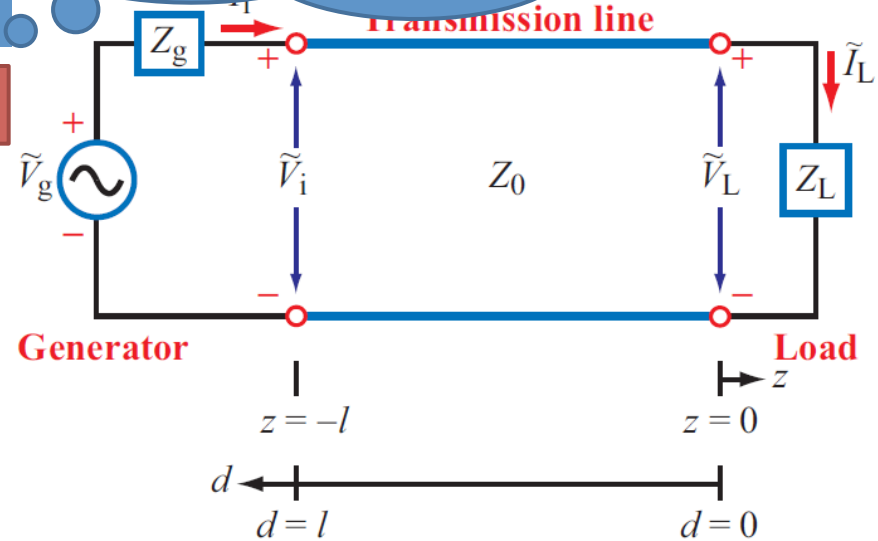
$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$




Remember: Standing wave is created due to **interference** between the traveling waves (incident & reflected)

Note: When there is no REFLECTION Coef. Of Ref. = 0  $\rightarrow$  No standing wave!
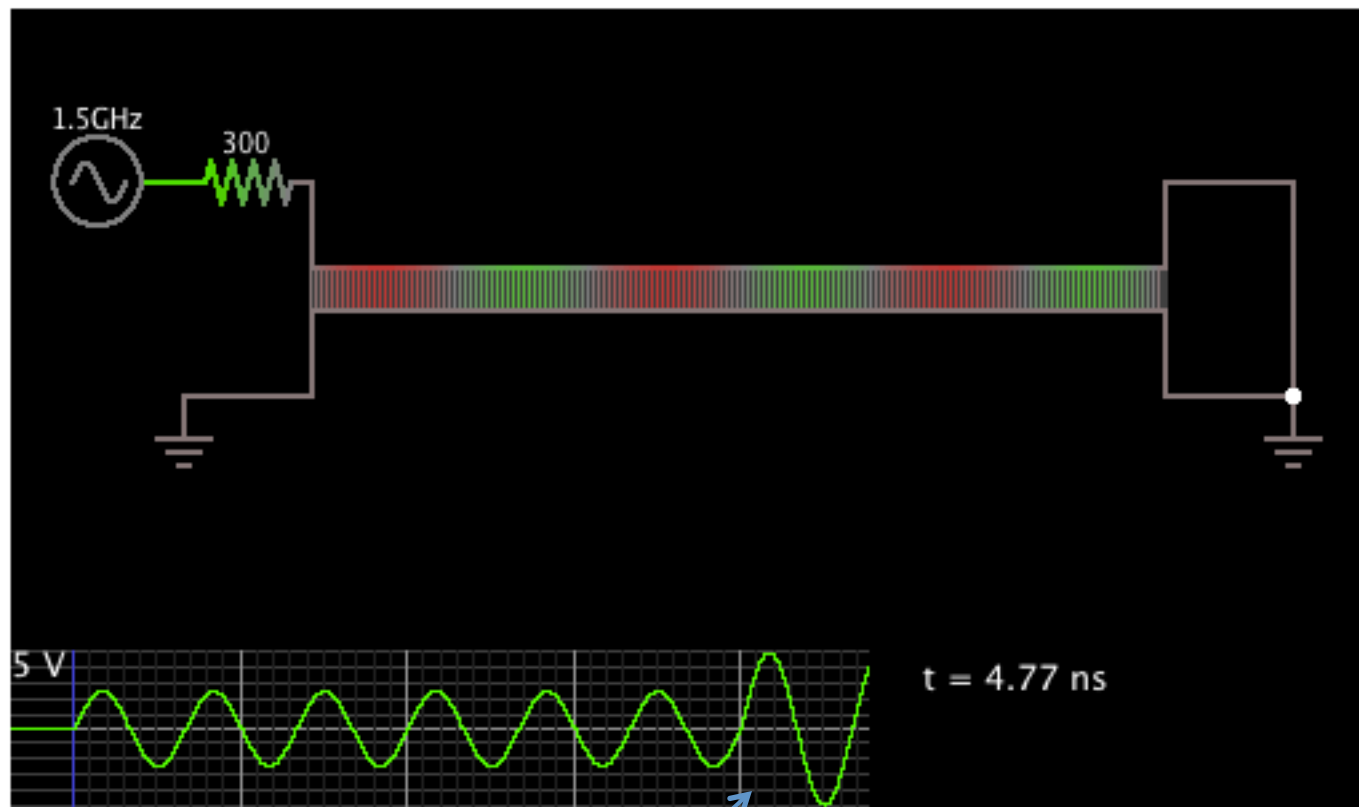
# Standing Wave

<http://www.falstad.com/circuit/e-tlstand.html>



Due to standing wave the received wave at the load is now different

# Standing Waves

## Finding Voltage Magnitude

$$V_0^- = \Gamma V_0^+$$

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$


voltage magnitude due to interference

$$|\tilde{V}(z)| = \left\{ \left[ V_0^+ (e^{-j\beta z} + |\Gamma| e^{j\theta_r} e^{j\beta z}) \right] \cdot \left[ (V_0^+)^* (e^{j\beta z} + |\Gamma| e^{-j\theta_r} e^{-j\beta z}) \right] \right\}^{1/2}$$

$$= |V_0^+| \left[ 1 + |\Gamma|^2 + |\Gamma| (e^{j(2\beta z + \theta_r)} + e^{-j(2\beta z + \theta_r)}) \right]^{1/2}$$

$$= |V_0^+| \left[ 1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta z + \theta_r) \right]^{1/2},$$

Conjugate!

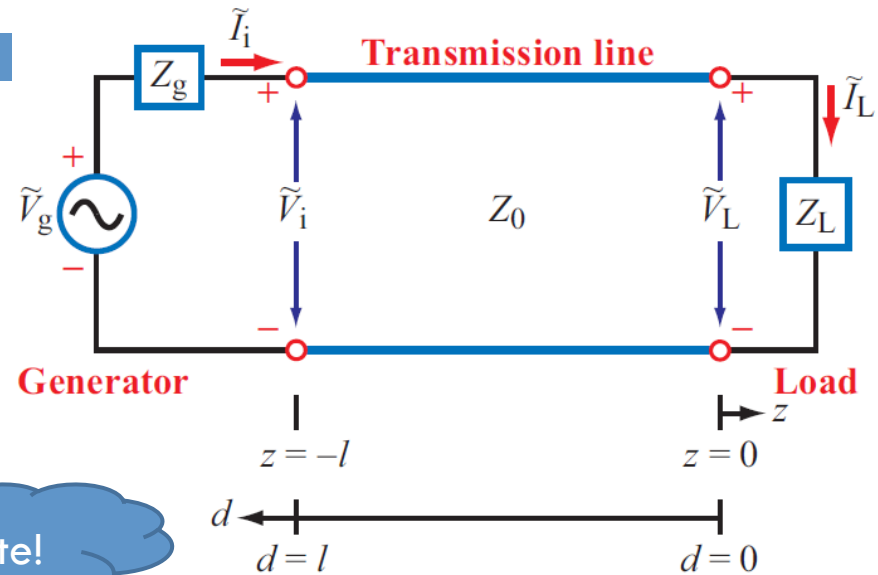

This is **standing wave!**  
Each position has a different value!

voltage magnitude

is the magnitude at the load?  
What  $Z=-d$



# Standing Waves

## Finding Voltage Magnitude

$$V_0^- = \Gamma V_0^+$$

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$


$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$

$$|\tilde{V}(d)| = |V_0^+| \left[ 1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}$$

$$|\tilde{I}(d)| = \frac{|V_0^+|}{Z_0} \left[ 1 + |\Gamma|^2 - 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}$$

Let's see how the magnitude looks like at different z values!

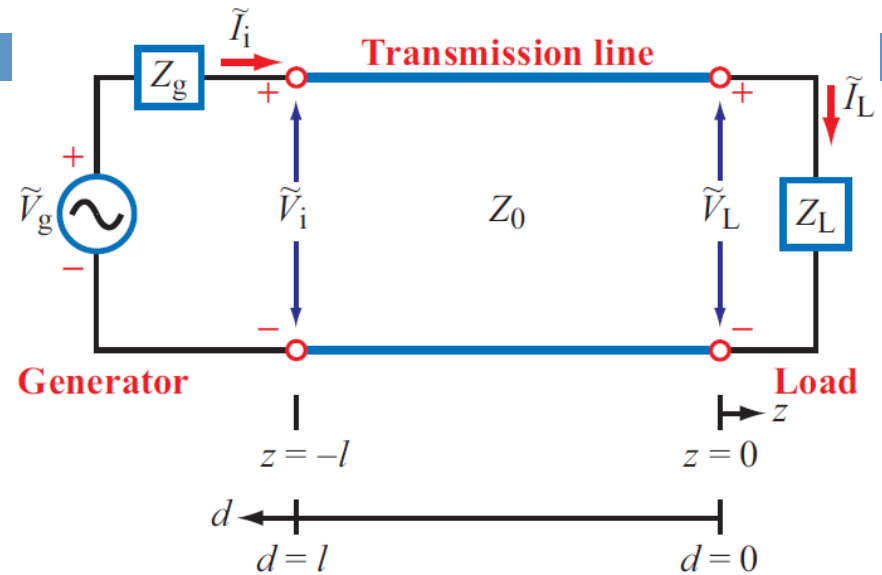Remember max current occurs where minimum voltage occurs!




voltage magnitude at  $z = -d$

current magnitude at the source

# Standing Wave Patterns for 3 Types of Loads



(Matched, Open, Short)

No reflection, No standing wave

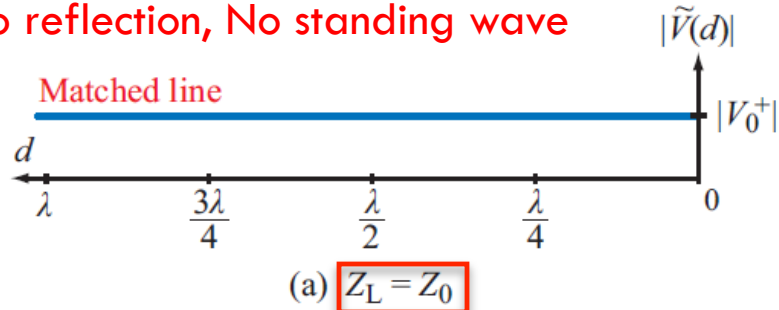

$$|\tilde{V}(d)| = |V_0^+| \left[ 1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}.$$

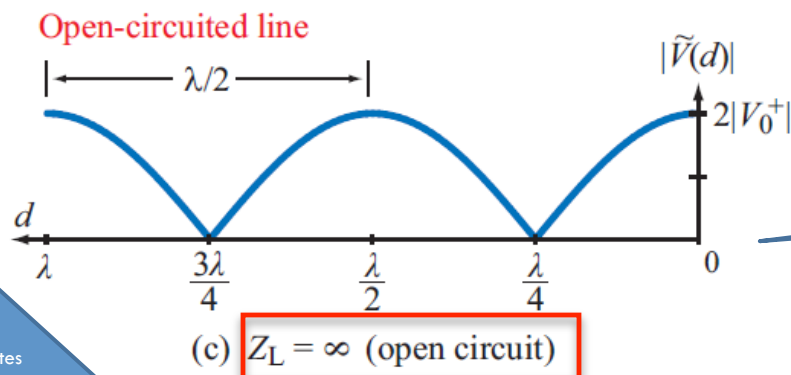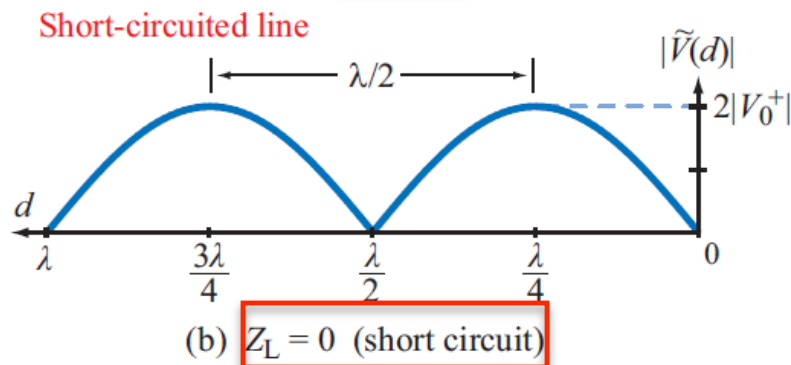- Matching line
  - ▣  $Z_L = Z_0 \rightarrow \Gamma = 0; V_{ref} = 0$
- Short Circuit
  - ▣  $Z_L = 0 \rightarrow \Gamma = -1; V_{ref} = -V_{inc}$  (angle  $-/+ \pi$ )
- Open Circuit
  - ▣  $Z_L = \infty \rightarrow \Gamma = 1; V_{ref} = V_{inc}$  (angle is 0)




Remember max current occurs where minimum voltage occurs!


# Standing Wave Patterns for 3 Types of Loads

(Matched, Open, Short)


No reflection, No standing wave

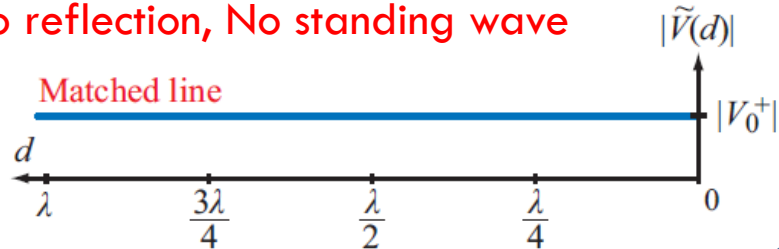

(a)  $Z_L = Z_0$

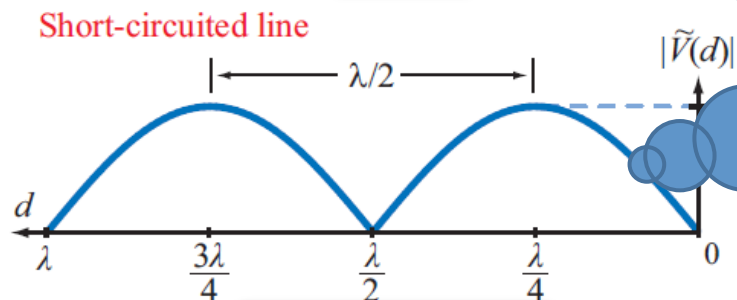

(b)  $Z_L = 0$  (short circuit)

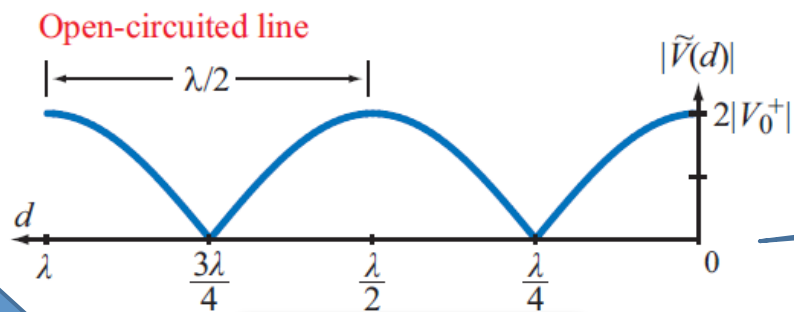


(c)  $Z_L = \infty$  (open circuit)

BUT WHEN DO  
MAX & MIN  
Voltages Occur?

Remember max current occurs  
where minimum voltage occurs!

# Standing Wave Pattern

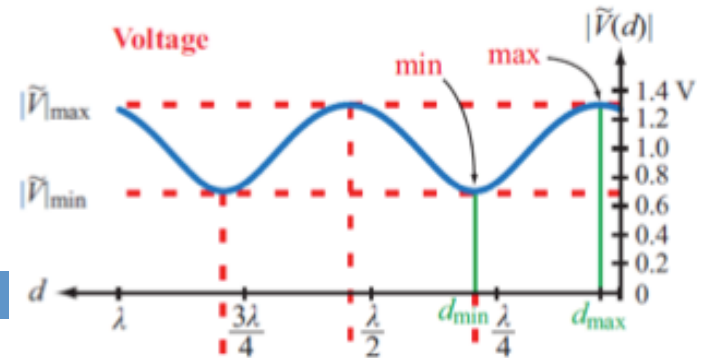

## □ For Voltage:

- Max occurs when  $\cos(\ ) = 1 \rightarrow$
- In this case  $n=0,1,2,\dots$
- NOTE that the FIRST & SECOND  $d_{\max}$  are  $\lambda/2$  apart
- Thus, First MIN happens  $\lambda/4$  after first  $d_{\max}$
- And so on....

$$2\beta d_{\max} - \theta_r = 2n\pi$$

$$d_{\max} = \frac{\theta_r + 2n\pi}{2\beta} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2},$$

$$\begin{cases} n = 1, 2, \dots & \text{if } \theta_r < 0, \\ n = 0, 1, 2, \dots & \text{if } \theta_r \geq 0, \end{cases}$$

$$|\tilde{V}(d)| = |V_0^+| \left[ 1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}.$$

$$|\tilde{I}(d)| = \frac{|V_0^+|}{Z_0} \left[ 1 + |\Gamma|^2 - 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}.$$

# Finding Maxima & Minima Of Voltage Magnitude

$$|\tilde{V}(d)| = |V_0^+| \left[ 1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}.$$

$$|\tilde{V}|_{\min} = |V_0^+| [1 - |\Gamma|],$$

$$\text{when } (2\beta d_{\min} - \theta_r) = (2n + 1)\pi$$



$$|\tilde{V}(d)| = |\tilde{V}|_{\max} = |V_0^+| [1 + |\Gamma|],$$

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad (\text{dimensionless})$$

**S = Voltage Standing Wave Ratio (VSWR)**

For a matched load: **S = 1**

For a short, open, or purely reactive load:  
**S(open)=S(short) = INF where  $|\Gamma|=1$ ;**

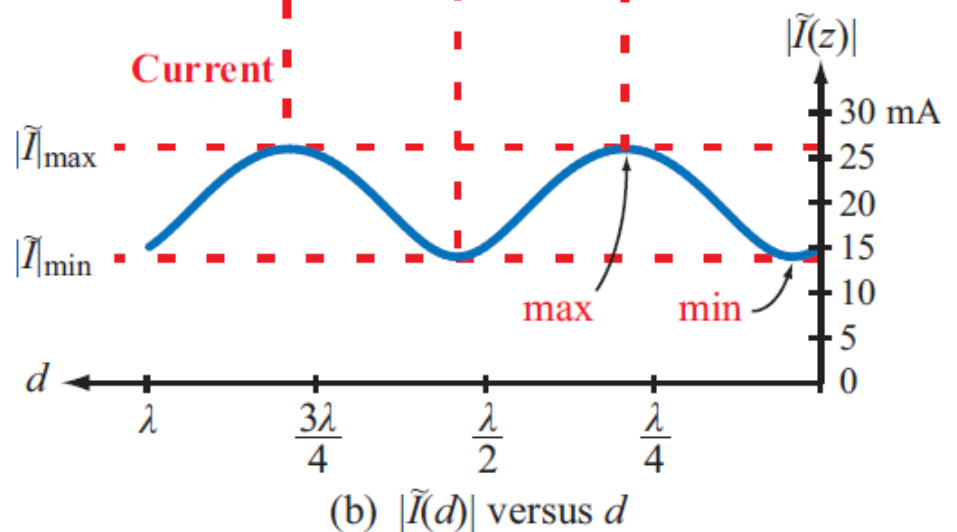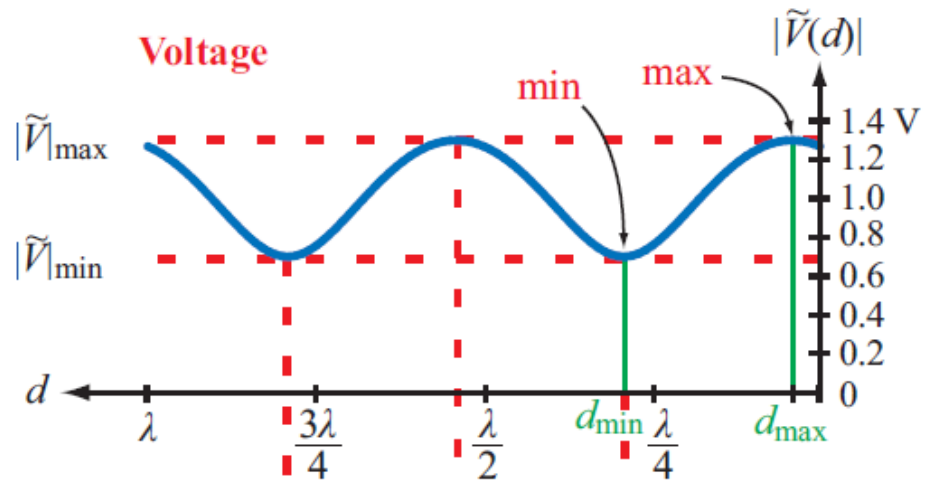

# What is the Reflection Coefficient ( $\Gamma_d$ ) at any point away from the load? (assume lossless line)


At a distance  $d$  from the load:

$$\begin{aligned}
 Z(d) &= \frac{\tilde{V}(d)}{\tilde{I}(d)} \\
 &= \frac{V_0^+ [e^{j\beta d} + \Gamma e^{-j\beta d}]}{V_0^+ [e^{j\beta d} - \Gamma e^{-j\beta d}]} Z_0 \\
 &= Z_0 \left[ \frac{1 + \Gamma e^{-j2\beta d}}{1 - \Gamma e^{-j2\beta d}} \right] \\
 &= Z_0 \left[ \frac{1 + \Gamma_d}{1 - \Gamma_d} \right] (\Omega),
 \end{aligned}$$

where we define

$$\Gamma_d = \Gamma e^{-j2\beta d} = |\Gamma| e^{j\theta_r} e^{-j2\beta d} = |\Gamma| e^{j(\theta_r - 2\beta d)}$$

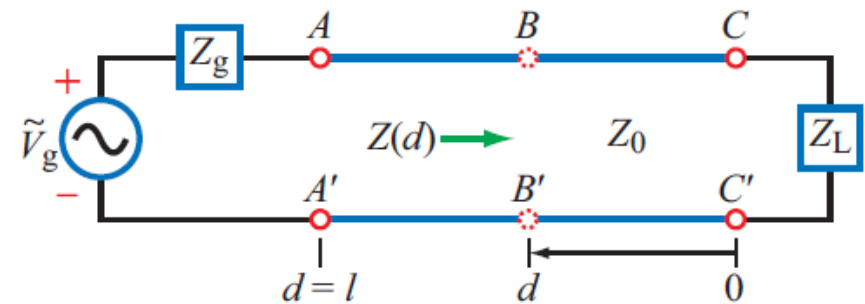as the *phase-shifted voltage reflection coefficient*,



(a) Actual circuit

Wave impedance

# Example

<http://www.bessernet.com/Ereflecto/tutorialFrameset.htm>

## Reflectometer Calculator

Type a value in one of the fields below and hit 'enter':

Reflection Coefficient

SWR

Return Loss



Mismatch Loss

eR




Z1

Show two interfaces

Resume

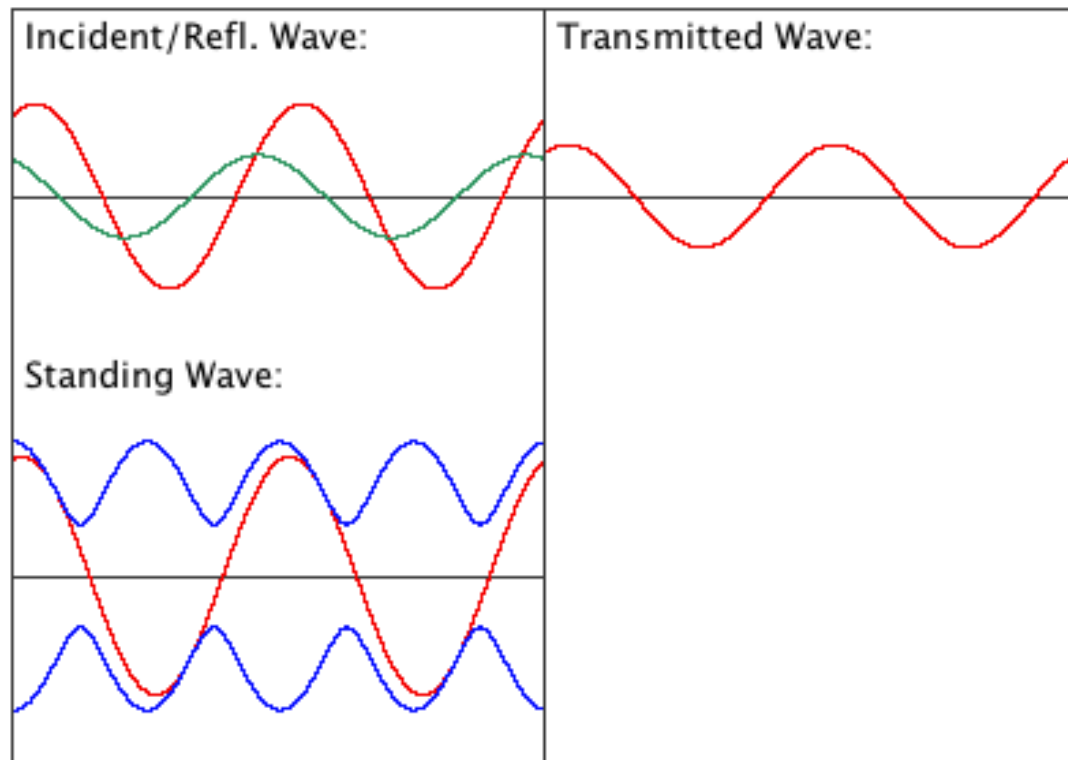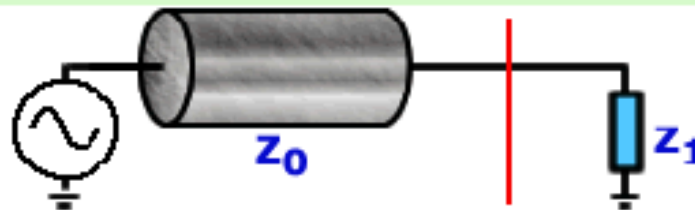

Example

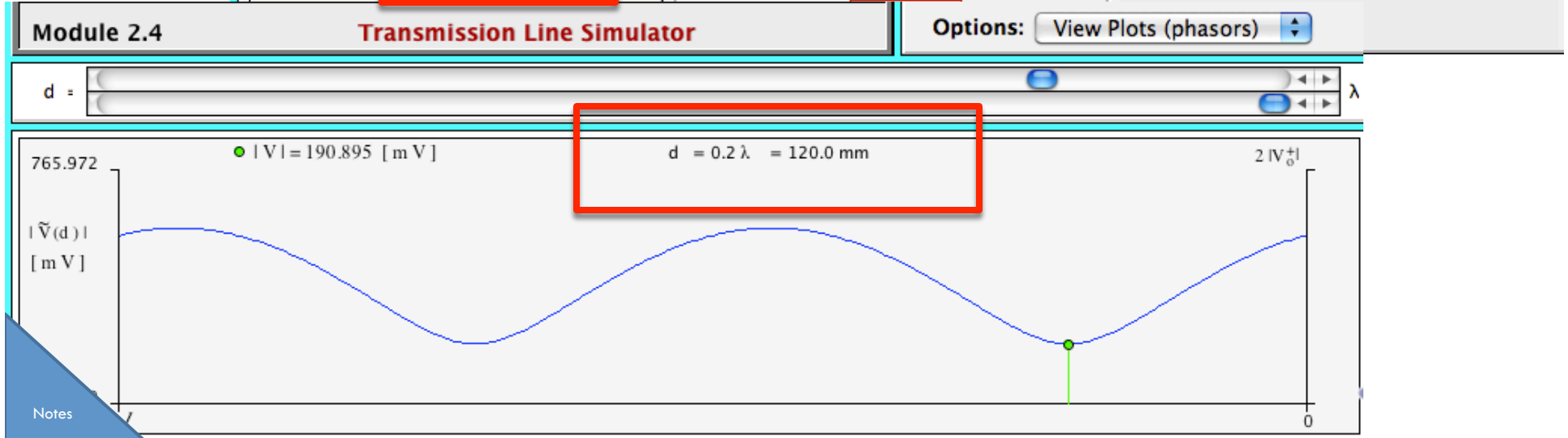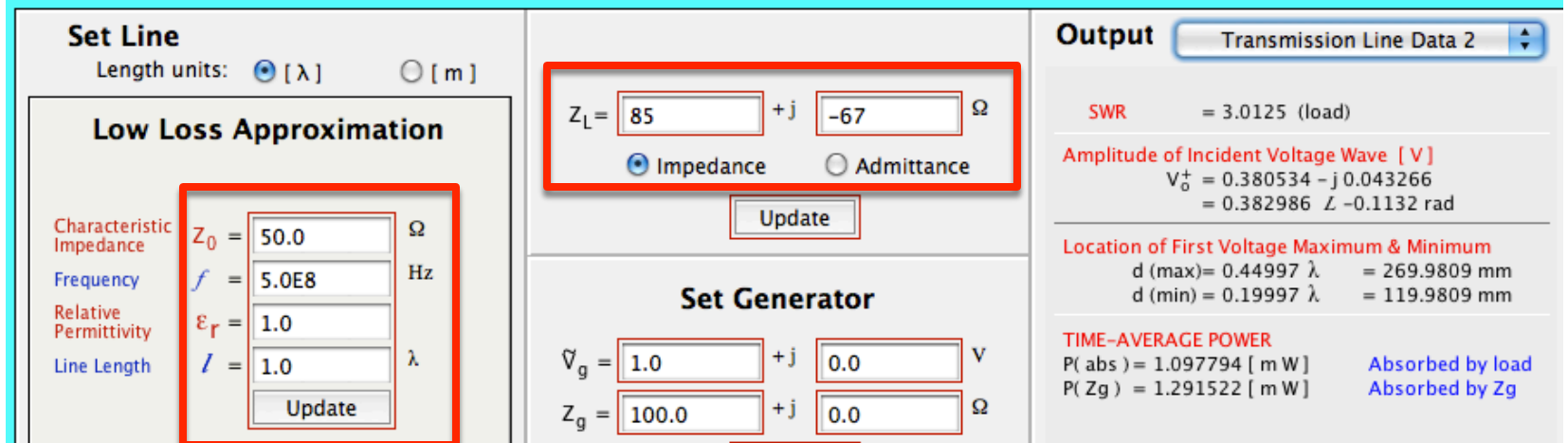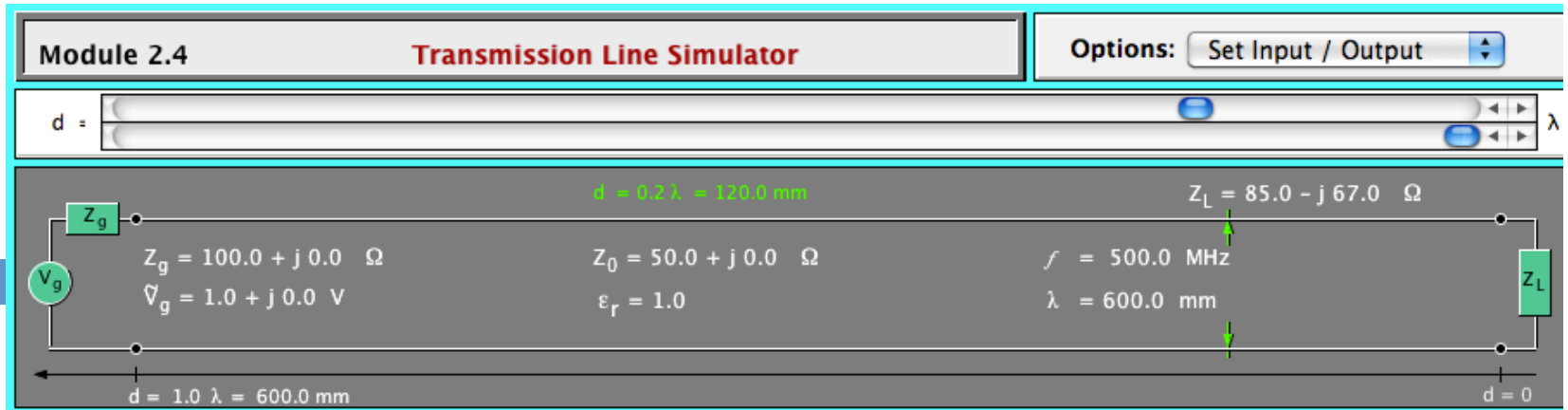



# Input Impedance

Wave Impedance

$$Z_d = Z_0 \left[ \frac{1 + \Gamma_d}{1 - \Gamma_d} \right]$$

$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta l + j \sin \beta l}{\cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left( \frac{Z_L + j \tan \beta l}{1 + j Z_L \tan \beta l} \right). \end{aligned} \quad (2.79)$$

What is input voltage?

$$\tilde{V}_i = \tilde{I}_i Z_{in} = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}}, \quad (2.80)$$



Simultaneously, from the standpoint of the transmission line, the voltage across it at the input of the line is given by Eq. (2.63a) with  $z = -l$ :

$$\tilde{V}_i = \tilde{V}(-l) = V_0^+ [e^{j\beta l} + \Gamma e^{-j\beta l}]. \quad (2.81)$$

Equating Eq. (2.80) to Eq. (2.81) and then solving for  $V_0^+$  leads

$$V_0^+ = \left( \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left( \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right). \quad (2.82)$$

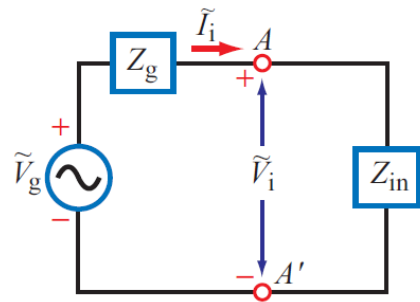
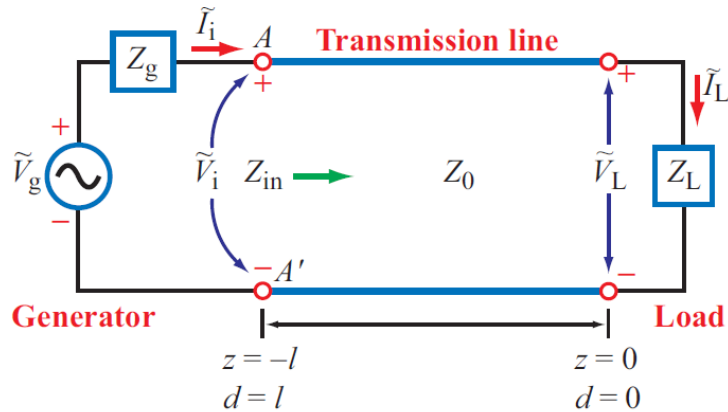
$$z_L = Z_L / Z_0 = (R + jX) / Z_0 = r + jx$$



At input,  $d = l$ :  $Z_{in} = Z(l) = Z_0 \left[ \frac{1 + \Gamma_l}{1 - \Gamma_l} \right]$  to

$$\Gamma_l = \Gamma e^{-j2\beta l} = |\Gamma| e^{j(\theta_r - 2\beta l)}.$$

# Short-Circuited Line

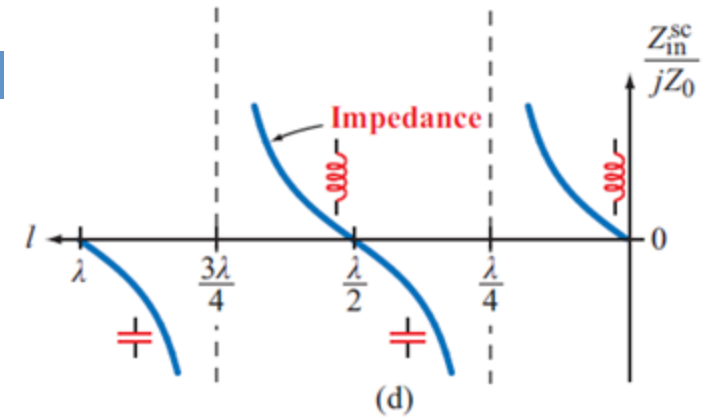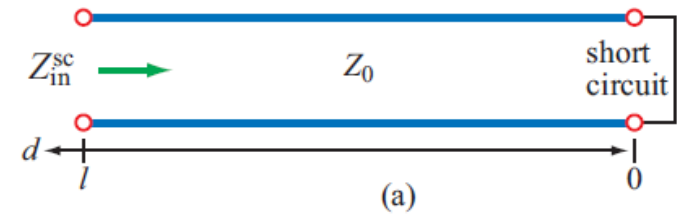

$$Z_{in} = Z_0 \left( \frac{z_L \cos \beta l + j \sin \beta l}{\cos \beta l + j z_L \sin \beta l} \right)$$

$$= Z_0 \left( \frac{z_L + j \tan \beta l}{1 + j z_L \tan \beta l} \right). \quad (2.79)$$

$$Z_L = 0$$

$$j\omega L_{eq} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \geq 0$$

$$\frac{1}{j\omega C_{eq}} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \leq 0$$

# Input Impedance

## Special Cases - Lossless

$$Z_{in} = Z_0 \left( \frac{z_L \cos \beta l + j \sin \beta l}{\cos \beta l + j z_L \sin \beta l} \right)$$

$$= Z_0 \left( \frac{z_L + j \tan \beta l}{1 + j z_L \tan \beta l} \right). \quad (2.79)$$





$$Z_{in}^{sc} = \frac{\tilde{V}_{sc}(l)}{\tilde{I}_{sc}(l)} = jZ_0 \tan \beta l.$$

$$j\omega L_{eq} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \geq 0$$

$$\frac{1}{j\omega C_{eq}} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \leq 0$$

$$Z_{in}^{oc} = \frac{\tilde{V}_{oc}(l)}{\tilde{I}_{oc}(l)} = -jZ_0 \cot \beta l.$$

What is  $Z_{in}$  when matched?

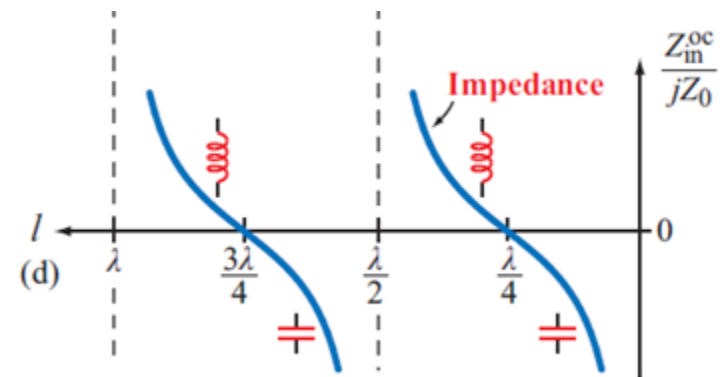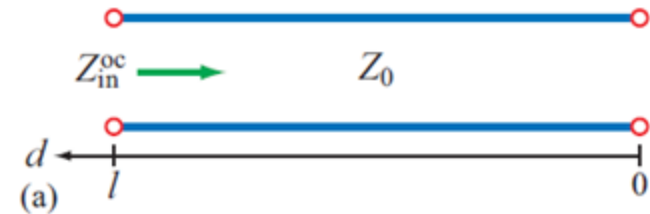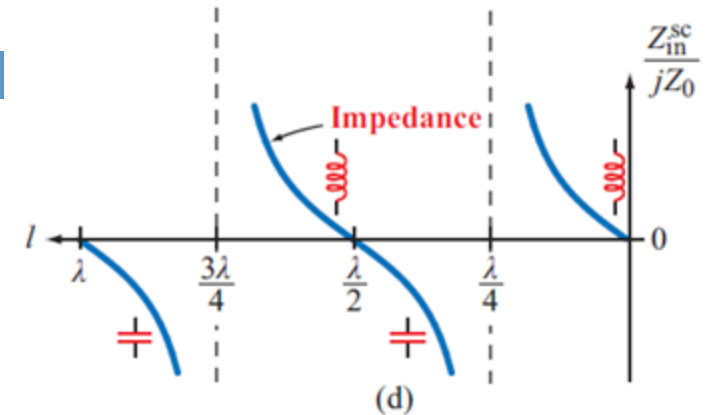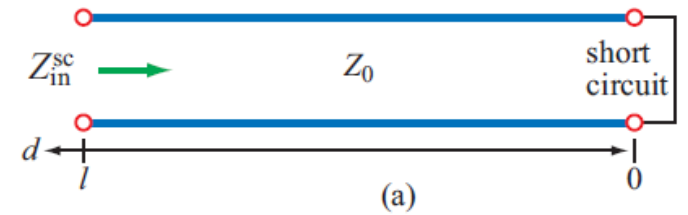

# Short-Circuit/Open-Circuit Method

- For a line of known length  $l$ , measurements of its input impedance, one when terminated in a short and another when terminated in an open, can be used to find its characteristic impedance  $Z_0$  and electrical length  $\beta l$

$$Z_{\text{in}}^{\text{sc}} = \frac{\tilde{V}_{\text{sc}}(l)}{\tilde{I}_{\text{sc}}(l)} = jZ_0 \tan \beta l.$$

$$Z_{\text{in}}^{\text{oc}} = \frac{\tilde{V}_{\text{oc}}(l)}{\tilde{I}_{\text{oc}}(l)} = -jZ_0 \cot \beta l.$$



$$Z_0 = \sqrt{+Z_{\text{in}}^{\text{sc}} Z_{\text{in}}^{\text{oc}}},$$

$$\tan \beta l = \sqrt{\frac{-Z_{\text{in}}^{\text{sc}}}{Z_{\text{in}}^{\text{oc}}}}.$$

**Table 2-4:** Properties of standing waves on a lossless transmission line.

<b>Voltage Maximum</b>	$ \tilde{V} _{\max} =  V_0^+ [1 +  \Gamma ]$
<b>Voltage Minimum</b>	$ \tilde{V} _{\min} =  V_0^+ [1 -  \Gamma ]$
Positions of voltage maxima (also positions of current minima)	$d_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n = 0, 1, 2, \dots$
Position of first maximum (also position of first current minimum)	$d_{\max} = \begin{cases} \frac{\theta_r \lambda}{4\pi}, & \text{if } 0 \leq \theta_r \leq \pi \\ \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2}, & \text{if } -\pi \leq \theta_r \leq 0 \end{cases}$
Positions of voltage minima (also positions of current maxima)	$d_{\min} = \frac{\theta_r \lambda}{4\pi} + \frac{(2n + 1)\lambda}{4}, \quad n = 0, 1, 2, \dots$
Position of first minimum (also position of first current maximum)	$d_{\min} = \frac{\lambda}{4} \left( 1 + \frac{\theta_r}{\pi} \right)$
<b>Input Impedance</b>	$Z_{\text{in}} = Z_0 \left( \frac{z_L + j \tan \beta l}{1 + j z_L \tan \beta l} \right) = Z_0 \left( \frac{1 + \Gamma_l}{1 - \Gamma_l} \right)$
Positions at which $Z_{\text{in}}$ is real	at voltage maxima and minima
$Z_{\text{in}}$ at voltage maxima	$Z_{\text{in}} = Z_0 \left( \frac{1 +  \Gamma }{1 -  \Gamma } \right)$
$Z_{\text{in}}$ at voltage minima	$Z_{\text{in}} = Z_0 \left( \frac{1 -  \Gamma }{1 +  \Gamma } \right)$
$Z_{\text{in}}$ of short-circuited line	$Z_{\text{in}}^{\text{sc}} = j Z_0 \tan \beta l$
$Z_{\text{in}}$ of open-circuited line	$Z_{\text{in}}^{\text{oc}} = -j Z_0 \cot \beta l$
$Z_{\text{in}}$ of line of length $l = n\lambda/2$	$Z_{\text{in}} = Z_L, \quad n = 0, 1, 2, \dots$
$Z_{\text{in}}$ of line of length $l = \lambda/4 + n\lambda/2$	$Z_{\text{in}} = Z_0^2/Z_L, \quad n = 0, 1, 2, \dots$
$Z_{\text{in}}$ of matched line	$Z_{\text{in}} = Z_0$
$ V_0^+ $ = amplitude of incident wave; $\Gamma =  \Gamma e^{j\theta_r}$ with $-\pi < \theta_r < \pi$ ; $\theta_r$ in radians; $\Gamma_l = \Gamma e^{-j2\beta l}$ .	

# Example

- Check your notes!

# Power Flow

## □ How much power is flowing and reflected?

### □ Instantaneous $P(d,t) = v(d,t) \cdot i(d,t)$

■ Incident

■ Reflected

$$P^i(d, t) = \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)],$$

$$P^r(d, t) = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t - 2\beta d + 2\phi^+ + 2\theta_r)].$$

### □ Average power: $P_{av} = P_{av}^i + P_{av}^r$

■ Time-domain Approach

■ Phasor-domain Approach (z and t independent)

■  $\frac{1}{2} \operatorname{Re}\{I^*(z) \cdot V(z)\}$

# Instantaneous Power Flow

$$\begin{aligned}
 v(d, t) &= \Re\{[\tilde{V}e^{j\omega t}]\} \\
 &= \Re\{|V_0^+|e^{j\phi^+}(e^{j\beta d} + |\Gamma|e^{j\theta_r}e^{-j\beta d})e^{j\omega t}\} \\
 &= |V_0^+|[\cos(\omega t + \beta d + \phi^+) \\
 &\quad + |\Gamma| \cos(\omega t - \beta d + \phi^+ + \theta_r)], \quad (2.99a)
 \end{aligned}$$

$$\begin{aligned}
 i(d, t) &= \frac{|V_0^+|}{Z_0}[\cos(\omega t + \beta d + \phi^+) \\
 &\quad - |\Gamma| \cos(\omega t - \beta d + \phi^+ + \theta_r)], \quad (2.99b)
 \end{aligned}$$

$$\begin{aligned}
 P(d, t) &= v(d, t) i(d, t) \\
 &= |V_0^+|[\cos(\omega t + \beta d + \phi^+) \\
 &\quad + |\Gamma| \cos(\omega t - \beta d + \phi^+ + \theta_r)] \\
 &\quad \times \frac{|V_0^+|}{Z_0}[\cos(\omega t + \beta d + \phi^+) \\
 &\quad - |\Gamma| \cos(\omega t - \beta d + \phi^+ + \theta_r)] \\
 &= \frac{|V_0^+|^2}{Z_0}[\cos^2(\omega t + \beta d + \phi^+) \\
 &\quad - |\Gamma|^2 \cos^2(\omega t - \beta d + \phi^+ + \theta_r)]
 \end{aligned}$$

$$P^i(d, t) = \frac{|V_0^+|^2}{Z_0} \cos^2(\omega t + \beta d + \phi^+) \quad (\text{W}),$$

$$P^r(d, t) = -|\Gamma|^2 \frac{|V_0^+|^2}{Z_0} \cos^2(\omega t - \beta d + \phi^+ + \theta_r)$$

Using the trigonometric identity

$$\cos^2 x = \frac{1}{2}(1 + \cos 2x),$$

the expressions in Eq. (2.101) can be rewritten as

$$P^i(d, t) = \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)],$$

$$\begin{aligned}
 P^r(d, t) &= -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t - 2\beta d \\
 &\quad + 2\phi^+ + 2\theta_r)].
 \end{aligned}$$

*The power oscillates at twice the rate of the voltage or current.*




# Average Power

(Phasor Approach)

Avg Power:  $\frac{1}{2} \text{Re}\{I(z) * V_{-}(z)\}$

$$P^i(d, t) = \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)]$$

$$P^r(d, t) = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t - 2\beta d + 2\phi^+ + 2\theta_r)].$$

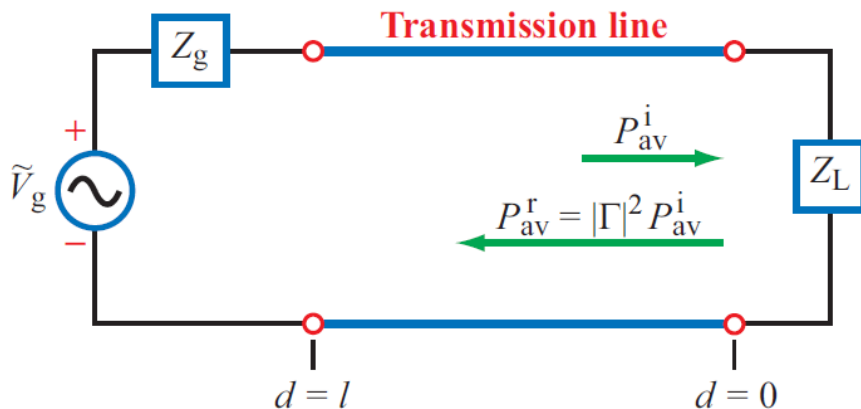

$$V_0^+ = \left( \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left( \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right).$$

Fraction of power reflected!

$$P_{av}^i = \frac{|V_0^+|^2}{2Z_0} \quad (\text{W}), \quad (2.104)$$

which is identical with the dc term of  $P^i(d, t)$  given by Eq. (2.102a). A similar treatment for the reflected wave gives

$$P_{av}^r = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} = -|\Gamma|^2 P_{av}^i. \quad (2.105)$$

*The average reflected power is equal to the average incident power, diminished by a multiplicative factor of  $|\Gamma|^2$ .*

# Example

- Assume  $Z_0=50$  ohm,  $Z_L=100+i50$  ohm; What fraction of power is reflected?

$$P_{av}^r = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} = -|\Gamma|^2 P_{av}^i. \quad (2.105)$$

```
>> x=(50+i*50)/(150+i*50)
```

```
x =
```

```
0.4000 + 0.2000i
```

```
>> mag=abs(x)
```

```
mag =
```

```
0.4472
```

```
>> angle=cart2pol(.4,.2)
```

```
angle =
```

```
0.4636
```

```
angle =
```

```
0.4636
```

```
>> radtodeg(.4636)
```

```
ans =
```

```
26.5623
```

```
>> mag^2
```

```
ans =
```

```
0.2000
```


$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

20 percent! This is  $|\Gamma|^2$



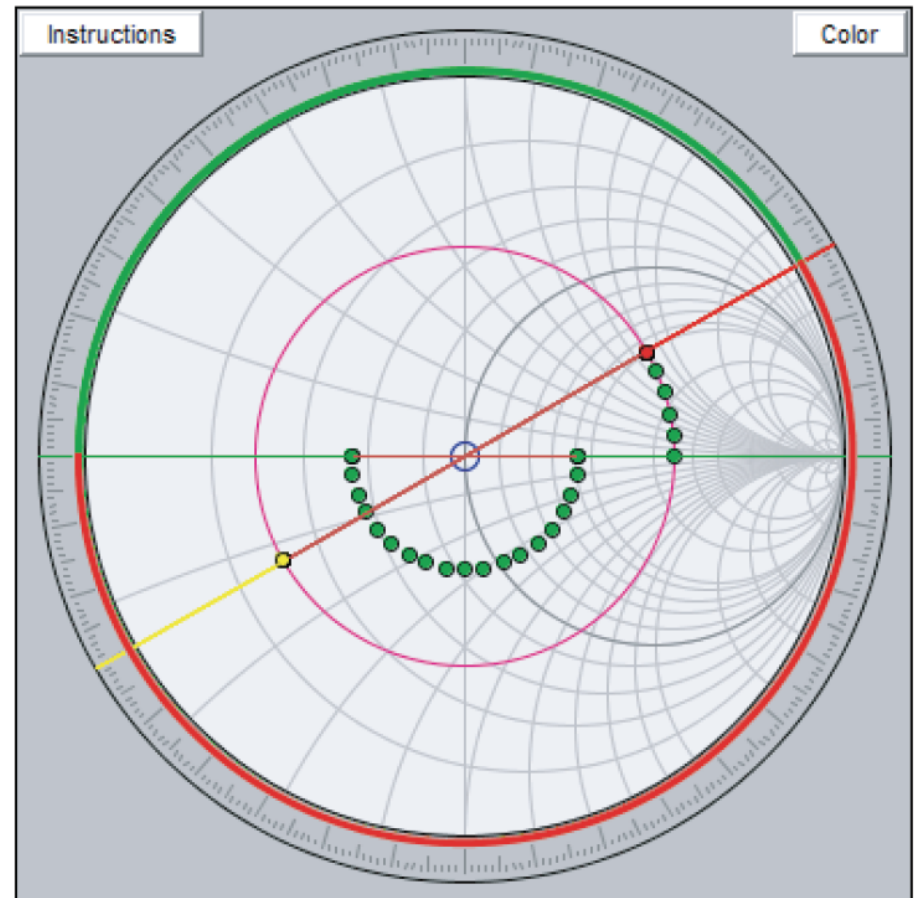
# The Smith Chart

- Developed in 1939 by P. W. Smith as a graphical tool to analyze and design transmission-line circuits
- Today, it is used to characterize the performance of microwave circuits



# Complex Plane

$$\Gamma = |\Gamma|e^{j\theta_r} = \Gamma_r + j\Gamma_i$$

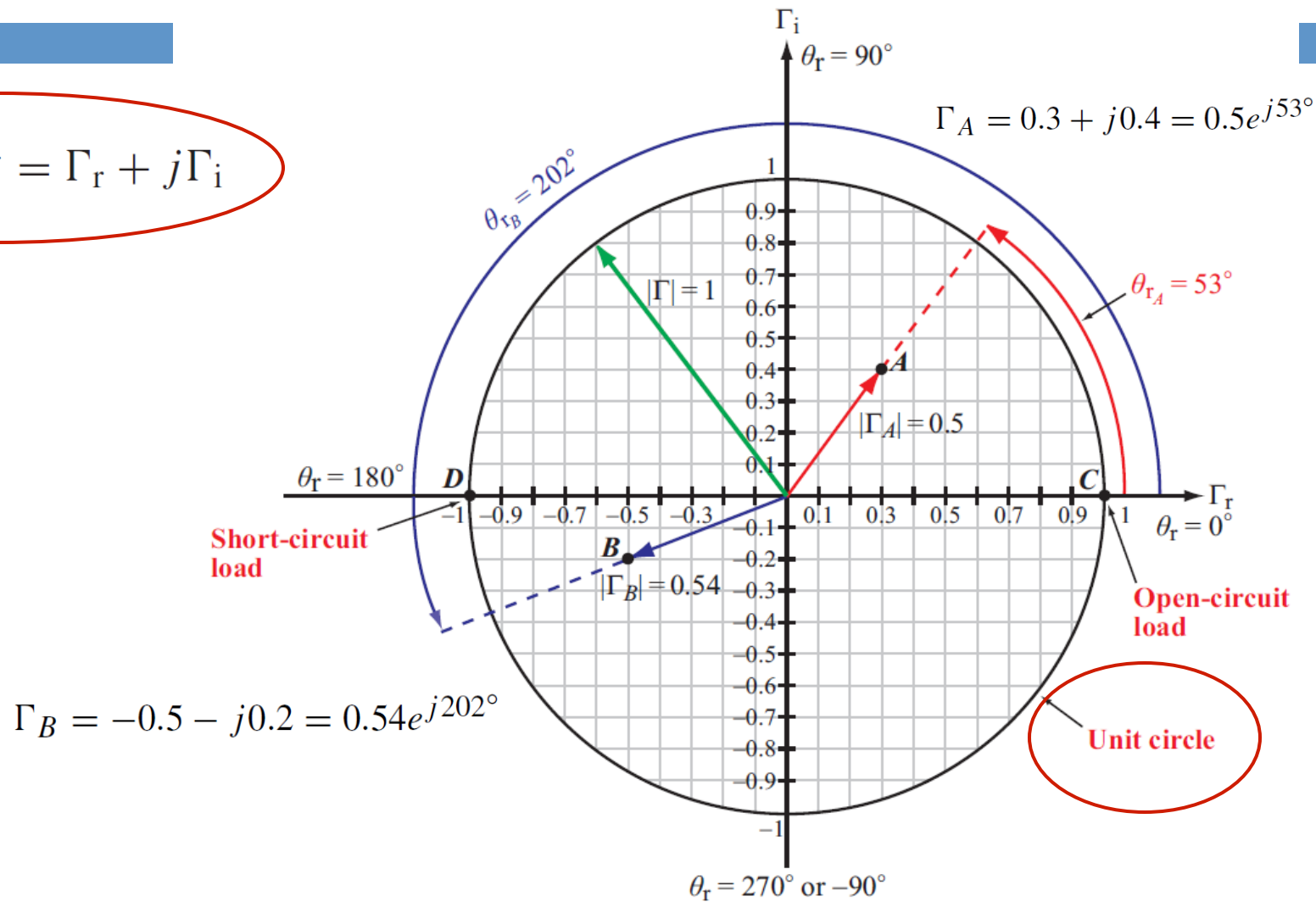

# Smith Chart Parametric Equations

$$\Gamma = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} = \frac{z_L - 1}{z_L + 1}$$

$$z_L = \frac{1 + \Gamma}{1 - \Gamma} \quad (2.112)$$

$$z_L = r_L + jx_L.$$

$$r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$x_L = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

Equation for a circle

$$\left(\Gamma_r - \frac{r_L}{1 + r_L}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1 + r_L}\right)^2 \quad (2.116)$$

Parametric Equation!

For a given Coef. Of Reflection various load combinations can be considered. These combinations can be represented by different circuits!

Smith Chart help us see these variations!

$$r_L + jx_L = \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i}$$

$$\Gamma = |\Gamma|e^{j\theta_r} = \Gamma_r + j\Gamma_i$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L}\right)^2 = \left(\frac{1}{x_L}\right)^2, \quad (2.118)$$

# Smith Chart Parametric Equations

$$\left(\Gamma_r - \frac{r_L}{1+r_L}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r_L}\right)^2. \quad (2.116)$$

$r_L$  circles

$r_L$  circles are contained inside the unit circle

Each node on the chart will tell us about the load characteristics and coef. of ref. of the line!

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L}\right)^2 = \left(\frac{1}{x_L}\right)^2, \quad (2.118)$$

$x_L$  circles

Imag. Part of ZL

Only parts of the  $x_L$  circles are contained within the unit circle


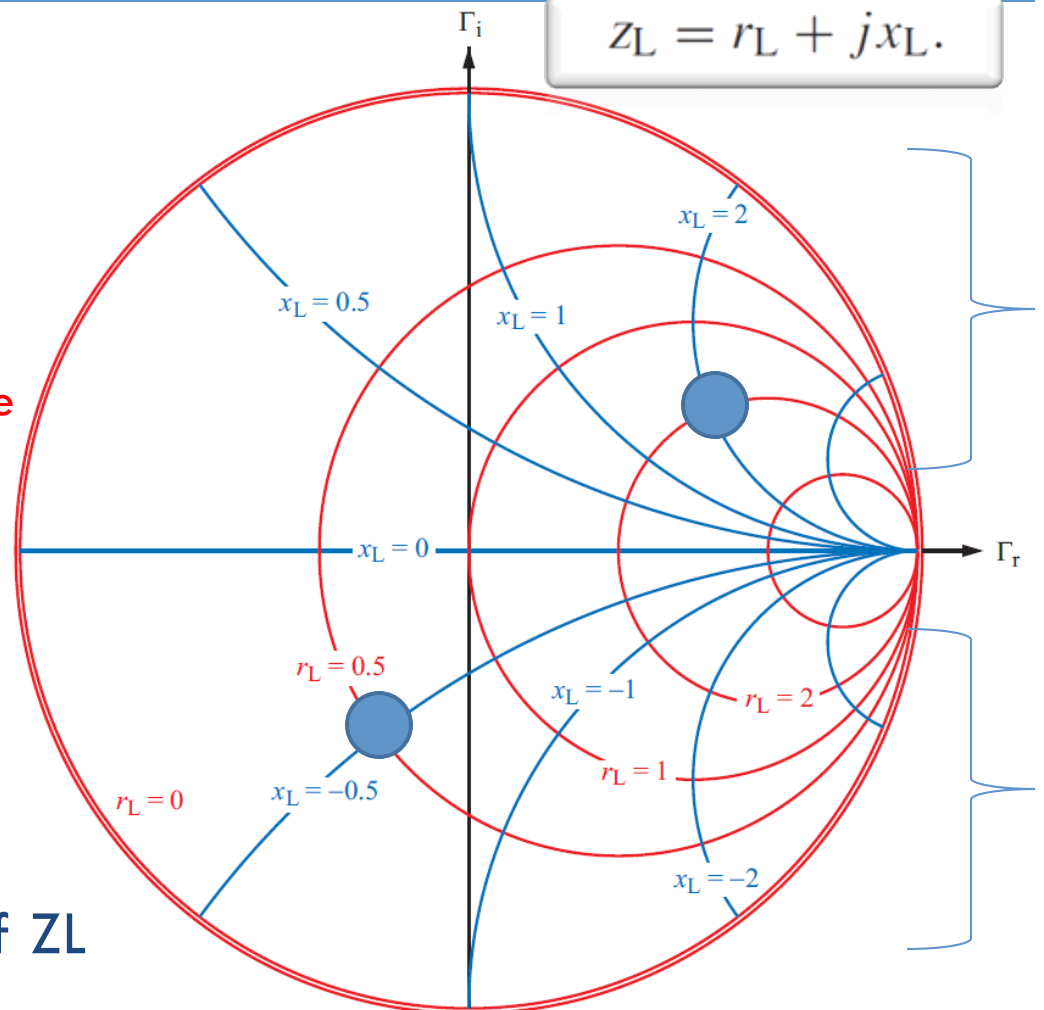


Figure 2-25: Families of  $r_L$  and  $x_L$  circles within the domain  $|\Gamma| \leq 1$ .

# Complete Smith Chart

$$Z_L = r_L + jx_L.$$

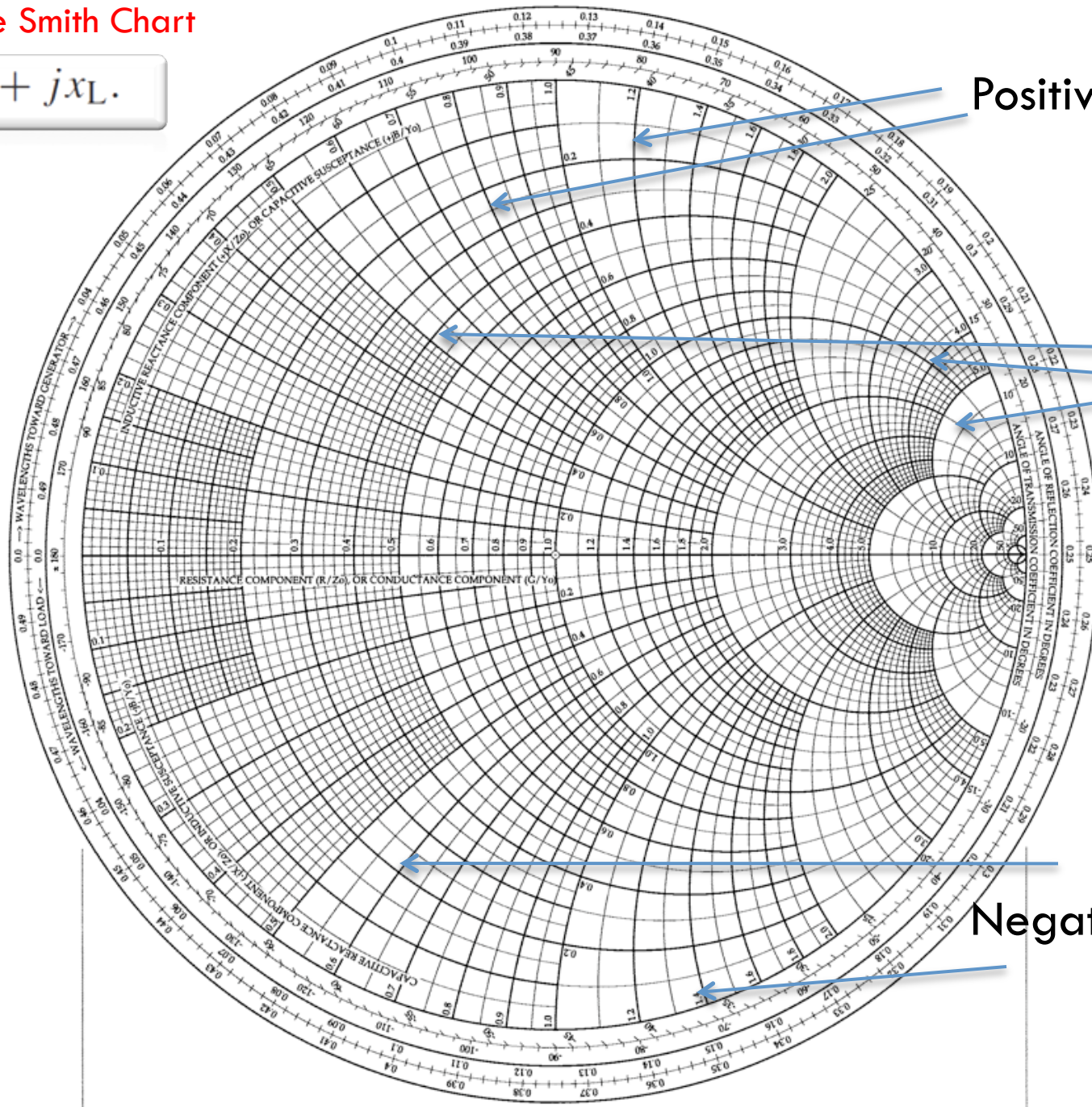

Positive  $x_L$  Circles



$r_L$  Circles

Negative  $x_L$  Circles

# Basic Rules

- Given ZL find the coefficient of reflection (COR)
  - ▣ Find ZL on the chart (Pt. P) [1] – Normalized Load
  - ▣ Extend it and find the angle of COR [3]
  - ▣ Use ruler to measure find OP/OR ; OR is simply unity circle - This will be the magnitude of COR
- Find dmin and dmax
  - ▣ From the extended OP to
- Find VSWR (or S)
  - ▣ Draw a circle with radius of ZL (OP)
  - ▣ Find Pmin and Pmax=S along the circle (where |Vmin| and |Vmax| are)
- Input impedance  $Z_d = Z_{in}$ 
  - ▣ Find S on the chart (OP)
  - ▣ Extend ZL all the way to hit a point on the outer circle
  - ▣ Then move away in the direction of WL TOWARD GENERATOR by  $d = x\lambda$
  - ▣ Draw a line toward the center of the circle
    - The intersection of the S circle and this line will be the input load ( $Z_{in}$ )

ZL/Zo  
COR  
dmin/dmax  
SWR  
zin & Zin  
yin & Yin




# Basic Rules

- Input impedance  $Y_d = Y_{in}$  (admittance)
  - ▣ Once  $z_{in}$  (normalized

$Z_L/Z_o$   
COR  
 $d_{min}/d_{max}$   
SWR  
 $z_{in}$  &  $Z_{in}$   
 $y_{in}$  &  $Y_{in}$


# Reflection coefficient at the load

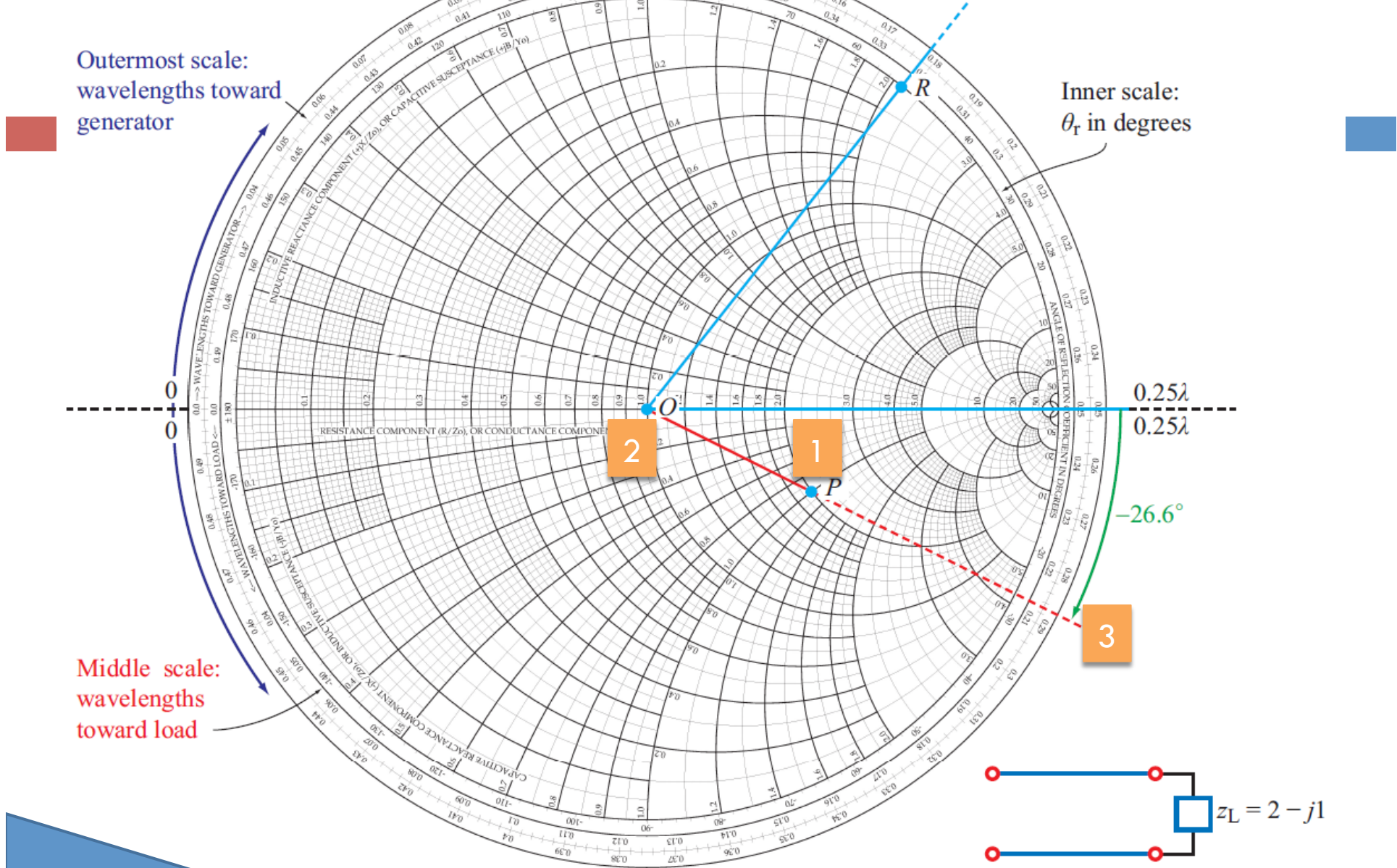

## Example 1

presents a normalized load impedance  $z_L = 2 - j1$ . The reflection coefficient has a magnitude  $|\Gamma| = 0.484$  and an angle  $\theta_r = -26.6^\circ$ . Point  $R$  is an arbitrary point on the  $r_L = 0$  circle (which also is the  $|\Gamma| = 1$  circle).


# Input Impedance

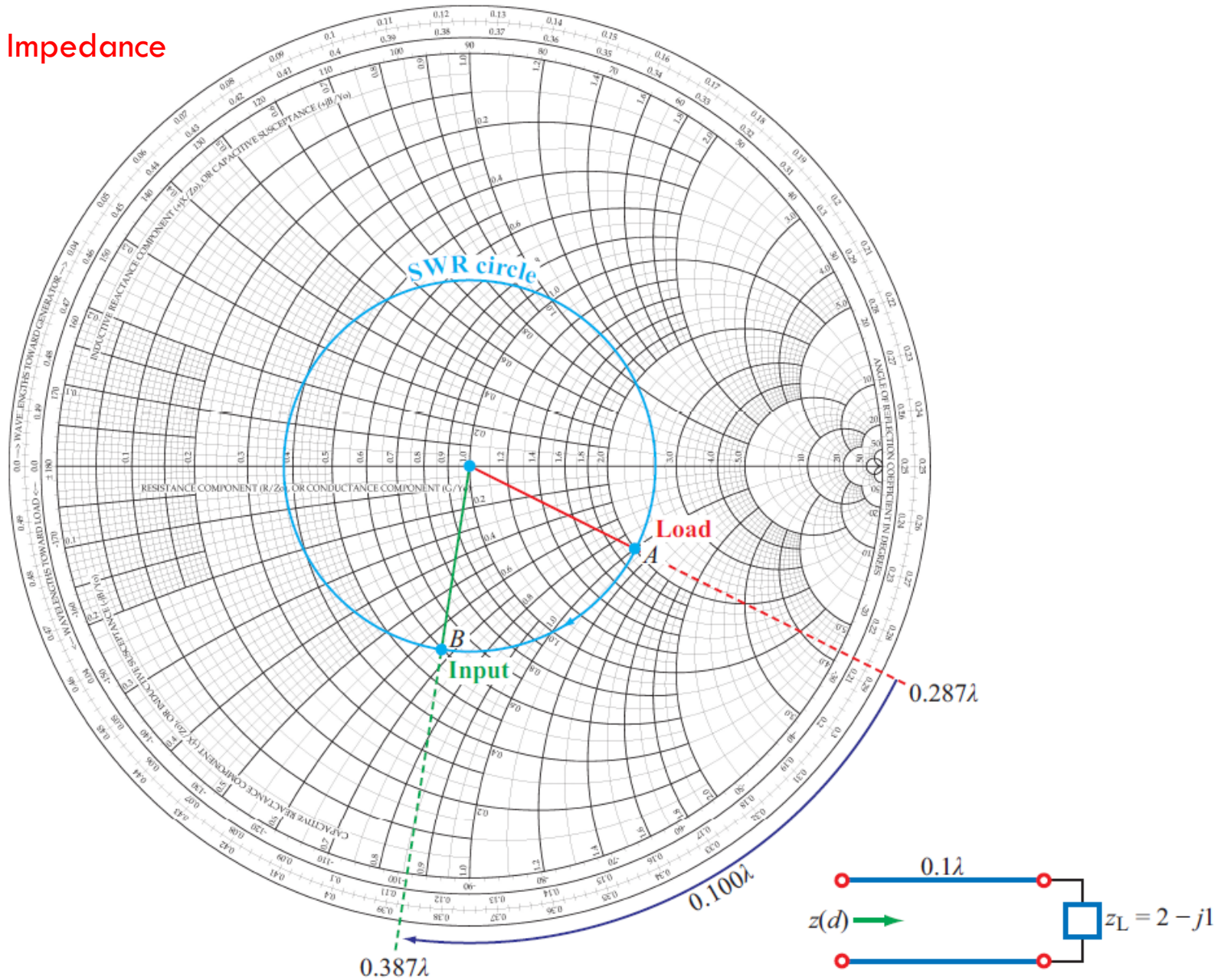

**Figure 2-27:** Point A represents a normalized load  $z_L = 2 - j1$  at  $0.287\lambda$  on the WTG scale. Point B represents the line input at  $d = 0.1\lambda$  from the load. At B,  $z(d) = 0.6 - j0.66$ .

## Maxima and Minima



$S$  is numerically equal to the value of  $r_0$  at  $P_{\max}$ , the point at which the SWR circle intersects the real  $\Gamma$  axis to the right of the chart's center.

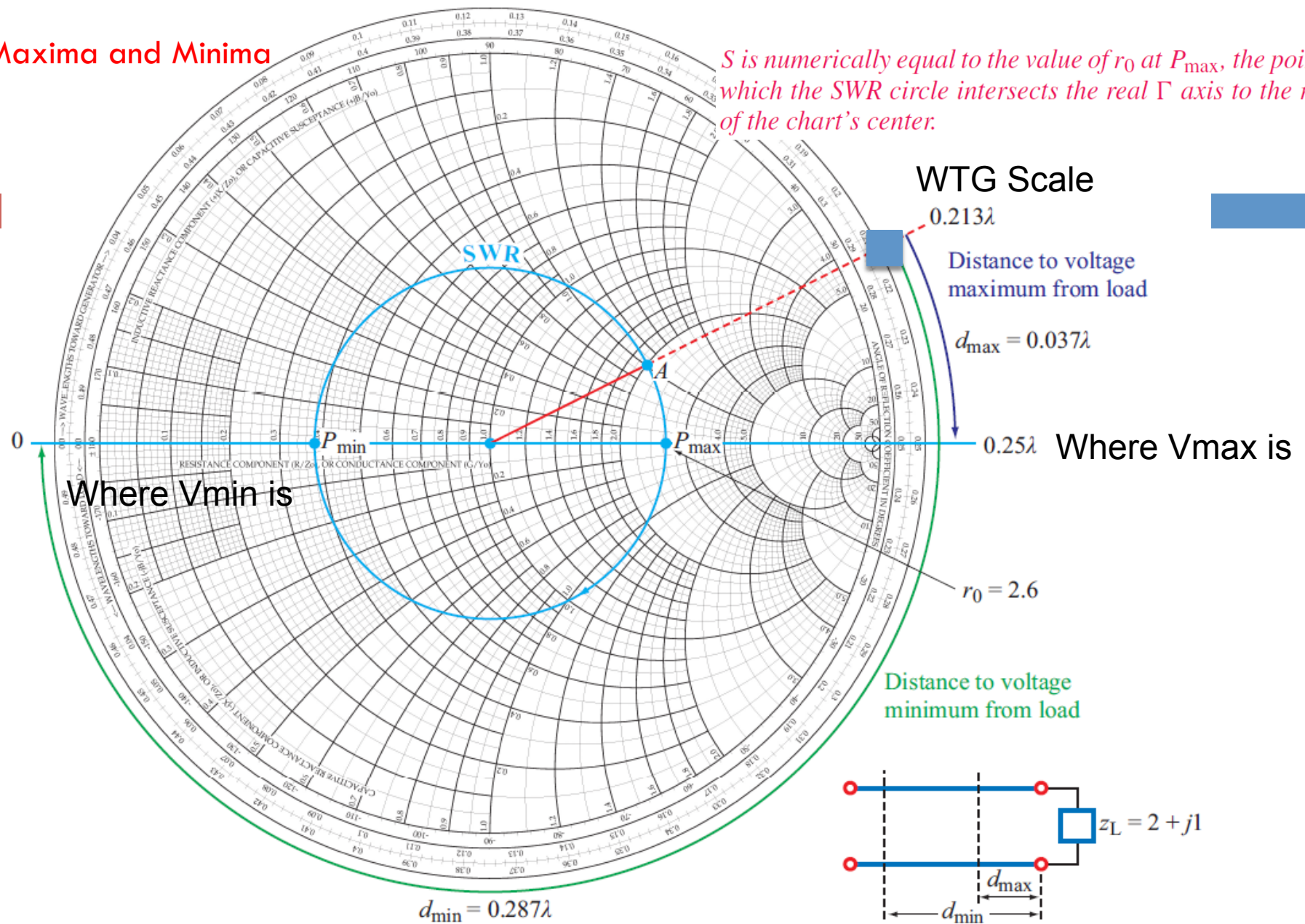

**Figure 2-28:** Point A represents a normalized load with  $z_L = 2 + j1$ . The standing wave ratio is  $S = 2.6$  (at  $P_{\max}$ ), the distance between the load and the first voltage maximum is  $d_{\max} = (0.25 - 0.213)\lambda = 0.037\lambda$ , and the distance between the load and the first voltage minimum is  $d_{\min} = (0.037 + 0.25)\lambda = 0.287\lambda$ .
 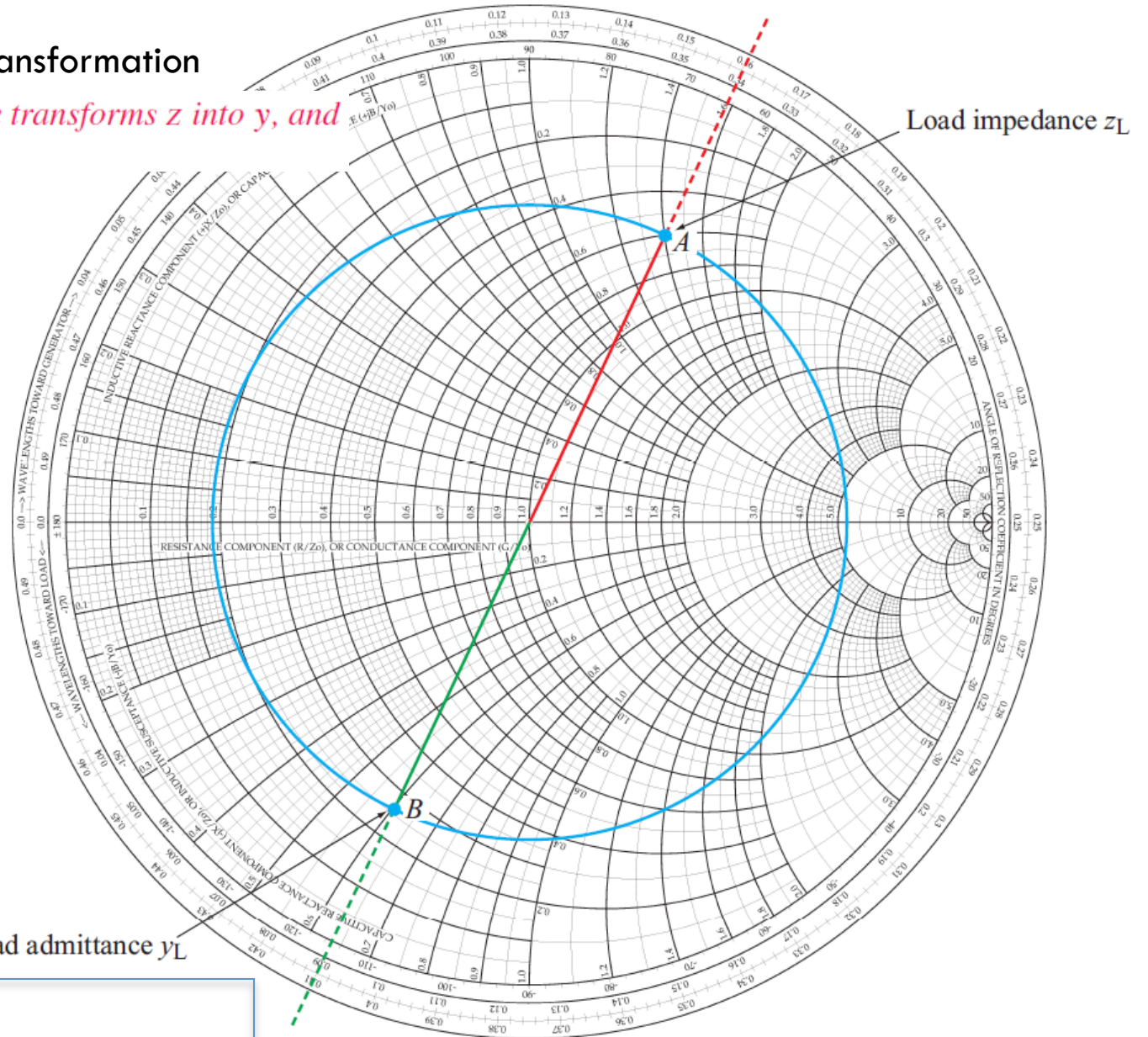
# Impedance to Admittance Transformation

Rotation by  $\lambda/4$  on the SWR circle transforms  $z$  into  $y$ , and vice versa.



## Example 2-11: Smith Chart Calculations

$$(3.3)\lambda \rightarrow (0.3)\lambda$$

A  $50\text{-}\Omega$  lossless transmission line of length  $3.3\lambda$  is terminated by a load impedance  $Z_L = (25 + j50)\ \Omega$ .

$$z_L = \frac{Z_L}{Z_0} = \frac{25 + j50}{50} = 0.5 + j1$$

(c)

$$d_{\max} = (0.25 - 0.135)\lambda = 0.115\lambda$$

$$d_{\min} = (0.5 - 0.135)\lambda = 0.365\lambda$$


(d)

The generator is at  $(0.135 + 0.3)\lambda = 0.435\lambda$  – this is pt. D


→  $Z_{in}$  normalized is the intersection of D and S

$$z_{in} = 0.28 - j0.40$$

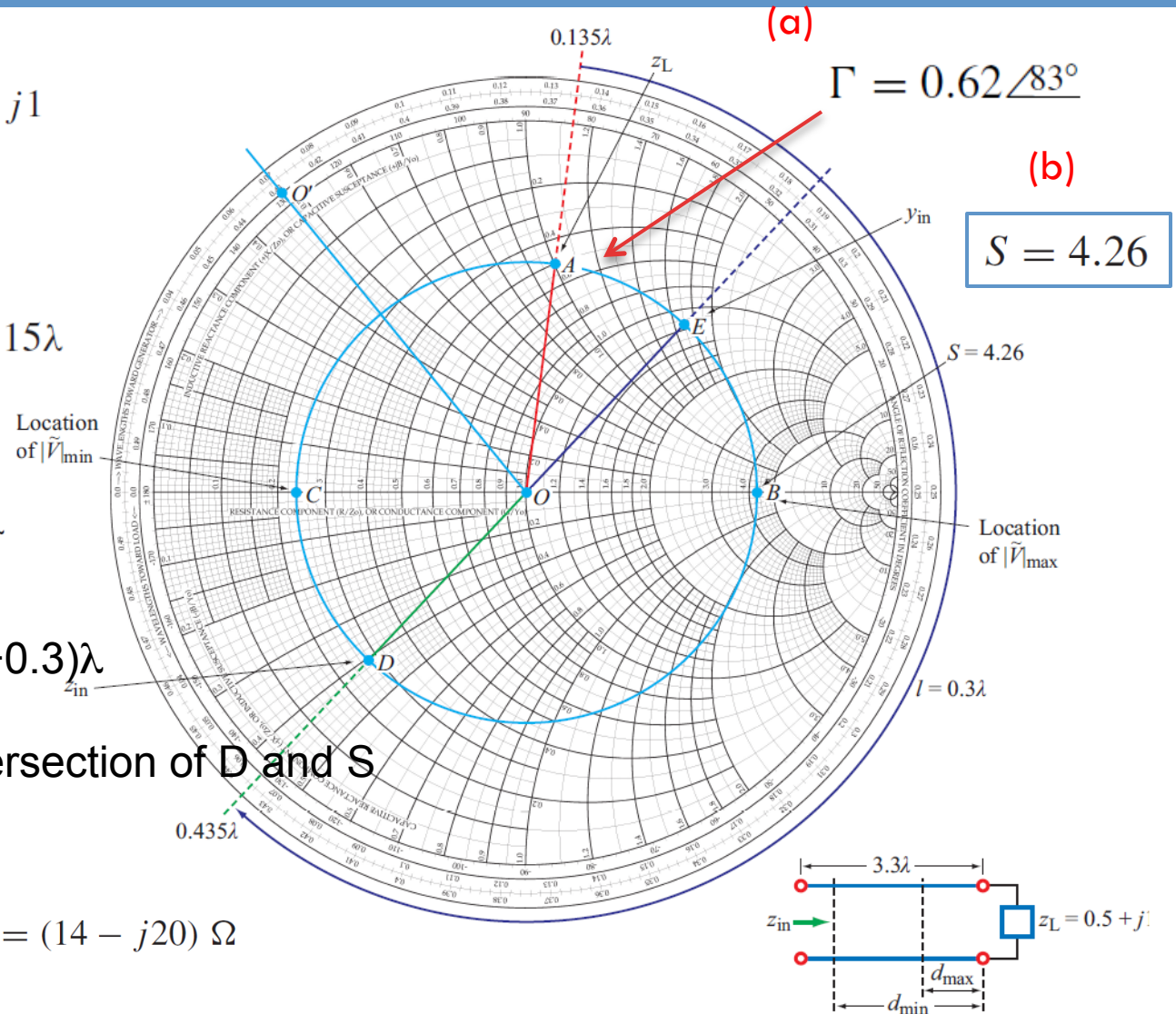
$$Z_{in} = z_{in} Z_0 = (0.28 - j0.40)50 = (14 - j20)\ \Omega$$



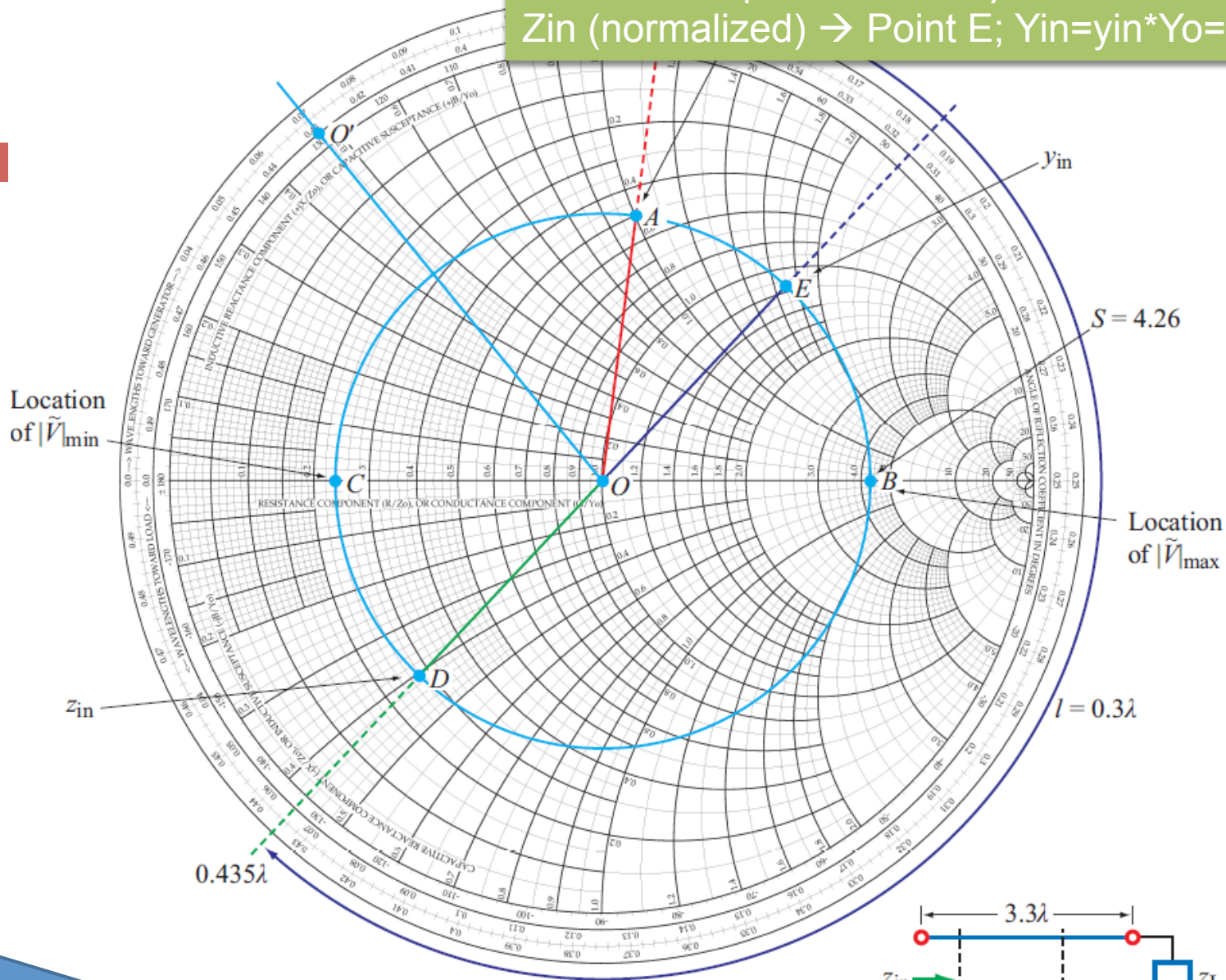Normalized input admittance  $y_{in}$  is 0.25 away from  $Z_{in}$  (normalized)  $\rightarrow$  Point E;  $Y_{in} = y_{in} * Y_o = y_{in} / Z_o$



### Example 3

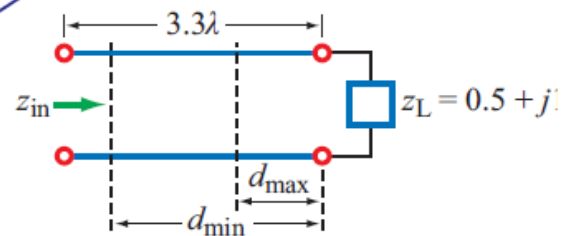

## Example 2-12: Determining $Z_L$ Using the Smith Chart

Given:

$$S = 3$$

$$Z_0 = 50 \Omega$$

first voltage min @ 5 cm from load


Distance between adjacent minima = 20 cm

Determine:  $Z_L$

$$d_{\min} = \frac{5}{40} = 0.125\lambda$$

$$z_L = 0.6 - j0.8$$

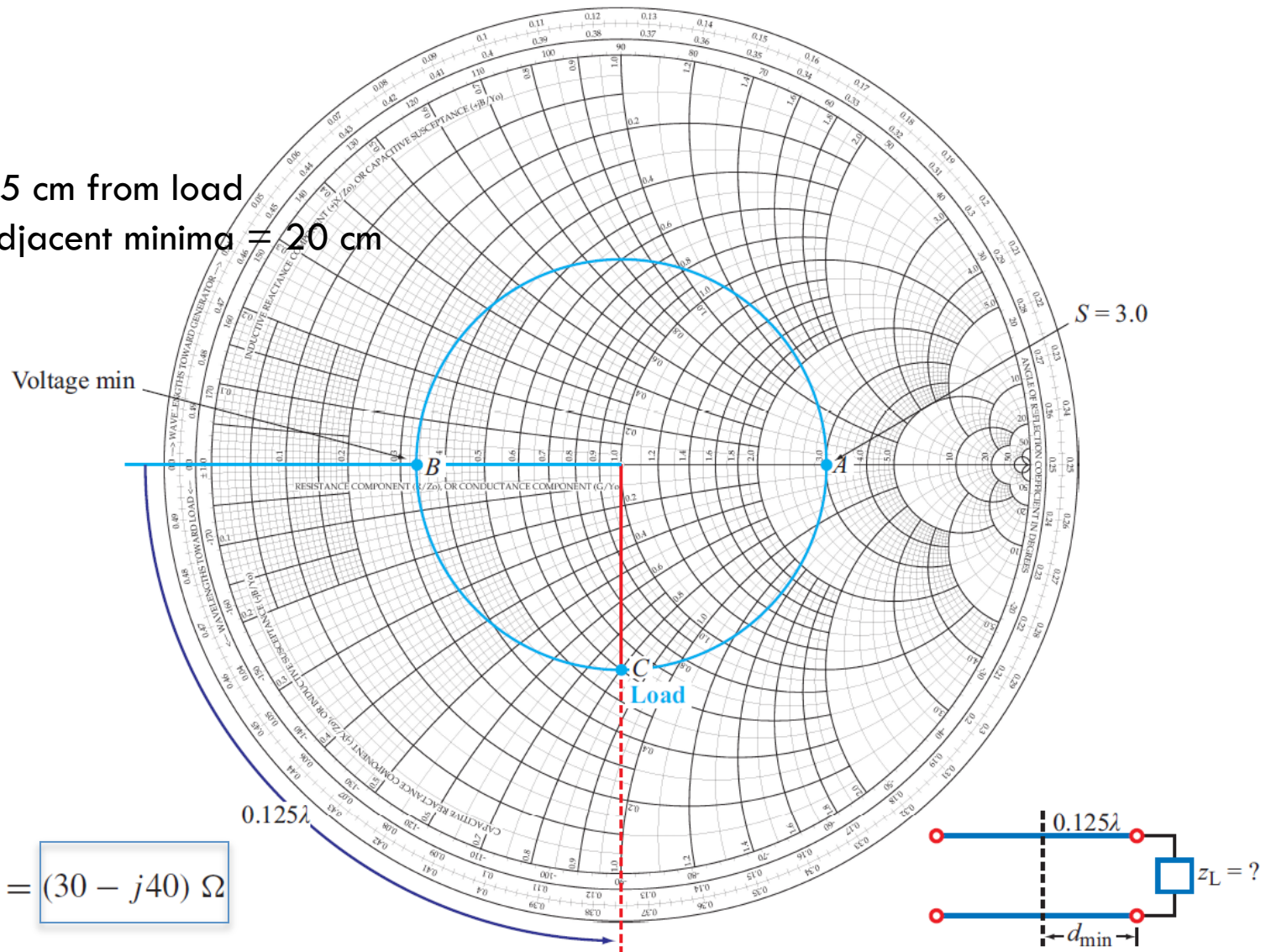
$$Z_L = 50(0.6 - j0.8) = (30 - j40) \Omega$$





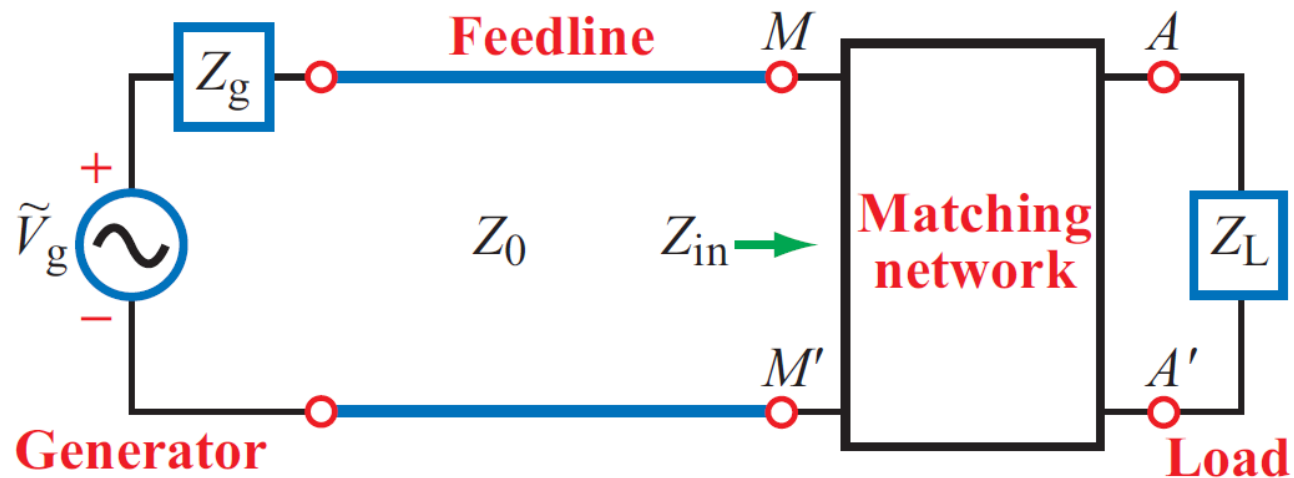
# Matching Networks


*The purpose of the matching network is to eliminate reflections at terminals  $MM'$  for waves incident from the source. Even though multiple reflections may occur between  $AA'$  and  $MM'$ , only a forward traveling wave exists on the feedline.*




# Examples of Matching Networks

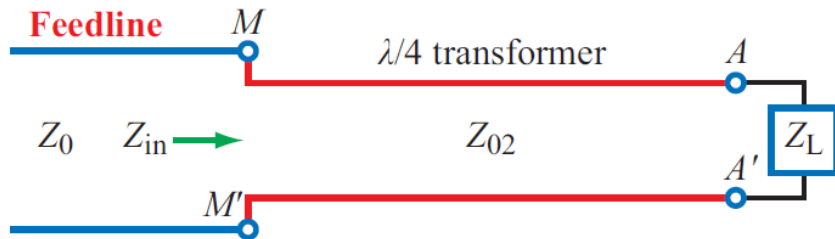

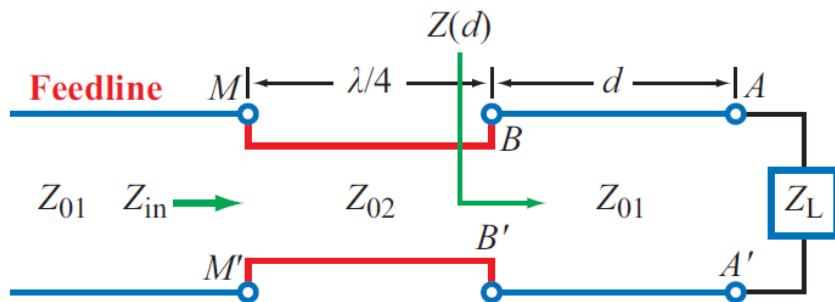
(a) In-series  $\lambda/4$  transformer inserted at  $AA'$



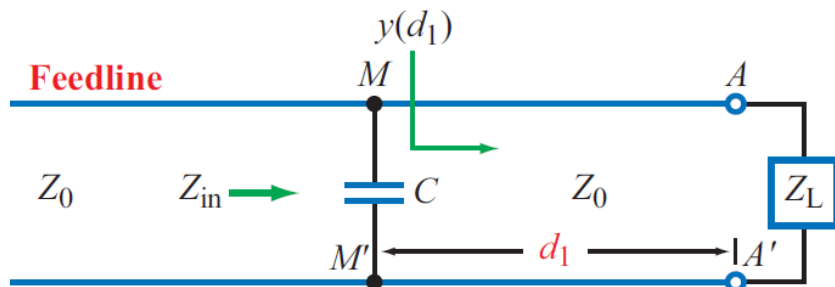
(b) In-series  $\lambda/4$  transformer inserted at  $d = d_{max}$  or  $d = d_{min}$



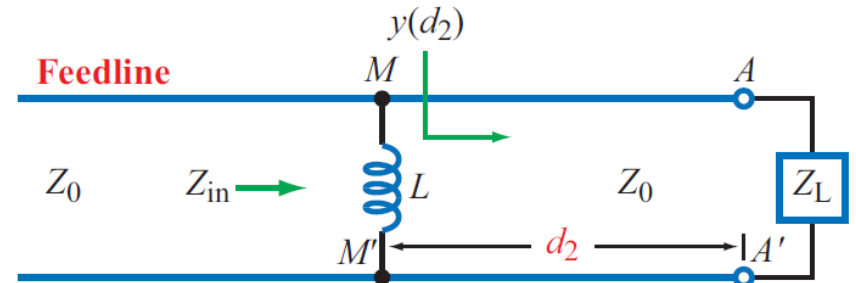(c) In-parallel insertion of capacitor at distance  $d_1$



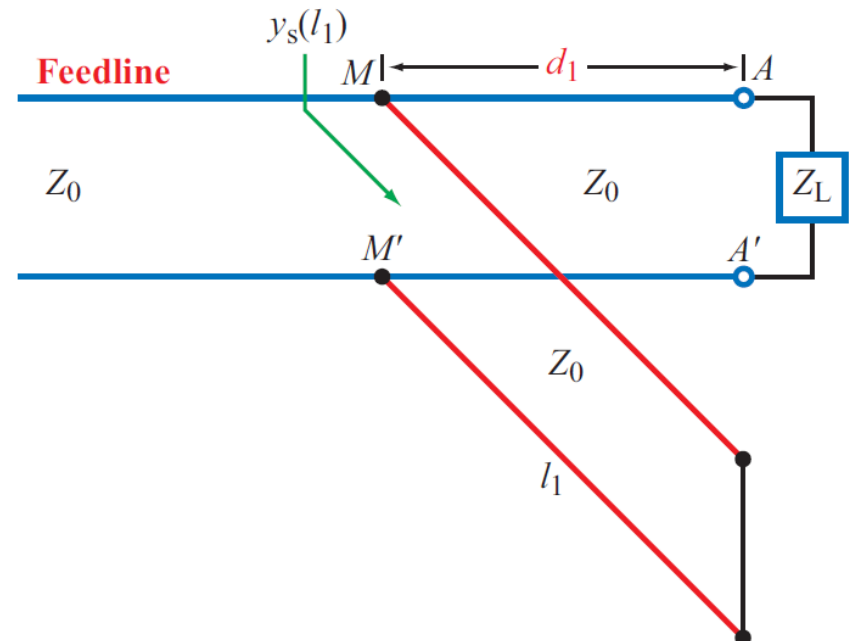
(d) In-parallel insertion of inductor at distance  $d_2$



(e) In-parallel insertion of a short-circuited stub

# Lumped-Element Matching

Choose  $d$  and  $Y_s$  to achieve a match at  $MM'$

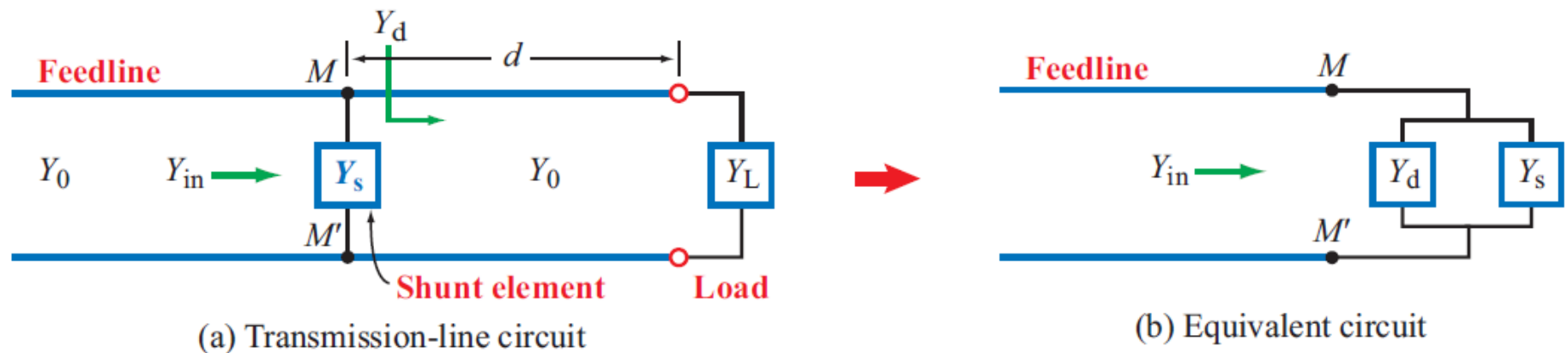

**Figure 2-34:** Inserting a reactive element with admittance  $Y_s$  at  $MM'$  modifies  $Y_d$  to  $Y_{in}$ .

$$y_{in} = g_d + j(b_d + b_s). \quad (2.140)$$

$$Y_{in} = Y_d + Y_s$$

$$\begin{aligned} Y_{in} &= (G_d + jB_d) + jB_s \\ &= G_d + j(B_d + B_s). \end{aligned}$$

To achieve a matched condition at  $MM'$ , it is necessary that  $y_{in} = 1 + j0$ , which translates into two specific conditions, namely

$$g_d = 1 \quad (\text{real-part condition}), \quad (2.141a)$$

$$b_s = -b_d \quad (\text{imaginary-part condition}). \quad (2.141b)$$

### Example 2-13: Lumped Element

A load impedance  $Z_L = 25 - j50 \Omega$  is connected to a  $50\text{-}\Omega$  transmission line. Insert a shunt element to eliminate reflections towards the sending end of the line. Specify the insert location  $d$  (in wavelengths), the type of element, and its value, given that  $f = 100 \text{ MHz}$ .

$$z_L = \frac{Z_L}{Z_0} = \frac{25 - j50}{50} = 0.5 - j1$$

$$y_L = 0.4 + j0.8$$

**Solution for Point C (Fig. 2-36):** At C,

$$y_d = 1 + j1.58,$$

which is located at  $0.178\lambda$  on the WTG scale. The distance between points B and C is


$$d_1 = (0.178 - 0.115)\lambda = 0.063\lambda.$$


we need  $y_{in} = 1 + j0$ . Thus,

$$1 + j0 = y_s + 1 + j1.58,$$

or

$$y_s = -j1.58.$$

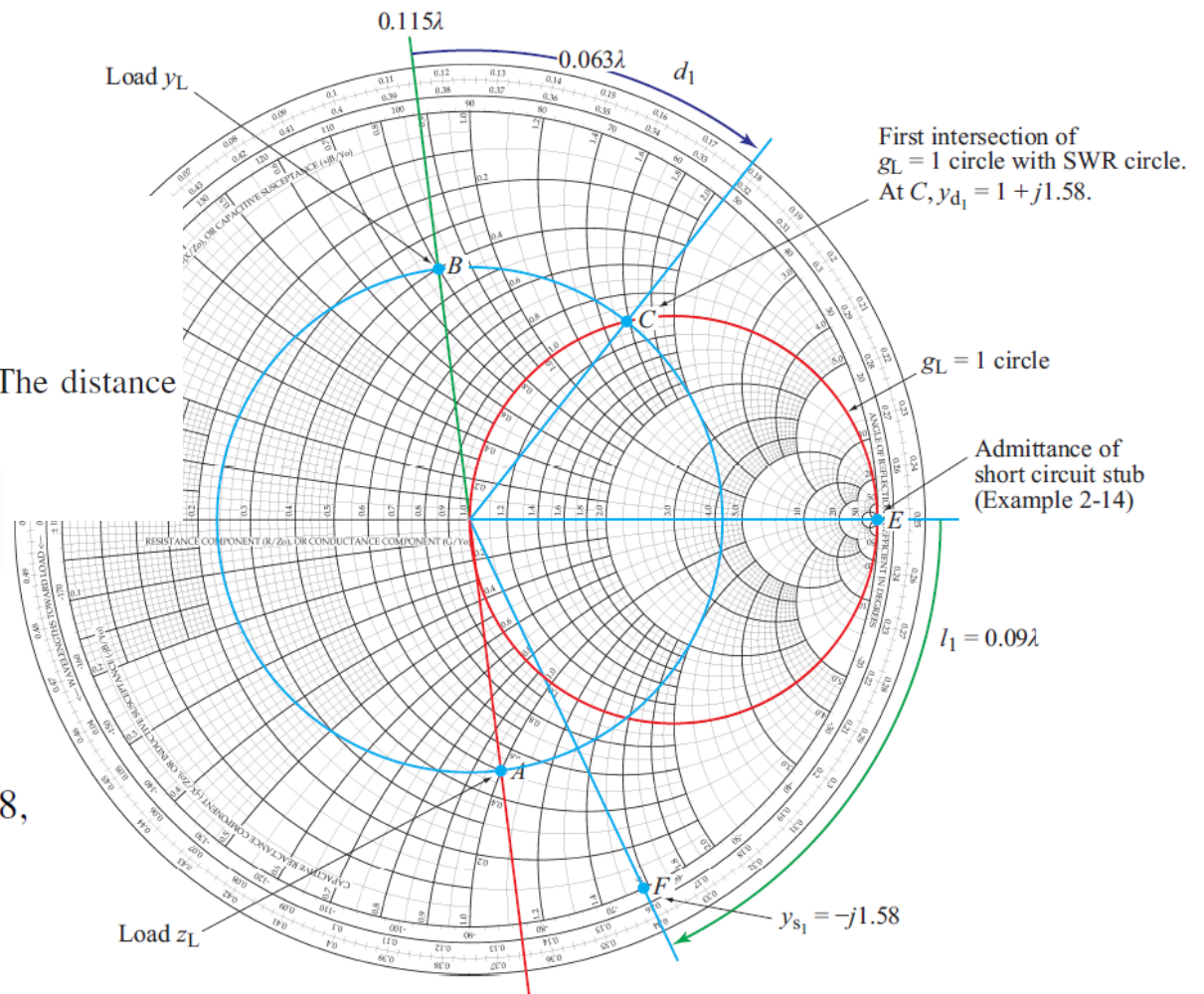

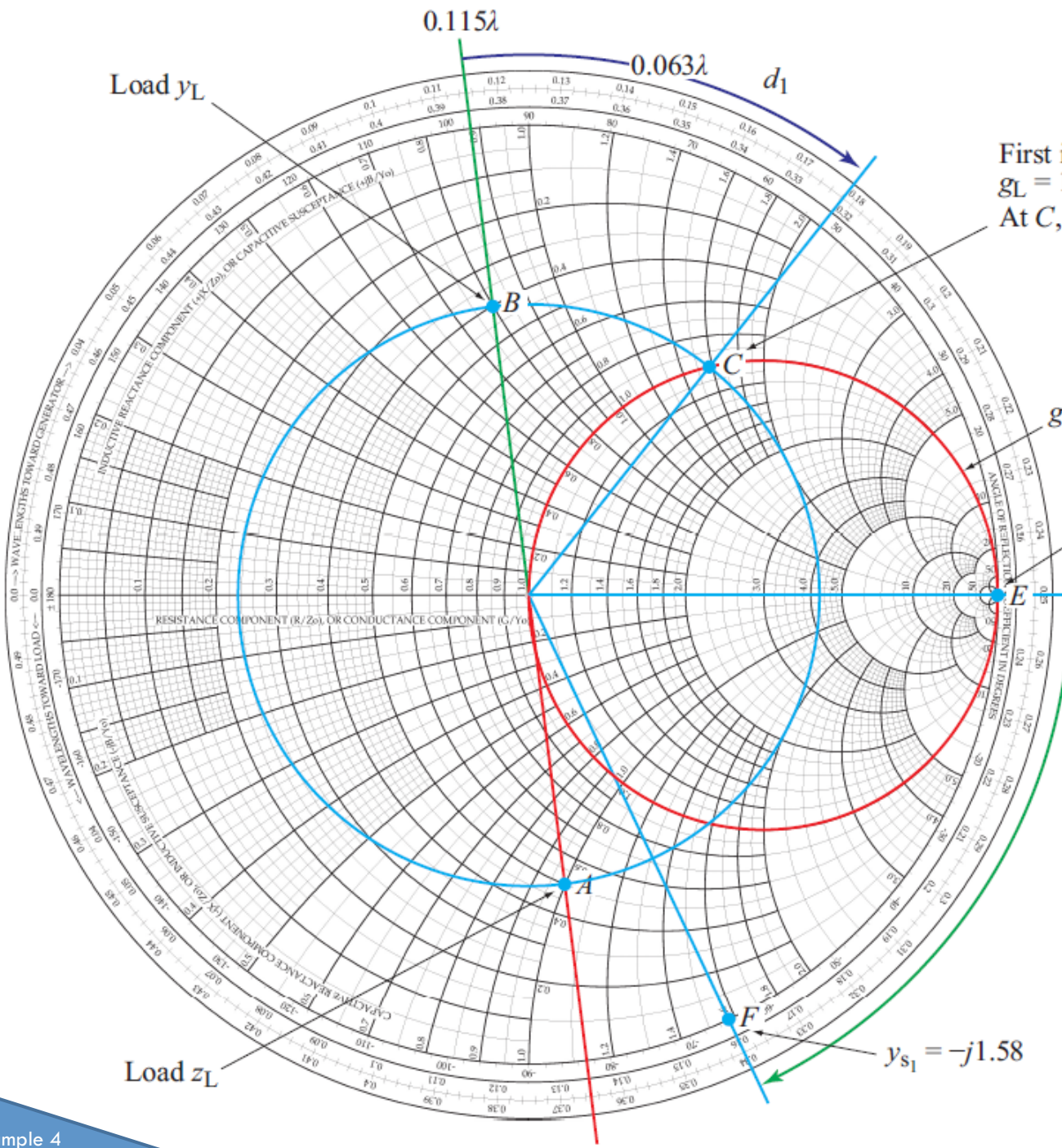

Load  $y_L$

$0.115\lambda$

$0.063\lambda$

$d_1$

First intersection of  $g_L = 1$  circle with SWR circle.  
At C,  $y_{d1} = 1 + j1.58$ .

$g_L = 1$  circle

Admittance of short circuit stub (Example 2-14)

$l_1 = 0.09\lambda$

Load  $z_L$

$y_{s1} = -j1.58$

Example 4

**Example 2-13: Lumped Element Cont.**

A load impedance  $Z_L = 25 - j50 \Omega$  is connected to a  $50\text{-}\Omega$  transmission line. Insert a shunt element to eliminate reflections towards the sending end of the line. Specify the insert location  $d$  (in wavelengths), the type of element, and its value, given that  $f = 100 \text{ MHz}$ .

$$z_L = \frac{Z_L}{Z_0} = \frac{25 - j50}{50} = 0.5 - j1$$

$$y_L = 0.4 + j0.8$$

The corresponding impedance of the lumped element is

$$Z_{s1} = \frac{1}{Y_{s1}} = \frac{1}{y_{s1}Y_0} = \frac{Z_0}{jb_{s1}} = \frac{Z_0}{-j1.58} = \frac{jZ_0}{1.58} = j31.62 \Omega.$$

Since the value of  $Z_{s1}$  is positive, the element to be inserted should be an inductor and its value should be

$$L = \frac{31.62}{\omega} = \frac{31.62}{2\pi \times 10^8} = 50 \text{ nH.}$$

**Solution for Point C (Fig. 2-36):** At  $C$ ,

$$y_d = 1 + j1.58,$$

which is located at  $0.178\lambda$  on the WTG scale. The distance between points  $B$  and  $C$  is

$$d_1 = (0.178 - 0.115)\lambda = 0.063\lambda.$$

we need  $y_{in} = 1 + j0$ . Thus,


$$1 + j0 = y_s + 1 + j1.58,$$

or


$$y_s = -j1.58.$$
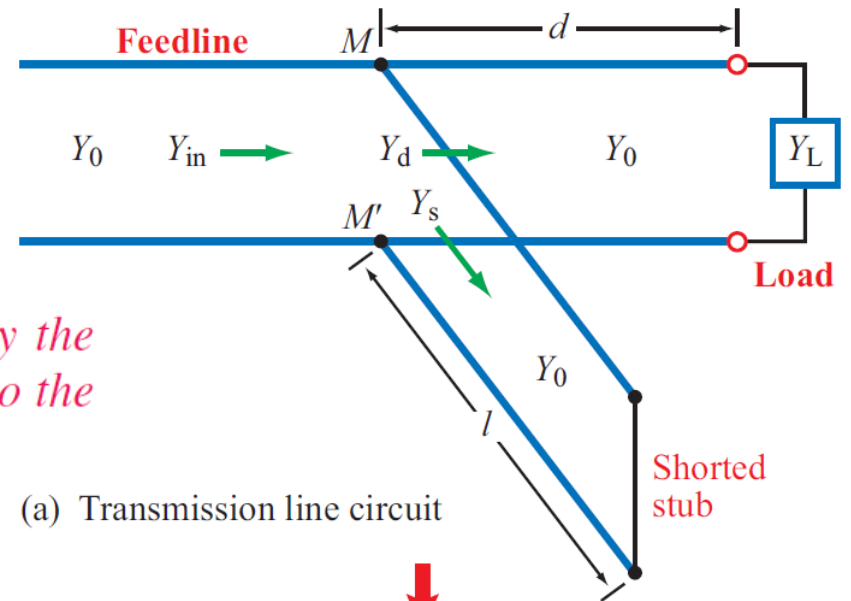
# Single-Stub Matching

*The required two degrees of freedom are provided by the length  $l$  of the stub and the distance  $d$  from the load to the stub position.*



(a) Transmission line circuit

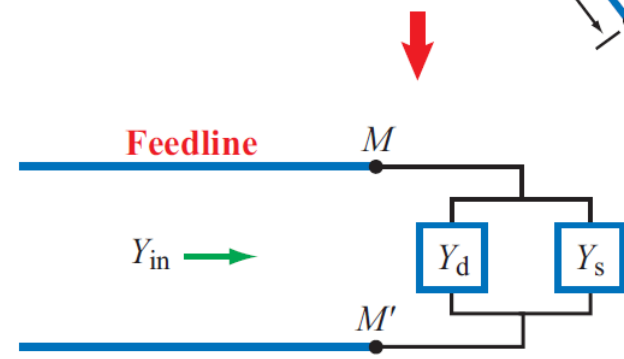

(b) Equivalent circuit




### Example 2-14: Single-Stub Matching

Repeat Example 2-13, but use a shorted stub (instead of a lumped element) to match the load impedance  $Z_L = (25 - j50) \Omega$  to the  $50\text{-}\Omega$  transmission line.

**Solution:** In Example 2-13, we demonstrated that the load can be matched to the line via either of two solutions:

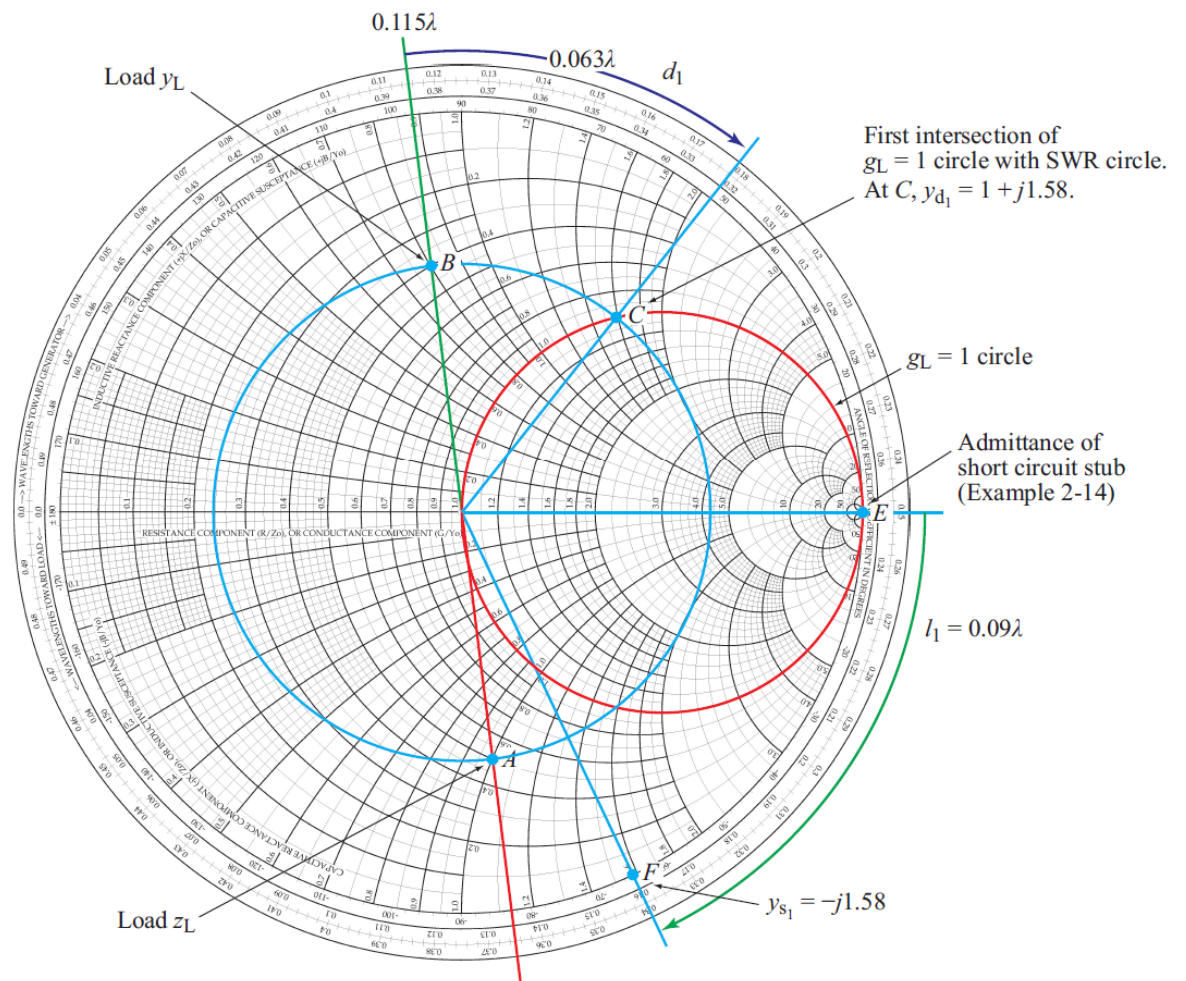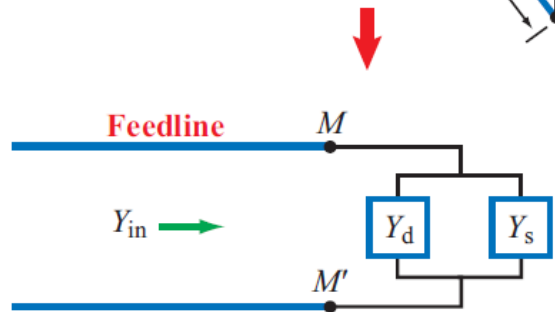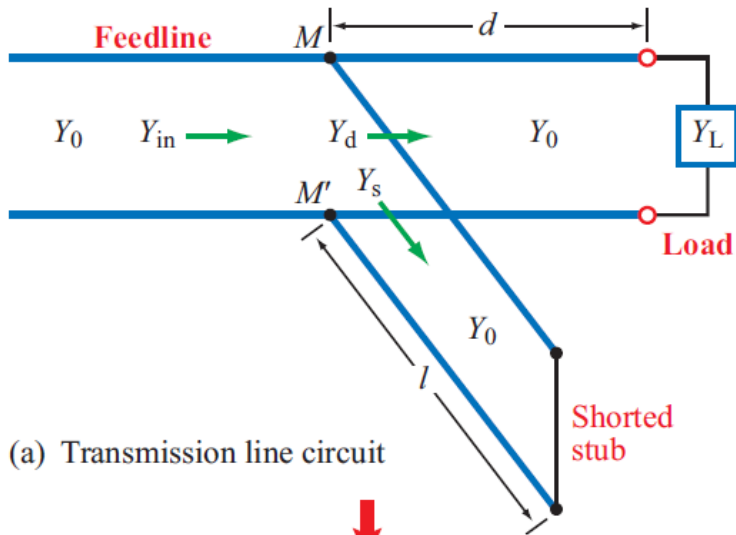- (1)  $d_1 = 0.063\lambda$ , and  $y_{s1} = jb_{s1} = -j1.58$ ,
- (2)  $d_2 = 0.207\lambda$ , and  $y_{s2} = jb_{s2} = j1.58$ .


$$l_1 = (0.34 - 0.25)\lambda = 0.09\lambda$$





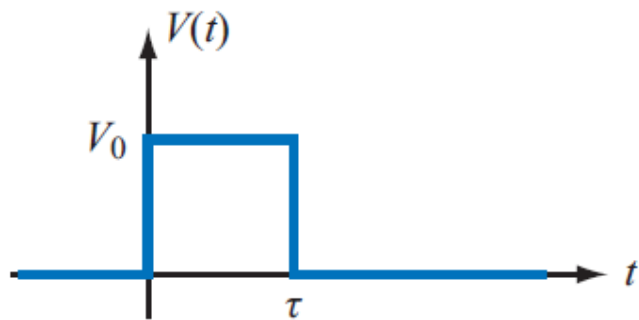
# Transients

*The transient response of a voltage pulse on a transmission line is a time record of its back and forth travel between the sending and receiving ends of the line, taking into account all the multiple reflections (echoes) at both ends.*




(a) Pulse of duration  $\tau$

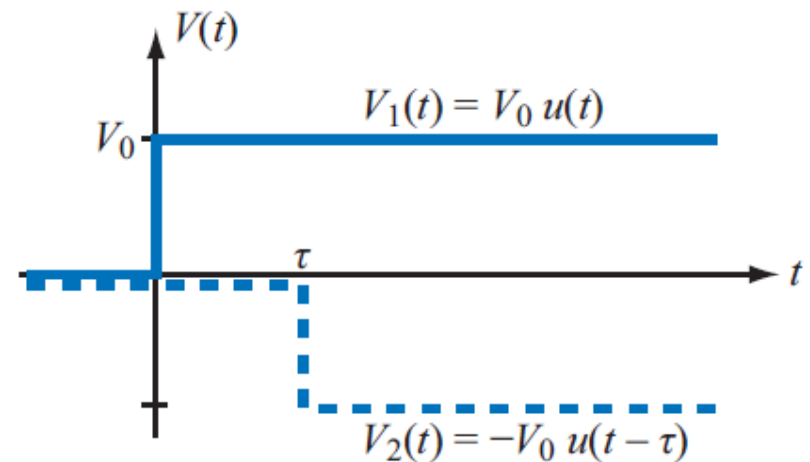

(b)  $V(t) = V_1(t) + V_2(t)$

Rectangular pulse is equivalent to the sum of two step functions

# Transient Response

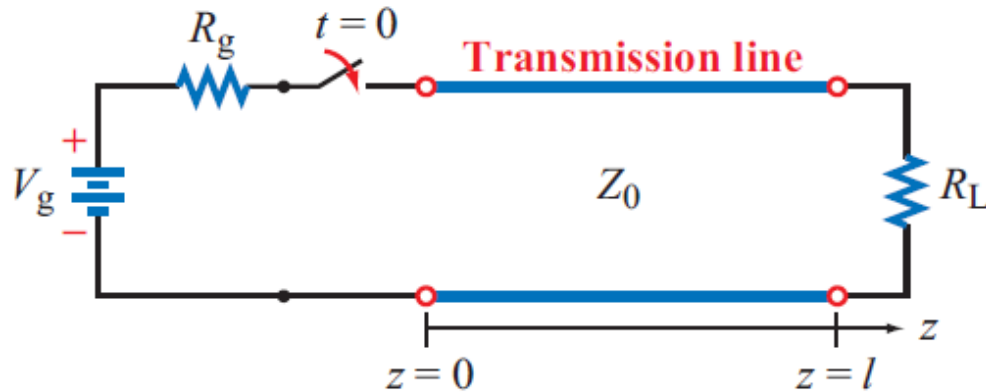

(a) Transmission-line circuit

Initial current and voltage

$$I_1^+ = \frac{V_g}{R_g + Z_0},$$

$$V_1^+ = I_1^+ Z_0 = \frac{V_g Z_0}{R_g + Z_0}$$


Reflection at the load

$$V_1^- = \Gamma_L V_1^+,$$

Load reflection coefficient  $\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}$


Second transient
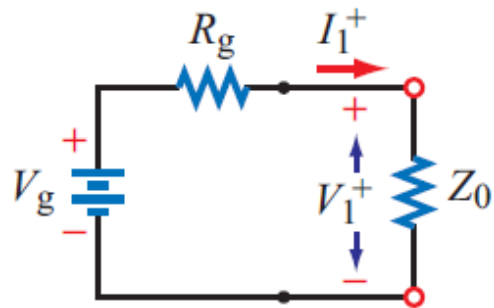
$$V_2^+ = \Gamma_g V_1^- = \Gamma_g \Gamma_L V_1^+$$



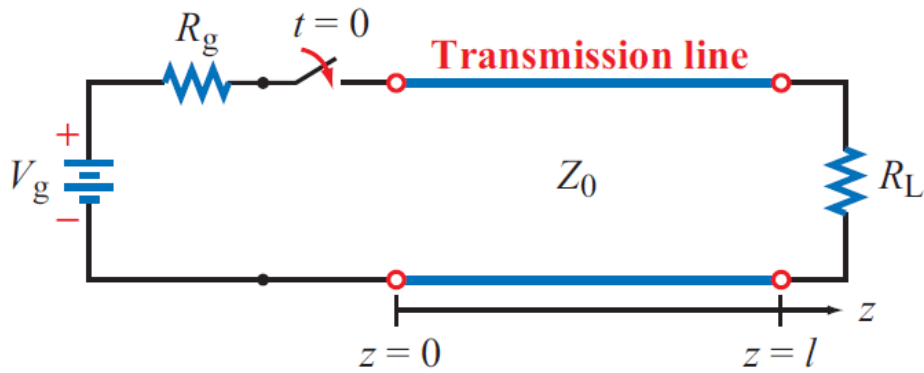(b) Equivalent circuit at  $t = 0^+$


Generator reflection coefficient  $\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0}$




(a) Transmission-line circuit
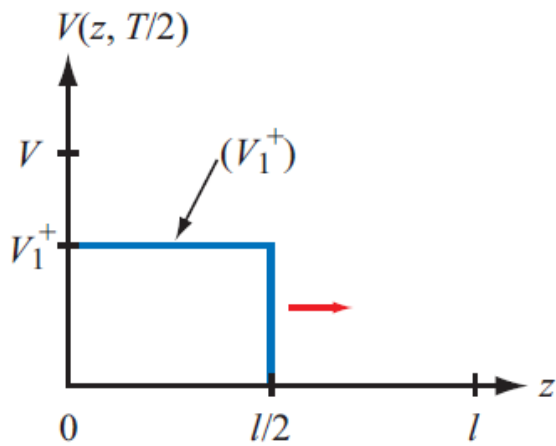
## Voltage Wave


$T = l/u_p$  is the time it takes the wave to travel the full length of the line



(a)  $V(z)$  at  $t = T/2$

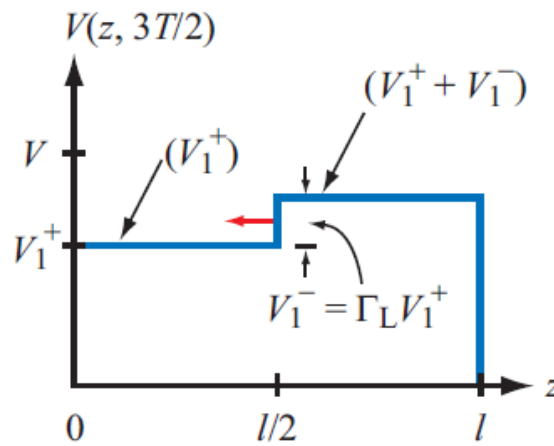


(b)  $V(z)$  at  $t = 3T/2$

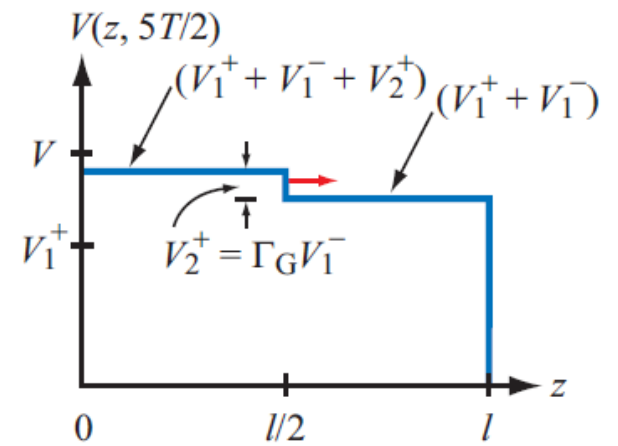

(c)  $V(z)$  at  $t = 5T/2$

$R_g = 4Z_0$  and  $R_L = 2Z_0$ . The corresponding reflection coefficients are  $\Gamma_L = 1/3$  and  $\Gamma_g = 3/5$ .

# Steady State Response

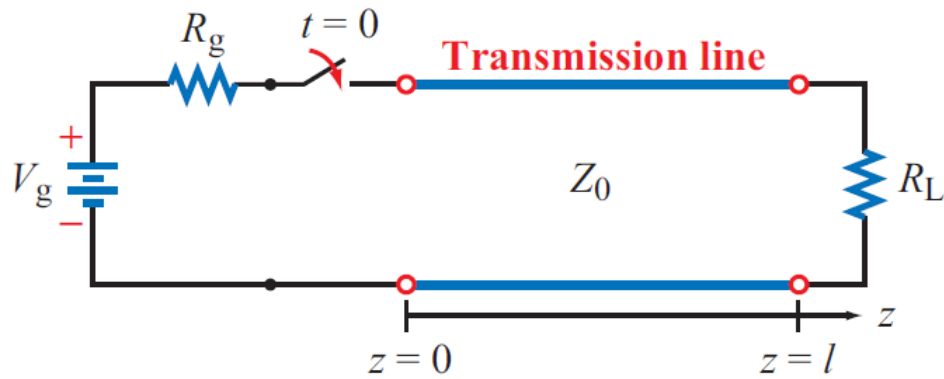


(a) Transmission-line circuit

$$V_{\infty} = \frac{V_g R_L}{R_g + R_L}$$


*The multiple-reflection process continues indefinitely, and the ultimate value that  $V(z, t)$  reaches as  $t$  approaches  $+\infty$  is the same at all locations on the transmission line.*

$$I_{\infty} = \frac{V_{\infty}}{R_L} = \frac{V_g}{R_g + R_L}$$


# Bounce Diagrams

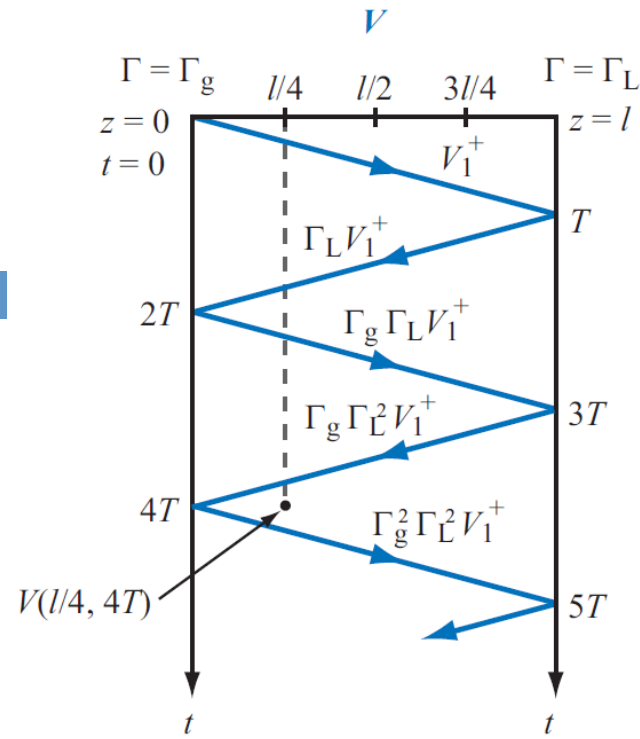

(a) Voltage bounce diagram

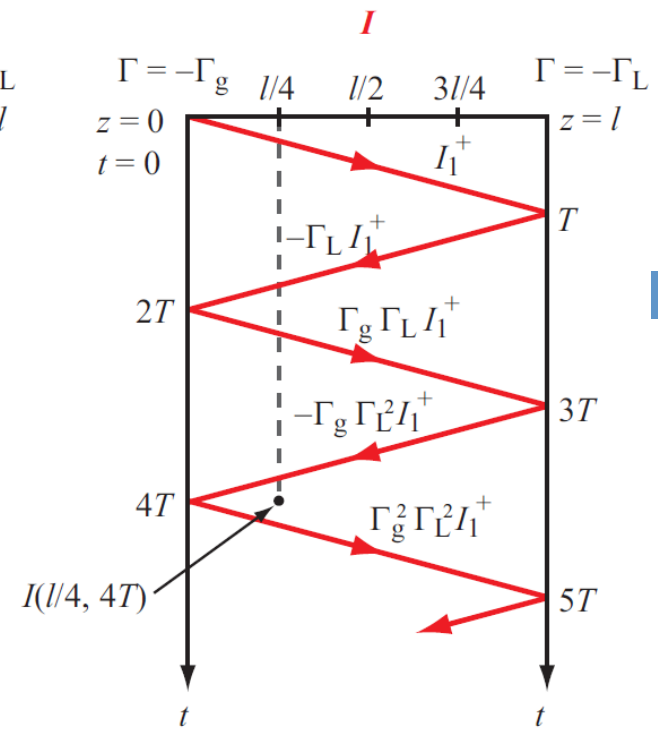

(b) Current bounce diagram

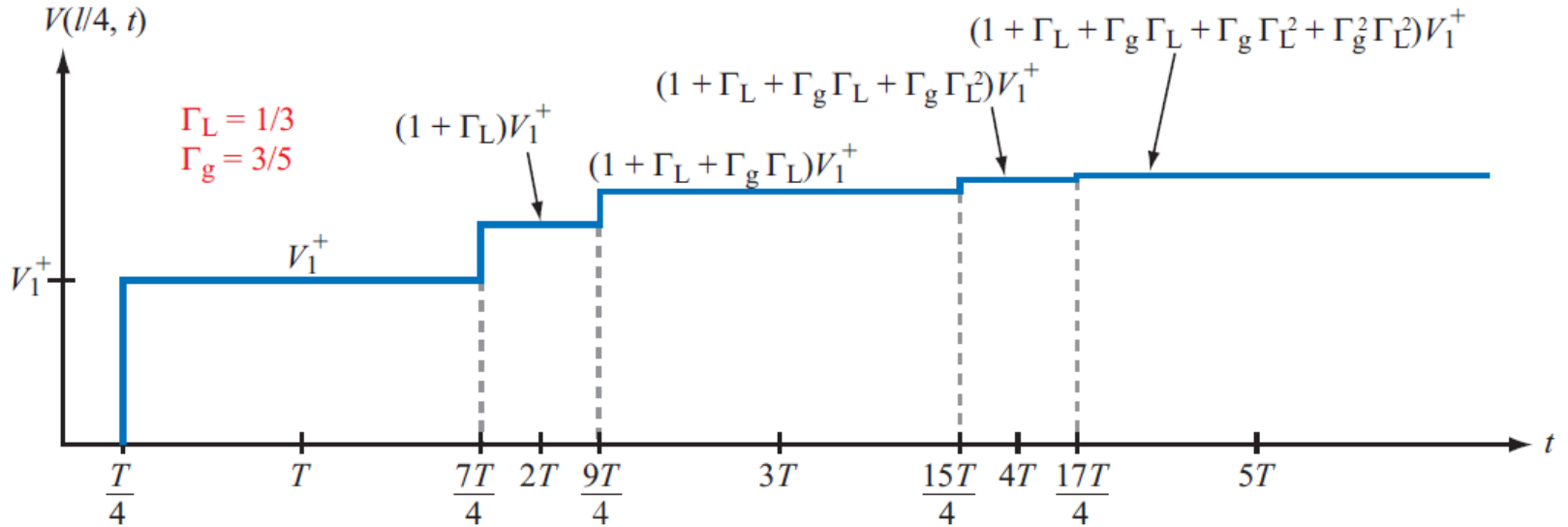

(c) Voltage versus time at  $z = l/4$