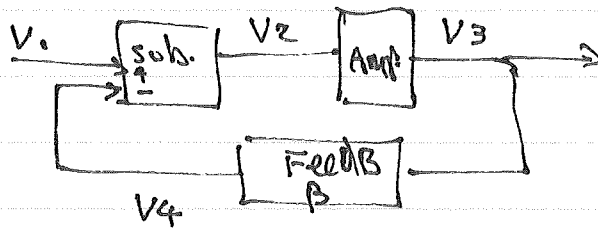


# PLL notes

PLL → Feedback oscillator

- { Amplification
- Positive feedback (regenerative - correct phase & freq.)
- { freq. determination (changes freq.) has a natural freq. source

loopback system




$$\frac{V_{out}}{V_{in}} = \frac{V_3}{V_1} = \frac{A_{ol}}{1 + \beta A_{ol}}$$

$$= A_{cl} \leftarrow \text{closed loop Gain}$$

$$A_{ol} = V_3/V_2$$


$$V_4 = \beta V_3$$

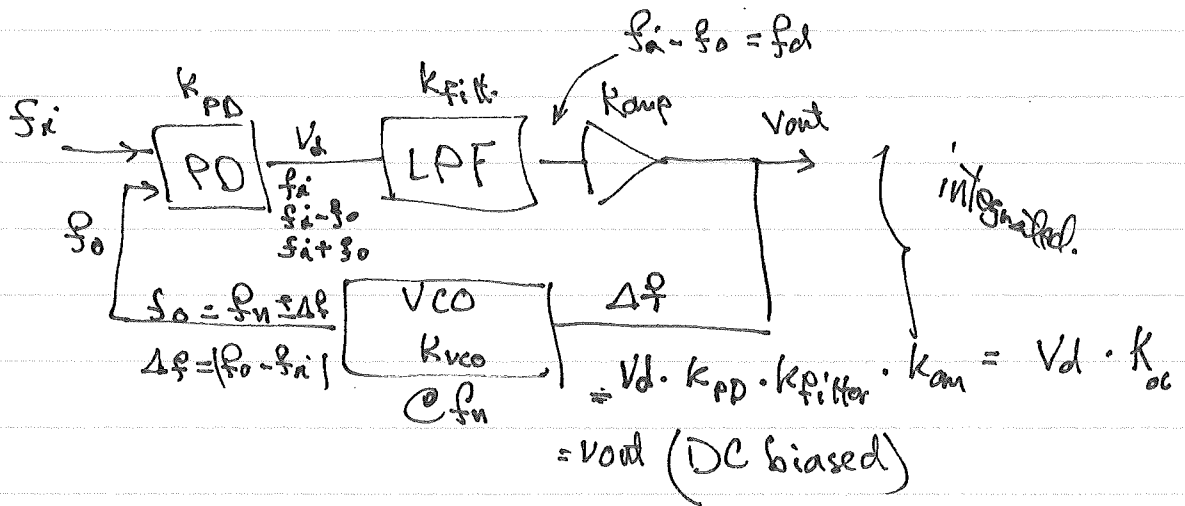

what it does:

→ Lock to freq.


→ Generate a voltage eq. to  $\phi_e$

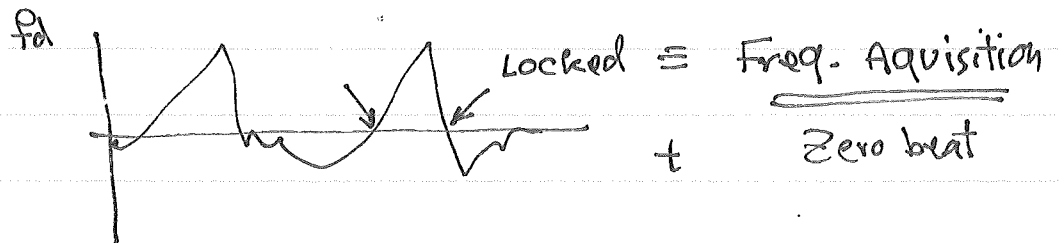

Locked  $f_i = f_o$

Acquisition time (Pull-in time)  $\Delta t \rightarrow f_i = f_o$

natural freq

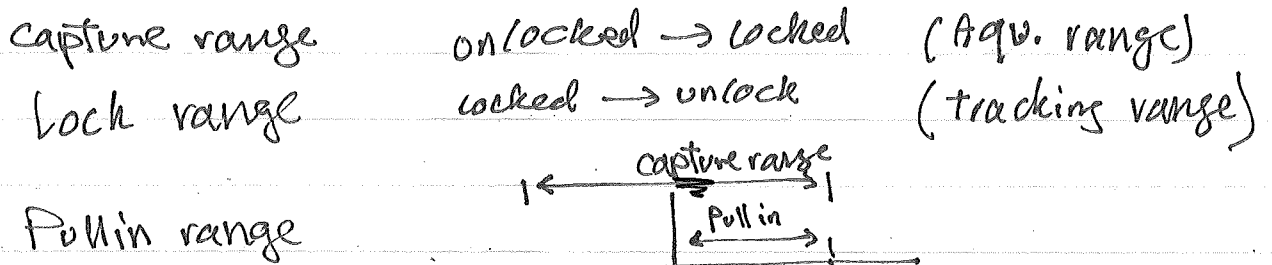



Example

$$f_n = 100 \text{ MHz}$$


$$\text{Pull-in range} = 1 \text{ percent of } f_n \rightarrow 100 \text{ MHz}$$

$$\text{hold in range} = 2 \text{ percent of } f_m \rightarrow 102 \text{ MHz}$$

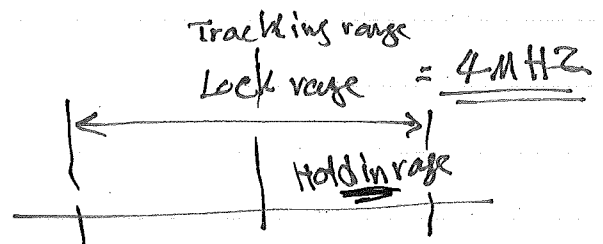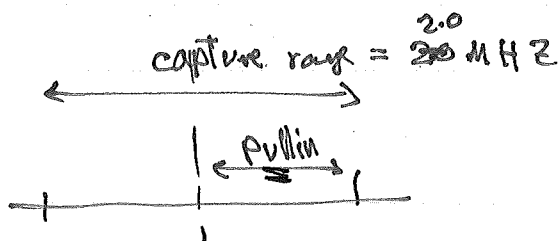Find  $\rightarrow$  capture range  
lock range




VCO

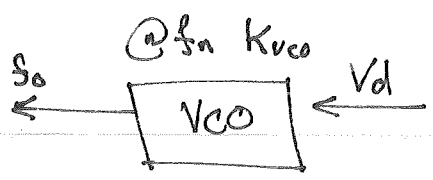



$$K_{VCO} = \text{Transfer function} = \frac{\text{Output}}{\text{Input}} = \frac{\Delta f}{\Delta V}$$

change in input freq.

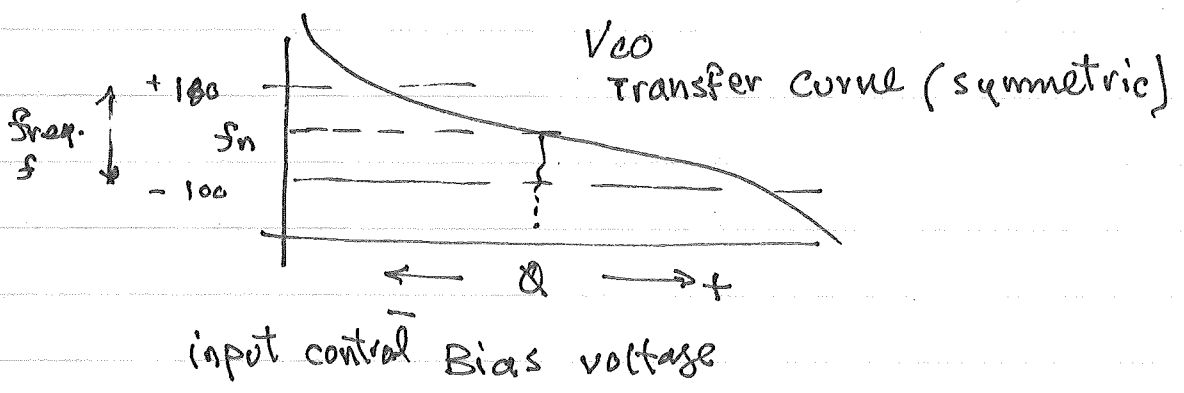

VCO transfer curve (symmetric)

# Phase Detection

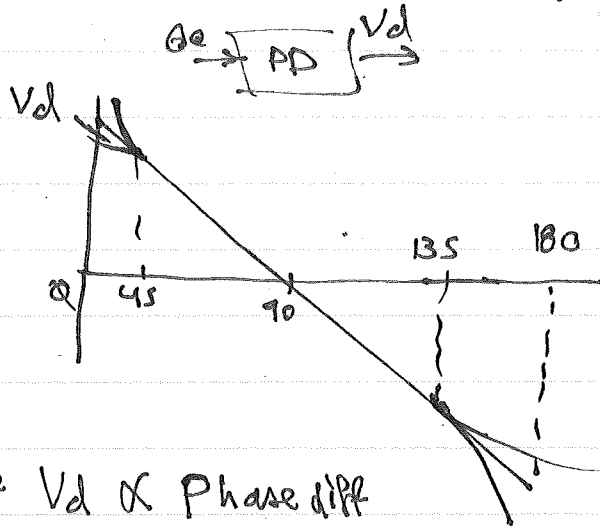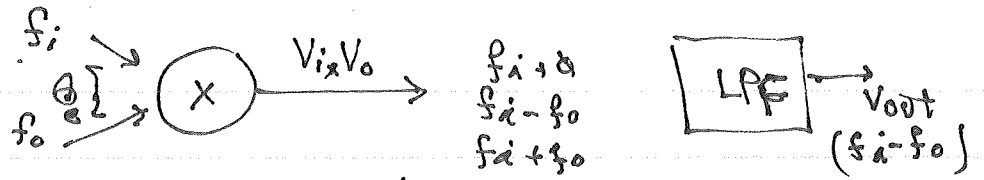


output voltage  $V_d \propto$  Phase diff

$$\theta_e = \theta_i - \theta_o$$

$$\text{Transfer function} = \frac{\text{Output}}{\text{Input}} = \frac{V_d}{\theta_e} \quad \left(\frac{V}{\text{rad}}\right) = K_{PD}$$

How do we convert phase diff to voltage?

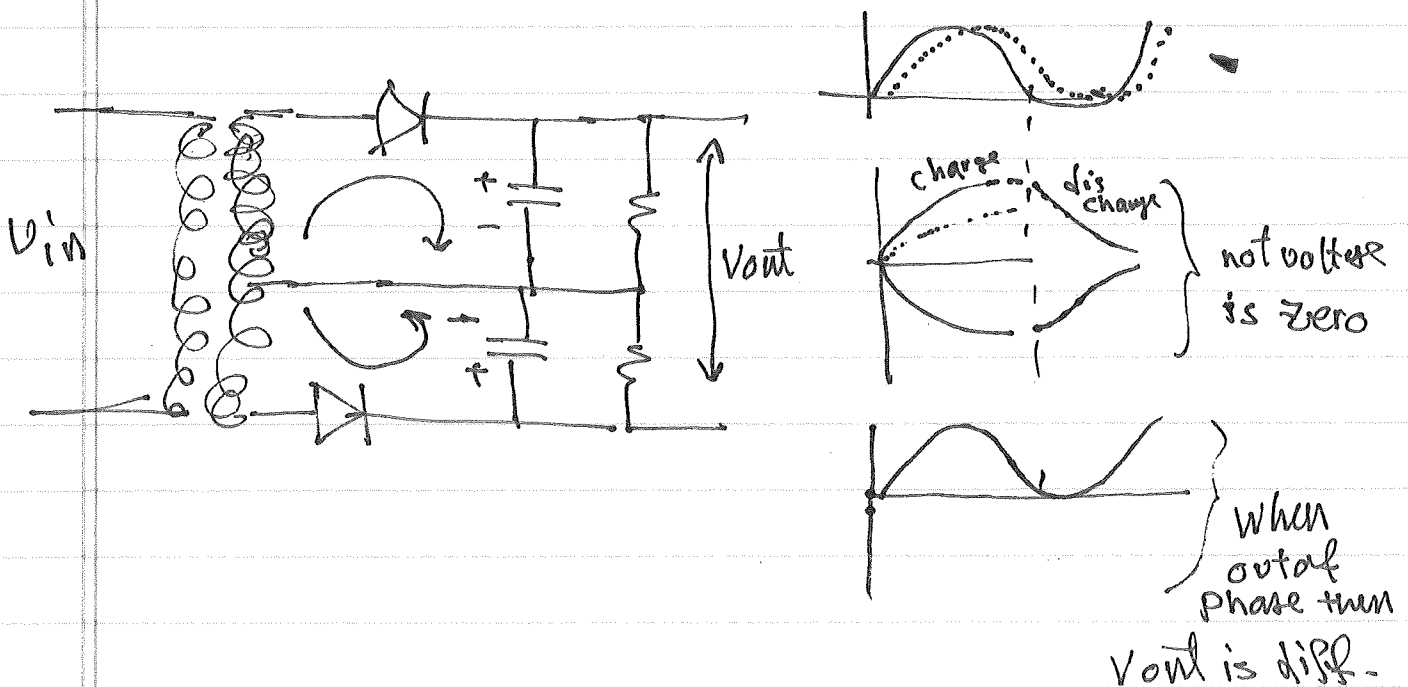

## PLL Terms

$$\text{open loop Gain} = K_{op} = K_{PD} \cdot K_{\text{filter}} \cdot K_{\text{amp}} \cdot K_{VCO} = K_{opLG}$$

$$K_{PD} = \text{phase detector gain} \quad (V/\text{rad})$$

$$K_{\text{filter}} = \text{filter gain} \quad (V/V)$$

$$K_{\text{amp}} = \quad (V/V)$$

$$K_{VCO} = \quad \text{Hz/Volt}$$

$$K_{\text{loop Gain}} = V/\text{rad} \cdot (V/V) \cdot (V/V) \cdot \frac{\text{Hz}}{\text{V}} = \underline{\underline{\text{Hz}/\text{rad}}}$$

or

$$K_{LG} = \frac{\text{Hz}}{\text{rad}} = \frac{\text{cycl}}{\text{rad-sec}} \cdot \frac{\text{rad } 2\pi}{\text{cycl}} = 2\pi K_{LG} \quad \text{rad/sec}$$

$$K_{VCO} = 20 \text{ kHz/V}$$

# PLL Example

Example  
P. 99

$$f_n = 200 \text{ kHz}$$

$$f_i = 210 \text{ kHz}$$


$$K_{PD} = 0.2 \text{ V/rad}$$

$$K_{Filter} = 1$$




$$K_{AMP} = 5$$

$$K_{VCO} = 20 \text{ kHz/V}$$

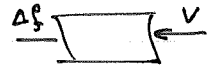

Find the following

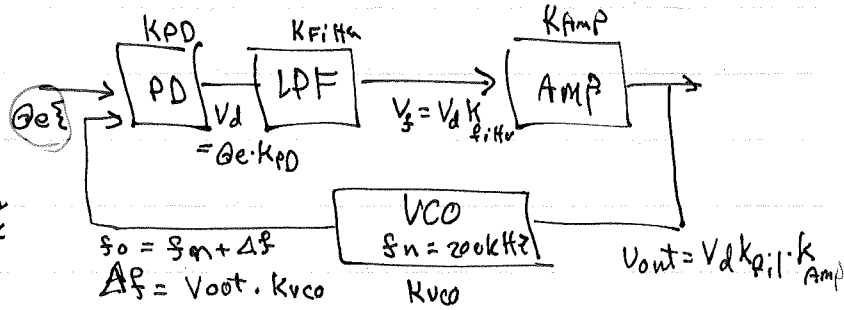
- + open loop gain (Hz/rad)  $\times \frac{\text{rad}}{\text{sec}}$
- + change in VCO for  $\Delta f$
- + PLL output voltage ( $V_{out}$ )
- + phase detector output voltage ( $V_d$ )
- + phase static error ( $\theta_e$ )
- + Hold-in range ( $\Delta f_{max}$ )



$$= \theta_e \cdot K_{PD} \cdot K_{Filter} \cdot K_{AMP} \cdot K_{VCO}$$

$$= \theta_e \cdot K_{openloop} \left( \text{rad} \cdot \frac{\text{Hz}}{\text{rad}} \right)$$

note: open loop gain:

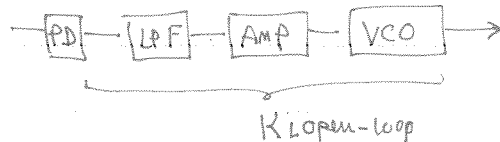

Solution

$$K_{L \text{ open loop}} = K_{PD} \cdot K_{\text{filter}} \cdot K_{\text{amp}} \cdot K_{VCO}$$

$$= 0.2 \text{ V/rad} \cdot 1 \cdot 5 \cdot 20 \text{ kHz/V} = \underline{\underline{20 \text{ kHz/rad}}}$$

a)

or

$$20 \frac{\text{kHz}}{\text{rad}} = 20 \frac{\text{k cycles}}{\text{rad-sec}} \cdot \frac{2\pi \text{ rad}}{\text{cycle}} = \boxed{125.6 \text{ k rad/sec}}$$

← note rad/sec

$$K_{\text{open loop (rad/sec)}} \text{ dB} = 20 \log (125.6 \times 10^3) = \underline{\underline{102 \text{ dB}}}$$

b)

$$\Delta f = f_i - f_n = 210 \text{ kHz} - 200 \text{ kHz} = \underline{\underline{10 \text{ kHz}}}$$

c)

$$V_{\text{out}} = V_d K_{\text{filter}} \cdot K_{\text{amp}}$$

$$K_{VCO} = \frac{\Delta f}{V_{\text{out}}} \Rightarrow V_{\text{out}} = \frac{\Delta f}{K_{VCO}} = \frac{10 \text{ kHz}}{20 \text{ kHz/V}} = \underline{\underline{0.5 \text{ V}}}$$

d)

$$V_d = K_{\text{filter}} \cdot K_{\text{amp}} = V_{\text{out}} \rightarrow V_d = (0.5) (1) (5) =$$

$$V_d = \frac{V_{\text{out}}}{K_{\text{filter}} \cdot K_{\text{amp}}} = \frac{0.5}{5 (1)} = \underline{\underline{0.1 \text{ V}}}$$

e)

$$\theta_e : \Delta f = \theta_e K_{L \text{ OLG}} \rightarrow \theta_e = \frac{\Delta f \text{ (Hz)}}{K_{L \text{ OLG}} \text{ (Hz/rad)}} = \frac{10 \text{ kHz}}{20 \text{ kHz/rad}} = \underline{\underline{0.5 \text{ rad}}}$$

→ 28.65 deg.  
pay attention

note: this is diff. from steady state  $\theta_e$ .


f)

Holdings-Hold-in range ( $\Delta f_{\text{max}}$ )

$$\left(\frac{\pi}{2} \text{ rad}\right) \cdot K_{L \text{ OLG}} \left(\frac{\text{Hz}}{\text{rad}}\right) = \left(\frac{\pi}{2}\right) (20 \text{ kHz}) = \boxed{31.4 \text{ kHz}}$$

locked

Away from the natural freq.

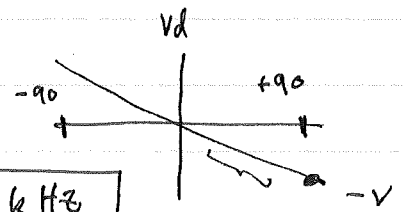


note  $\text{lock range} = 2\Delta f_{\max}$

$\text{capture range (LPF)} = \frac{2\sqrt{\Delta f_{\max}}}{RC \text{ (LPF)}} \leftarrow \text{Function of Filter}$

$\text{Lock range} > \text{capture range}$

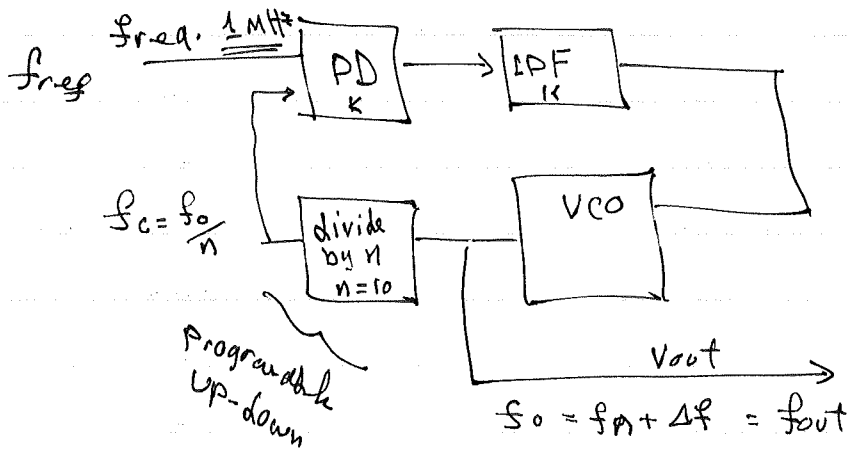Freq. synthesizer (single loop PLL)  $\rightarrow$  freq multiplier



$f_0 = n \text{ freq.} = [1, 10] \text{ freq.}$   
 $= 1 \text{ MHz to } 10 \text{ MHz}$

$K_V = \frac{K_{PD} \cdot K_{LPF} \cdot K_{VCO}}{n}$  Loop Gain